

Ex. For capacitors

Example 1

- (a) Calculate the charge stored on a 3-pF capacitor with 20V across it.
- (b) Find the energy stored in the capacitor.

Solution:

(a) Since $q = Cv$,

$$q = 3 \times 10^{-12} \times 20 = 60 \text{pC}$$

(b) The energy stored is

$$w = \frac{1}{2} Cv^2 = \frac{1}{2} \times 3 \times 10^{-12} \times 400 = 600 \text{pJ}$$

Example 2

- The voltage across a 5- μF capacitor is

$$v(t) = 10 \cos 6000t \text{ V}$$

Calculate the current through it.

Solution:

- By definition, the current is

$$\begin{aligned} i &= C \frac{dv}{dt} = 5 \times 10^{-6} \frac{d}{dt} (10 \cos 6000t) \\ &= -5 \times 10^{-6} \times 6000 \times 10 \sin 6000t = -0.3 \sin 6000t \text{ A} \end{aligned}$$

Example 3

- Determine the voltage across a 2- μ F capacitor if the current through it is

$$i(t) = 6e^{-3000t} \text{ mA}$$

Assume that the initial capacitor voltage is zero.


Solution:

- Since $v = \frac{1}{C} \int_0^t i dt + v(0)$ and $v(0) = 0$,

$$\begin{aligned} v &= \frac{1}{2 \times 10^{-6}} \int_0^t 6e^{-3000t} dt \cdot 10^{-3} = \frac{3 \times 10^3}{-3000} e^{-3000t} \Big|_0^t \\ &= (1 - e^{-3000t}) \text{ V} \end{aligned}$$

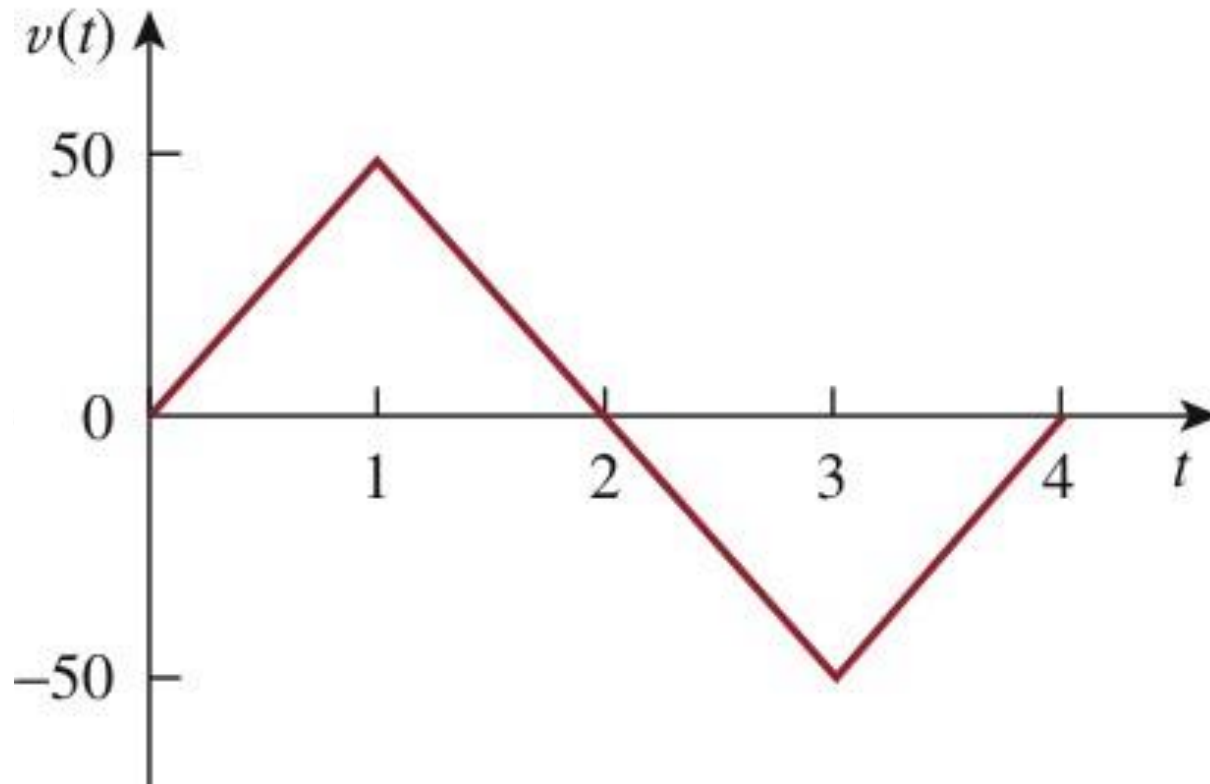
Example 4

- Determine the current through a $200\text{-}\mu\text{F}$ capacitor whose voltage is shown below.



Solution:

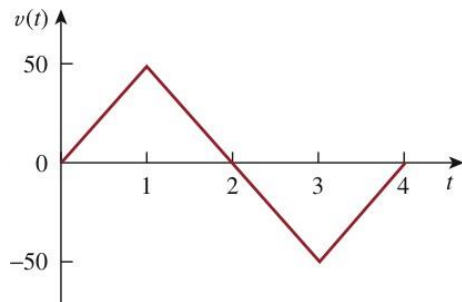- The voltage waveform can be described mathematically as




$$v(t) = \begin{cases} 50t \text{ V} & 0 < t < 1 \\ 100 - 50t \text{ V} & 1 < t < 3 \\ -200 + 50t \text{ V} & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases}$$

- Since $i = C \, dv/dt$ and $C = 200 \, \mu\text{F}$, we take the derivative of $v(t)$ to obtain

$$i(t) = 200 \times 10^{-6} \times \begin{cases} 50 & 0 < t < 1 \\ -50 & 1 < t < 3 \\ 50 & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases} = \begin{cases} 10\text{mA} & 0 < t < 1 \\ -10\text{mA} & 1 < t < 3 \\ 10\text{mA} & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases}$$

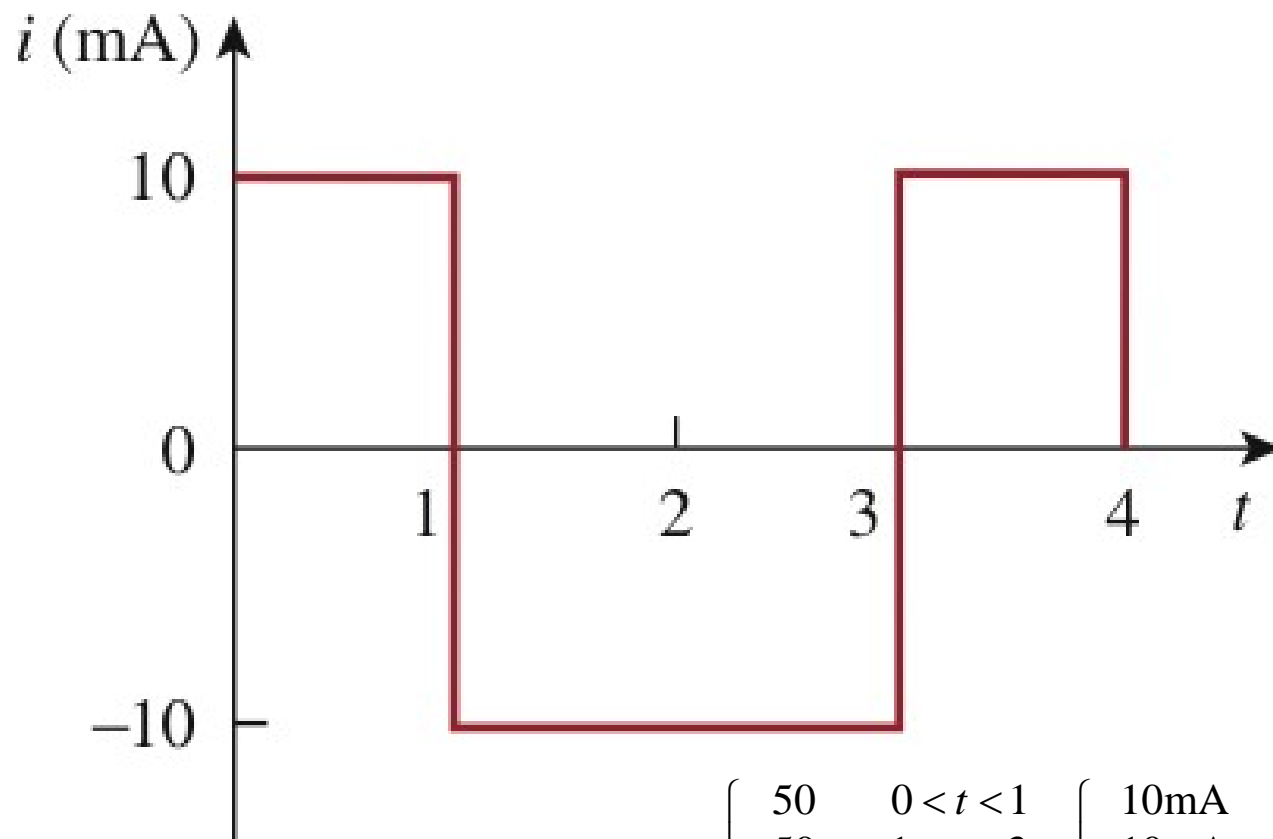
$$v(t) = \begin{cases} 50t \text{ V} & 0 < t < 1 \\ 100 - 50t \text{ V} & 1 < t < 3 \\ -200 + 50t \text{ V} & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases}$$



$$i(t) = 200 \times 10^{-6} \times \begin{cases} 50 & 0 < t < 1 \\ -50 & 1 < t < 3 \\ 50 & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases} = \begin{cases} 10\text{mA} & 0 < t < 1 \\ -10\text{mA} & 1 < t < 3 \\ 10\text{mA} & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases}$$

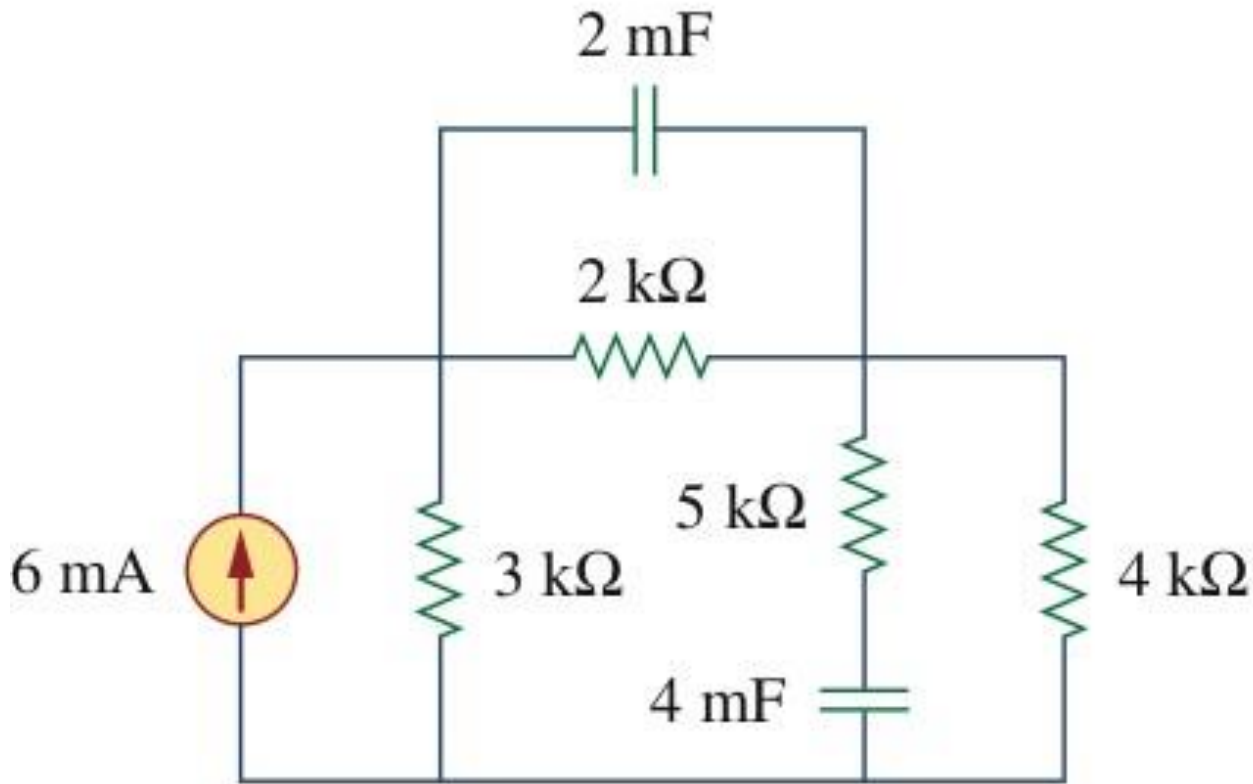Example 5

- Obtain the energy stored in each capacitor under **dc** condition (**freq=0, $t=\infty$**).




Solution:

- DC condition: each capacitor \rightarrow an open circuit.

– By current division,
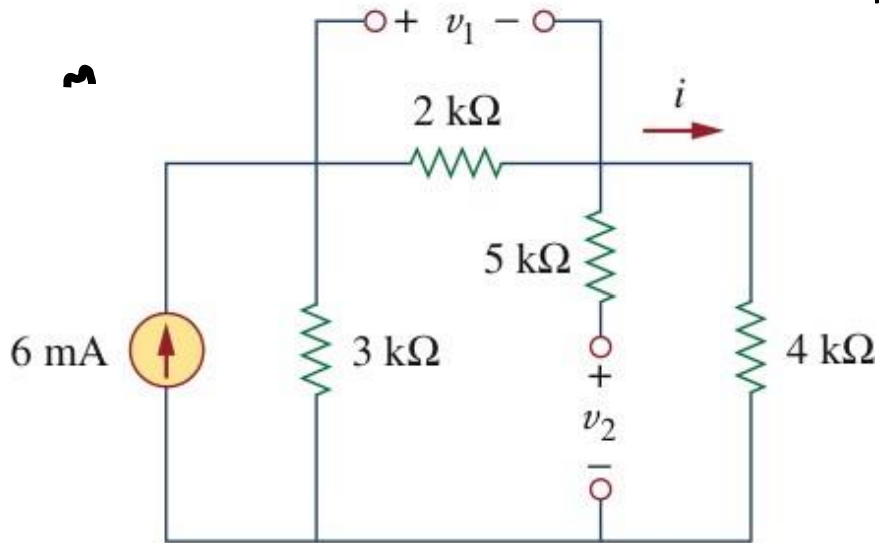
$$i = \frac{3}{3 + 2 + 4} (6\text{mA}) = 2\text{mA}$$



$$\therefore v_1 = 2000i = 4\text{ V},$$


$$v_2 = 4000i = 8\text{ V}$$

$$\therefore w_1 = \frac{1}{2} C_1 v_1^2 = \frac{1}{2} (2 \times 10^{-3}) (4)^2 = 16\text{mJ}$$

$$w_2 = \frac{1}{2} C_2 v_2^2 = \frac{1}{2} (4 \times 10^{-3}) (8)^2 = 128\text{mJ}$$

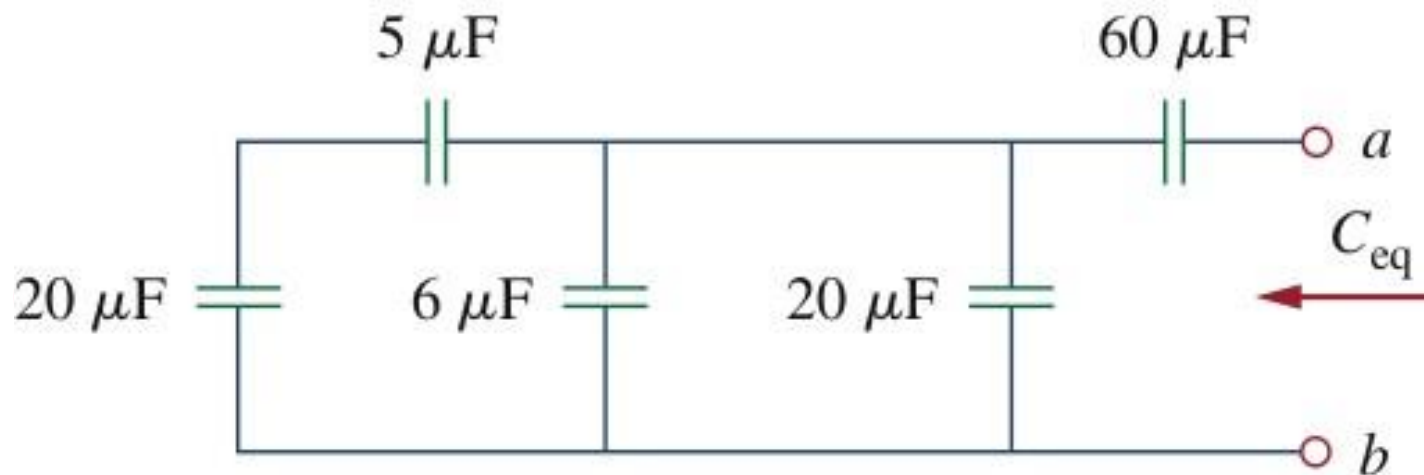Example 6

- Find the equivalent capacitance seen between terminals a and b of the circuit



Solution:

- $20 - \mu\text{F}$ and $5 - \mu\text{F}$ capacitors are in series:

$$\therefore \frac{20 \times 5}{20 + 5} = 4 \mu\text{F}$$

- $4 - \mu\text{F}$ capacitor is in parallel with the $6 - \mu\text{F}$ and $20 - \mu\text{F}$ capacitors:


$$\therefore 4 + 6 + 20 = 30 \mu\text{F}$$


- $30 - \mu\text{F}$ capacitor is in series with the $60 - \mu\text{F}$ capacitor.

$$C_{eq} = \frac{30 \times 60}{30 + 60} \mu\text{F} = 20 \mu\text{F}$$

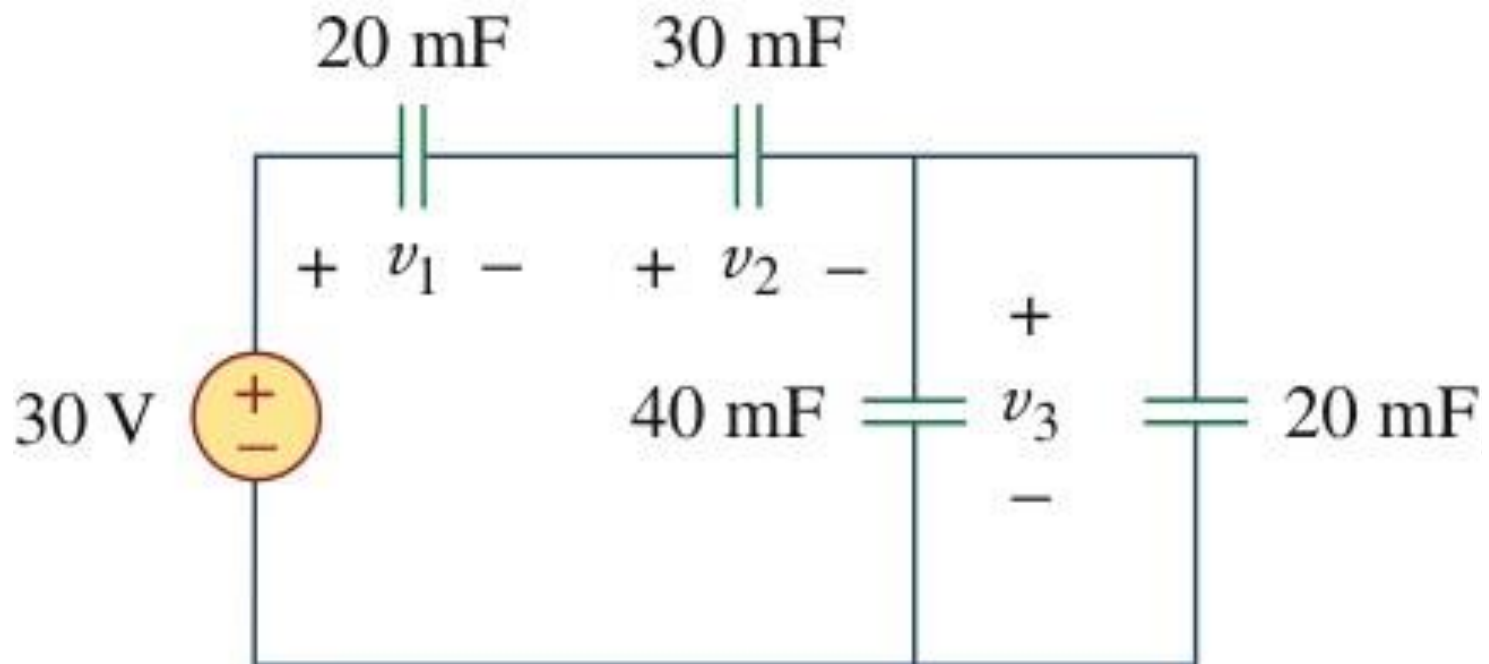Example 7

- Find the voltage across each capacitor.



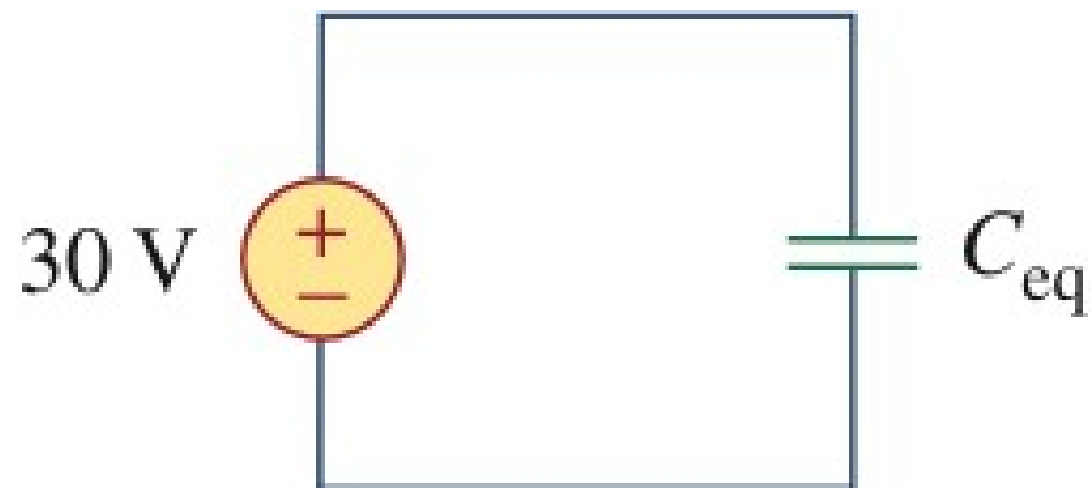

Solution:


- Two parallel capacitors:

$$\therefore C_{eq} = \frac{1}{\frac{1}{60} + \frac{1}{30} + \frac{1}{20}} \text{ mF} = 10 \text{ mF}$$

- Total charge

$$q = C_{eq} v = 10 \times 10^{-3} \times 30 = 0.3 \text{ C}$$

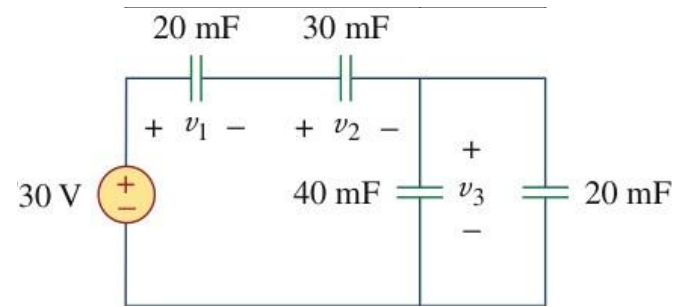- This is the charge on the 20-mF and 30-mF capacitors, because they are in series with the 30-v source.
 - A crude way to see this is to imagine that charge acts like current, since $i = dq/dt$



- Therefore,
$$v_1 = \frac{q}{C_1} = \frac{0.3}{20 \times 10^{-3}} = 15 \text{ V},$$

$$v_2 = \frac{q}{C_2} = \frac{0.3}{30 \times 10^{-3}} = 10 \text{ V}$$

- Having determined v_1 and v_2 , we now use KVL to determine v_3 by

$$v_3 = 30 - v_1 - v_2 = 5 \text{ V}$$

- Alternatively, since the 40-mF and 20-mF capacitors are in parallel, they have the same voltage v_3 and their combined capacitance is 40+20=60mF.

$$\therefore v_3 = \frac{q}{60 \text{ mF}} = \frac{0.3}{60 \times 10^{-3}} = 5 \text{ V}$$

Ex. For inductors

Example 1

- The current through a 0.1-H inductor is $i(t) = 10te^{-5t}$ A. Find the voltage across the inductor and the energy stored in it.

Solution:

Since $v = L \frac{di}{dt}$ and $L = 0.1\text{H}$,

$$v = 0.1 \frac{d}{dt} (10te^{-5t}) = e^{-5t} + t(-5)e^{-5t} = e^{-5t} (1 - 5t) \text{ V}$$

The energy stored is

$$w = \frac{1}{2} Li^2 = \frac{1}{2} (0.1) 100t^2 e^{-10t} = 5t^2 e^{-10t} \text{ J}$$

Example 2

- Find the current through a 5-H inductor if the voltage across it is

$$v(t) = \begin{cases} 30t^2, & t > 0 \\ 0, & t < 0 \end{cases}$$

Also find the energy stored within $0 < t < 5\text{s}$.

Assume $i(0)=0$.

Solution:

Since $i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$ and $L = 5\text{H}$.

$$i = \frac{1}{5} \int_0^t 30t^2 dt + 0 = 6 \times \frac{t^3}{3} = 2t^3 \text{ A}$$

The power $p = vi = 60t^5$, and the energy stored is then

$$w = \int p dt = \int_0^5 60t^5 dt = 60 \left. \frac{t^6}{6} \right|_0^5 = 156.25 \text{ kJ}$$

Alternatively, we can obtain the energy stored using


$$\begin{aligned} w(5) - w(0) &= \frac{1}{2} Li^2(5) - \frac{1}{2} Li(0) \\ &= \frac{1}{2} (5)(2 \times 5^3)^2 - 0 = 156.25 \text{ kJ} \end{aligned}$$

Example 3

- Consider the circuit, under dc conditions, find:


(a) i , v_C , and i_L .

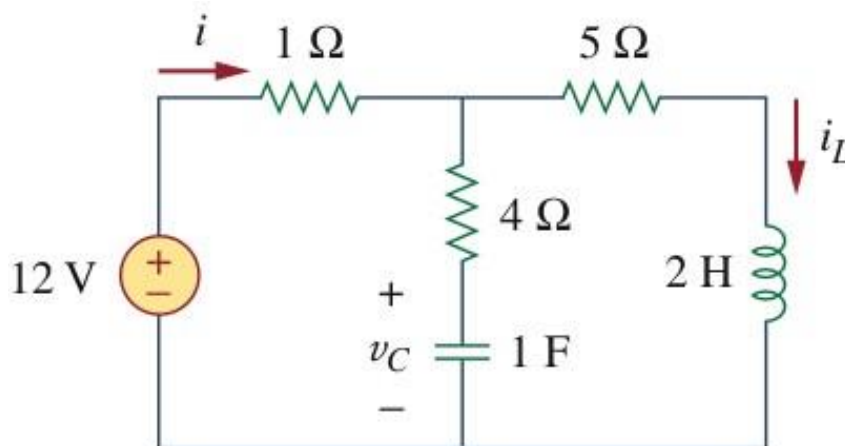(b) the energy stored in the capacitor and inductor.



Solution:

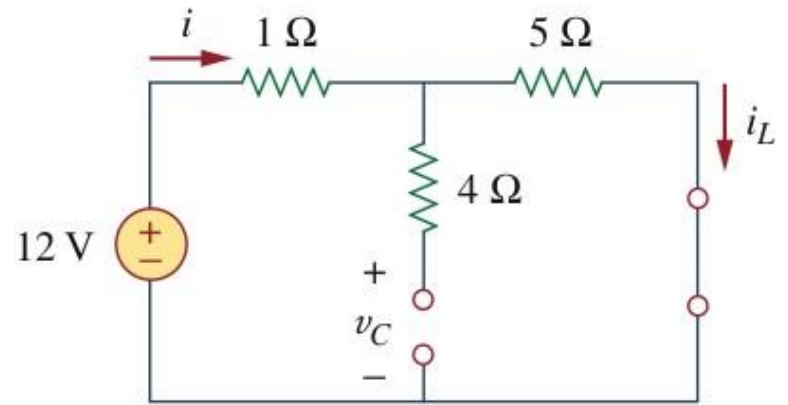(a) Under dc condition :
capacitor \rightarrow open circuit
inductor \rightarrow short circuit




$$i = i_L = \frac{12}{1+5} = 2A, v_c = 5i = 10V$$

$$(b) \quad w_c = \frac{1}{2} C v_c^2 = \frac{1}{2} (1)(10^2) = 50J,$$

$$w_L = \frac{1}{2} L i^2 = \frac{1}{2} (2)(2^2) = 4J$$

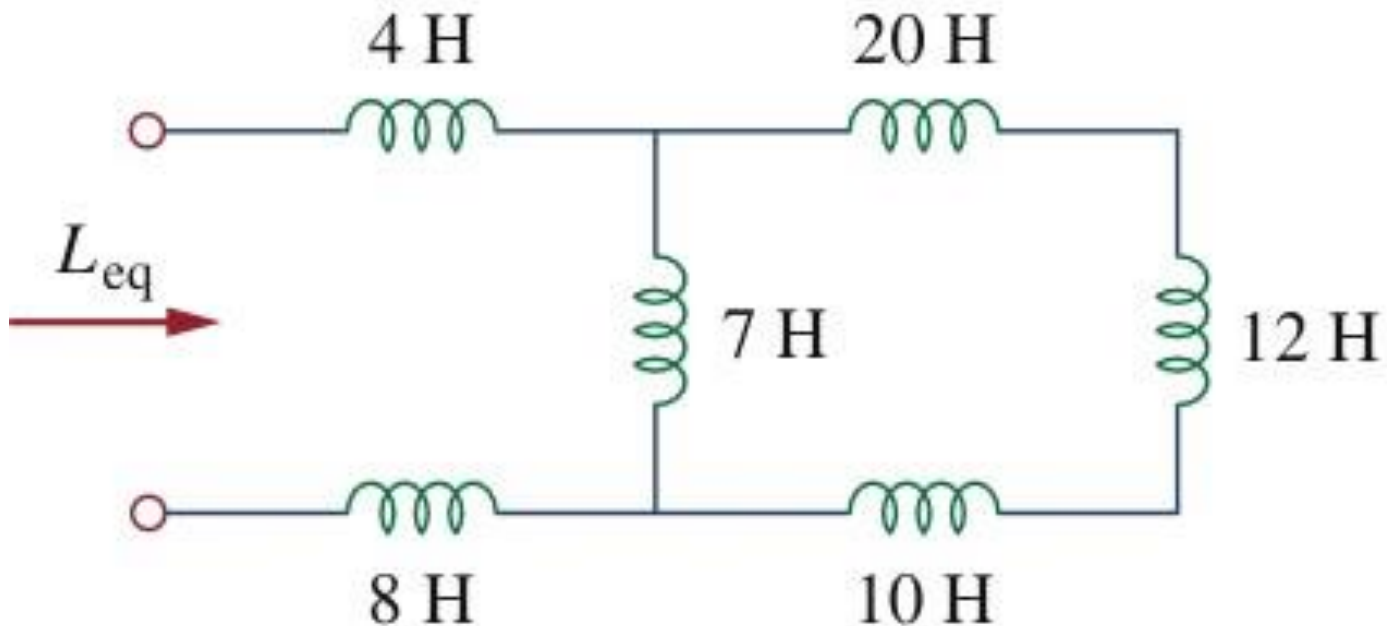Example 4

- Find the equivalent inductance of the circuit.



- **Solution:**


Series : 20H, 12H, 10H
→ 42H

Parallel : $\frac{7 \times 42}{7 + 42} = 6H$

$$\therefore L_{eq} = 4 + 6 + 8 = 18H$$

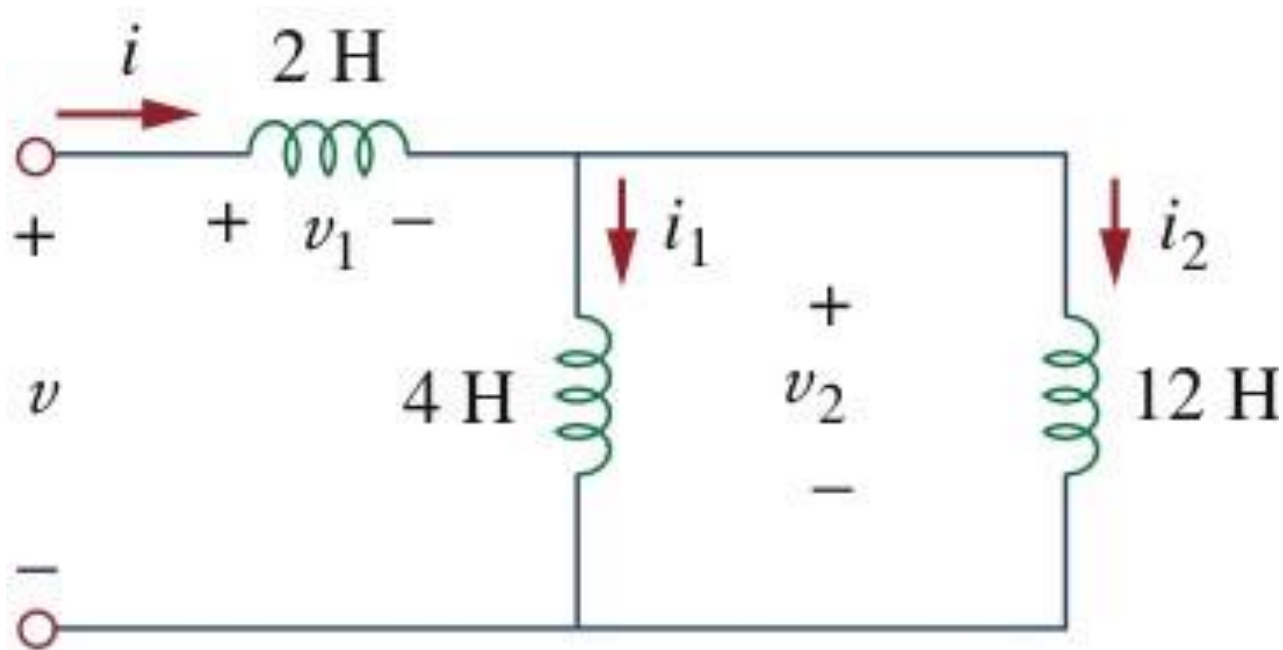Example 5

- $i(t) = 4(2 - e^{-10t})\text{mA}$. If $i_2(0) = -1\text{mA}$,
– find : (a) $i_1(0)$
(b) $v(t)$, $v_1(t)$, and $v_2(t)$;
(c) $i_1(t)$ and $i_2(t)$



Solution:

$$(a) \ i(t) = 4(2 - e^{-10t})\text{mA} \rightarrow i(0) = 4(2 - 1) = 4\text{mA}.$$

$$\therefore i_1(0) = i(0) - i_2(0) = 4 - (-1) = 5\text{mA}$$

(b) The equivalent inductance is

$$L_{eq} = 2 + 4 \parallel 12 = 2 + 3 = 5\text{H}$$

$$\therefore v(t) = L_{eq} \frac{di}{dt} = 5(4)(-1)(-10)e^{-10t}\text{mV} = 200e^{-10t}\text{mV}$$

$$v_1(t) = 2 \frac{di}{dt} = 2(-4)(-10)e^{-10t}\text{mV} = 80e^{-10t}\text{mV}$$

$$\therefore v_2(t) = v(t) - v_1(t) = 120e^{-10t}\text{mV}$$

$$(c) \ i = \frac{1}{L} \int_0^t v(t) dt + i(0) \Rightarrow$$

$$i_1(t) = \frac{1}{4} \int_0^t v_2 dt + i_1(0) = \frac{120}{4} \int_0^t e^{-10t} dt + 5 \text{ mA}$$

$$= -3e^{-10t} \Big|_0^t + 5 \text{ mA} = -3e^{-10t} + 3 + 5 = 8 - 3e^{-10t} \text{ mA}$$

$$i_2(t) = \frac{1}{12} \int_0^t v_2 dt + i_2(0) = \frac{120}{12} \int_0^t e^{-10t} dt - 1 \text{ mA}$$

$$= -e^{-10t} \Big|_0^t - 1 \text{ mA} = -e^{-10t} + 1 - 1 = -e^{-10t} \text{ mA}$$

Note that $i_1(t) + i_2(t) = i(t)$

Example 6

- Find the equivalent inductance of the circuit.

