

CET 141: Day 7

Dr. Noori KIM

Agenda

- R, L, and C under AC conditions
- Complex plane and Phasor

All tools for today

1. Phasor

$$- v(t) = A \cos(\omega t + \theta) [V] \rightarrow V_{phasor} = Ae^{j\theta} [V]$$

2. Impedance ($Z=R+jX$ [Ω])

$$- Z_R = R [\Omega]$$

$$- Z_C = \frac{1}{j\omega C} = jX_C = -j\frac{1}{\omega C} [\Omega]$$

$$- Z_L = jX_L = j\omega L [\Omega]$$

Recap: R, L, and C under DC conditions

- DC sources (i.e, $V=9V$ or $I=3A$),
 - Resistance R
 - Follows Ohm's law, $V=IR$
 - Capacitance, C
 - Opened, $I=0$
 - Inductance, L
 - Shorted, $V=0$ (just a wire)

Complete R = Transient R + Steady-State R

Tell us everything that you remember about each response.

If a source is AC

→ through RLC circuits


→ Steady-State R is also AC

→ phasor analysis can be used in *frequency domain*




$$\omega = 2\pi f$$

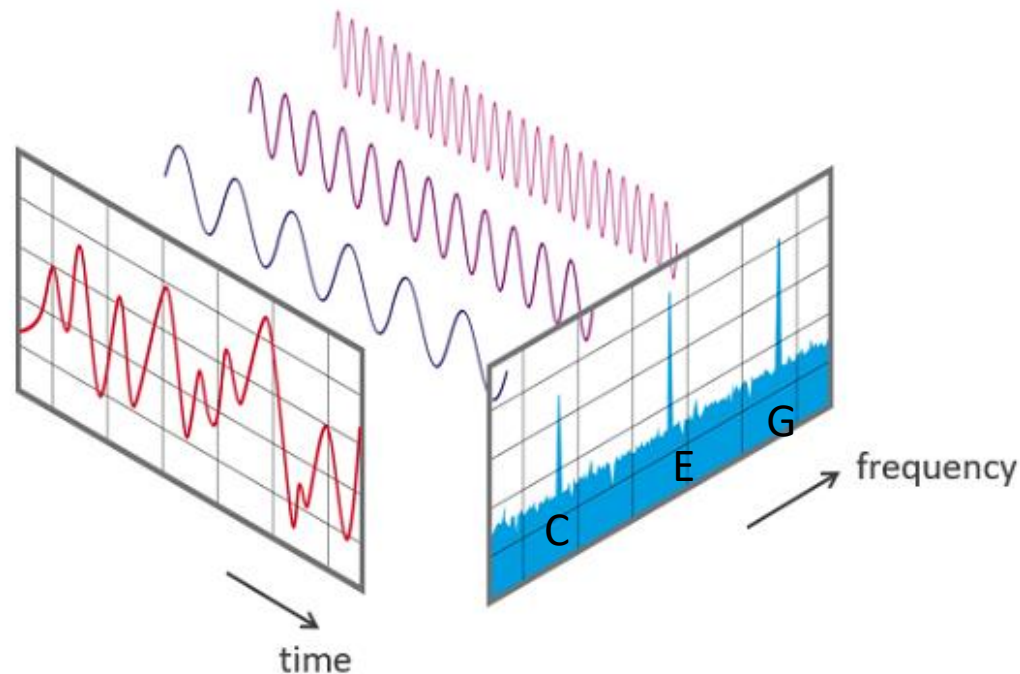- ω and f are both measures of frequency
- ω [rad/sec] and f [Hz]




Cycles (radian) and Frequency relation

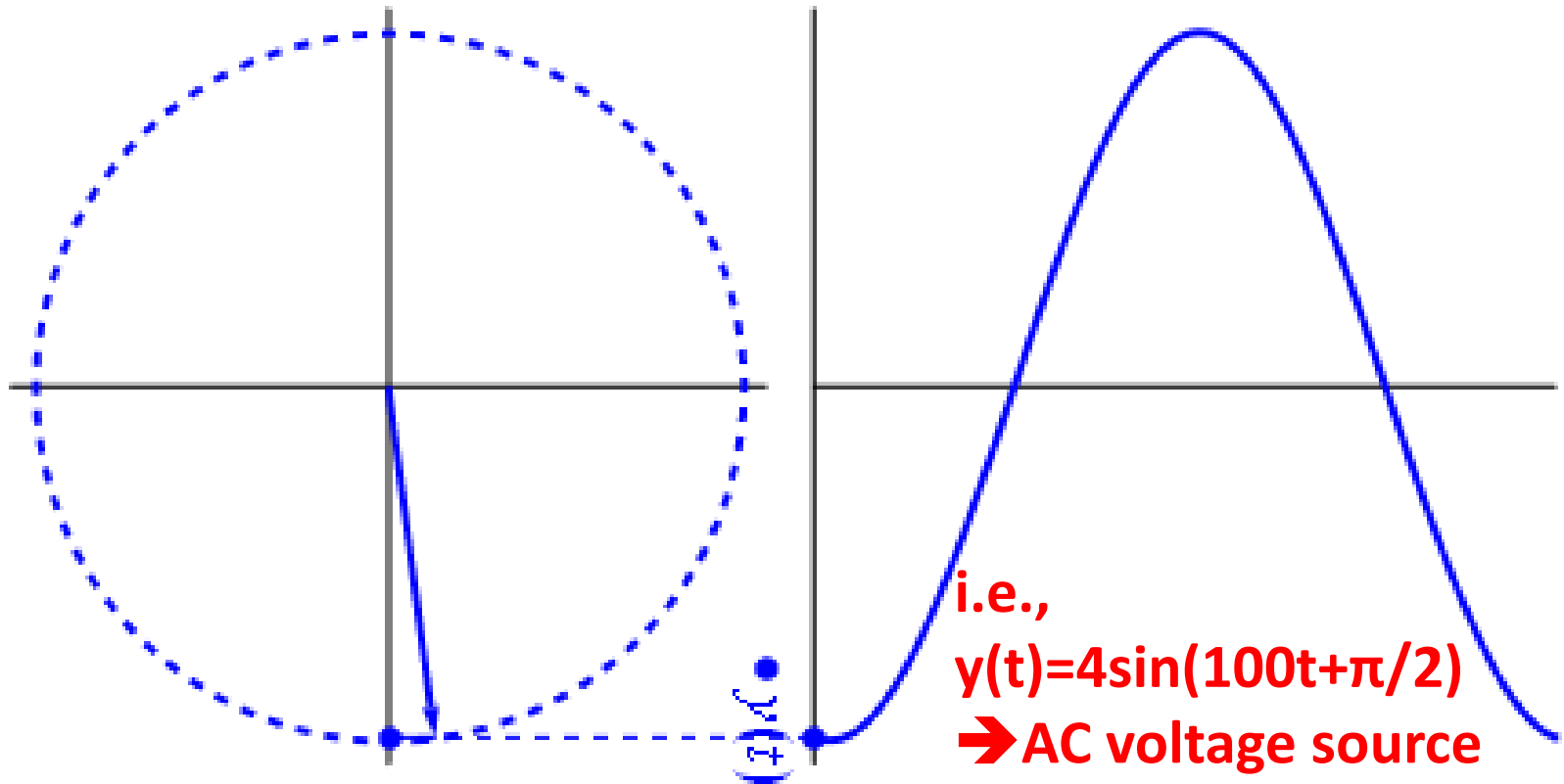

**Look at the time domain graph and think about why only steady-state R is considered in frequency domain analysis*

R under AC

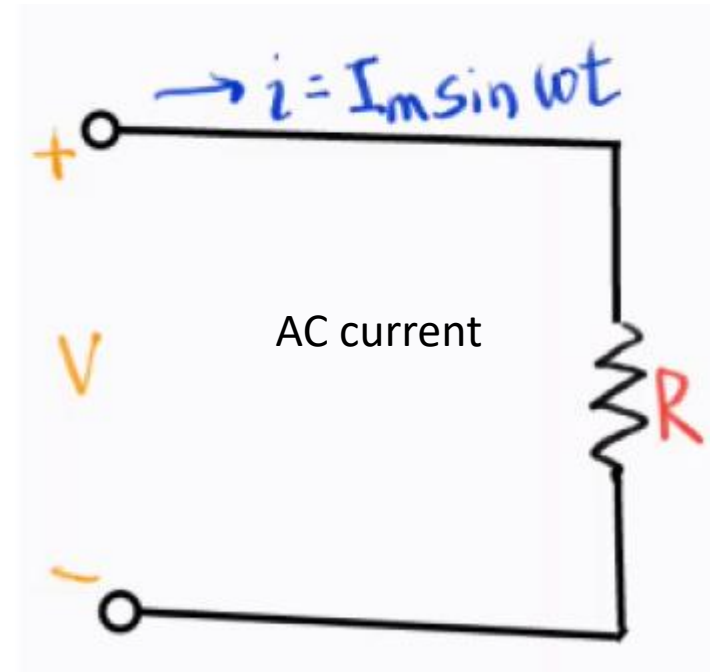
- How do we calculate V?
 - Based on Ohm's law $V=iR$
 $V = Ri = \mathbf{R}I_m \sin \omega t$ [V]
- R: a proportional constant between voltage v and current i
- If **i** is a sinusoidal form, then **v** is also a sinusoidal form sharing the same ω (angular freq)
 - (+) No phase diff.
 - Same phase = same angle...



$$\begin{aligned} i &= \mathbf{I_m} \sin \omega t \text{ [A]} \\ V &= RI_m \sin \omega t \\ &= \mathbf{V_m} \sin \omega t \text{ [V]} \end{aligned}$$


$$i = I_m \sin \omega t [A], V = V_m \sin \omega t [V]$$

Max values!!!

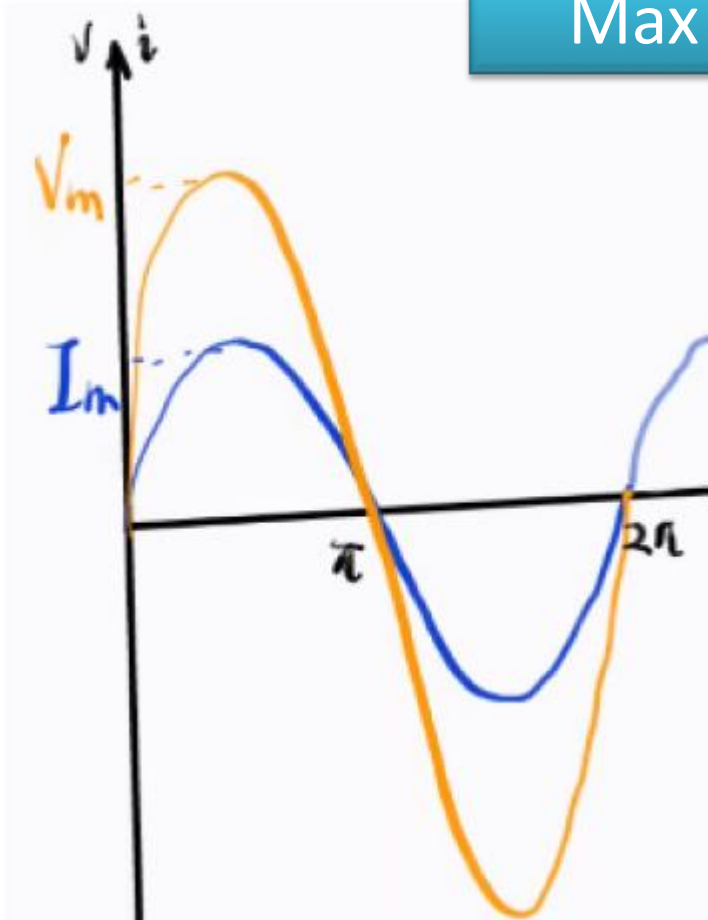

- Whether you use a current source or a voltage source;
 - the current flows through R or
 - the voltage across the R
- R Will not change.

Example: find i

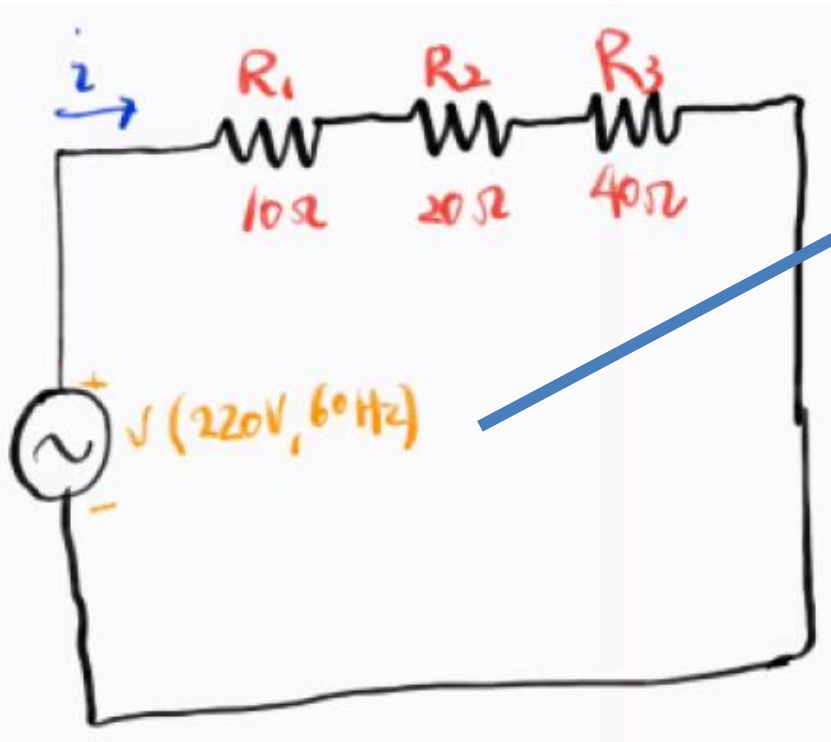

The V is given in this format (think about all appliances that we have 110V-60Hz...110V-50Hz...)

- 220V is RMS amplitude, not V_{max}
 - $\sqrt{2} * 220 = V_{max}$
- $V = 220\sqrt{2} \sin(60 * 2\pi t)$ [V]

Note that $\omega = 2\pi f$

- $R_{eq} = 10 + 20 + 40 = 70\Omega$
- Therefore

$$i = 220\sqrt{2} \sin(60 * 2\pi t) / 70 \text{ [A]}$$

L under AC

- How do we calculate V?


$$L = \frac{N^2 \mu A}{\ell} \rightarrow \Phi = L \cdot I \rightarrow V = \frac{\Delta \Phi}{\Delta t} \rightarrow V = L \cdot \frac{d}{dt} I$$

$$v = L \frac{d}{dt} (I_m \sin \omega t)$$

$$= \omega L I_m \cos \omega t$$

$$= \omega L I_m \sin(\omega t + 90^\circ) \text{ [V]}$$

$$i = I_m \sin \omega t \text{ [A]}$$

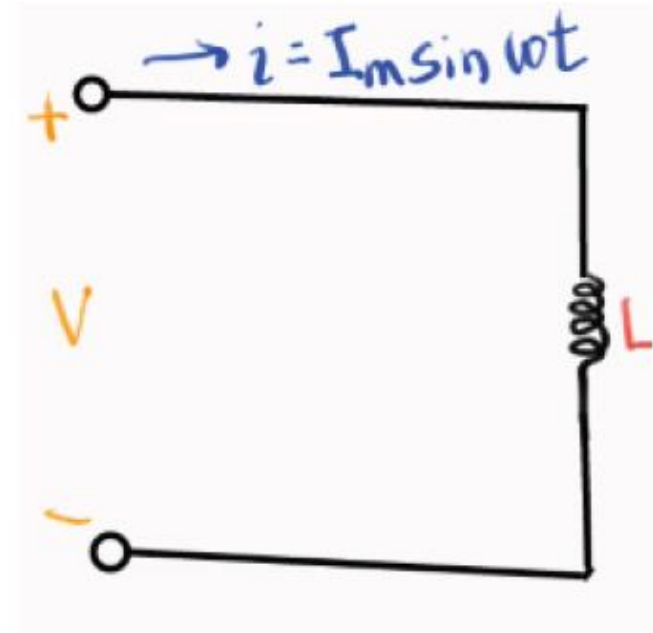

Do you see the clear difference compared to the R case?


$$\cos(\omega t + \phi) = \sin(\omega t + \phi + 90^\circ)$$

$$\sin(\omega t + \phi) = \cos(\omega t + \phi - 90^\circ)$$

$$-\sin(\omega t) = \sin(\omega t \pm 180^\circ)$$

$$-\cos(\omega t) = \cos(\omega t \pm 180^\circ)$$

$$-\cos(\omega t) = \sin(\omega t \pm 270^\circ)$$

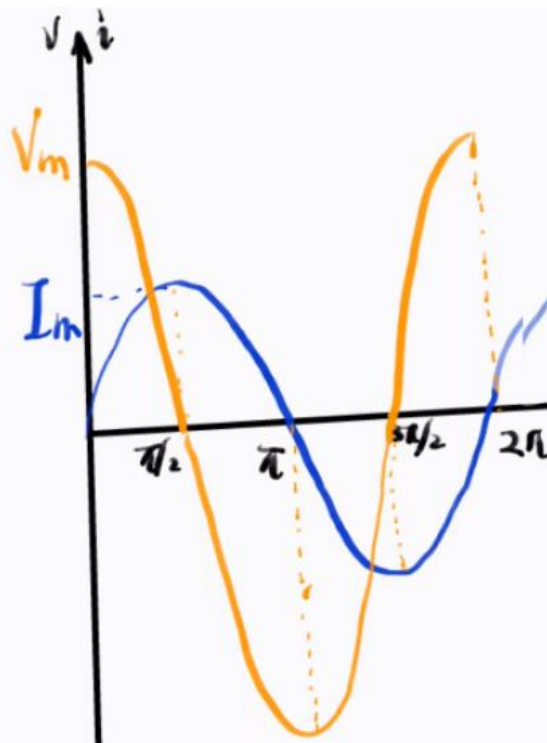

$$-\sin(\omega t) = \sin(-\omega t)$$

$$\cos(\omega t) = \cos(-\omega t)$$

$$i = I_m \sin \omega t \text{ [A]},$$

$$V = \omega L I_m \sin(\omega t + 90^\circ) \text{ [V]}$$

OMG!!! There is a phase difference between the V and I!!!




- ω is the same for V and I, but affects magnitude of I
- The V period is shifted $\frac{\pi}{2}$ from the I (to the left)
- The max V (V_m) is multiplied by ωL from the max I (I_m)

ωL : Inductive reactance X_L

- Imag. Coeffic. of impedance Z with a unit of Ω -ohm
 - $Z=R+jX$ [Ω]
 - Z : impedance
 - R : resistance (real part), X : reactance (imaginary part) where units for both R and X are Ω
- Basically it is a resistance (disturbing current flows) but depends on the frequency

- Therefore if *frequency ($\omega=2\pi f$) increases*, ωL *increases*.
 - An Inductor: Blocking high frequency signals.
 - At DC status, $f=0 \rightarrow \omega =0$:
 - Basically no inductive restiveness in the circuit, as $X_L=\omega L=0$
 - An Inductor behaves Just like a wire

Example find L_{\min}

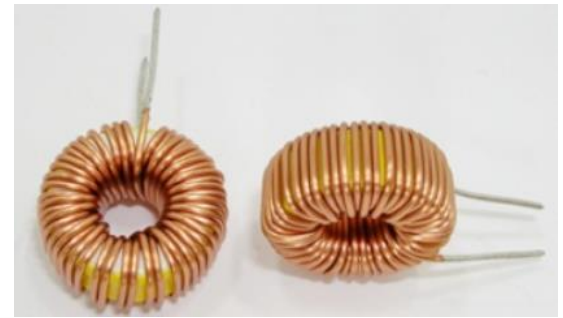

- A choke coil is an inductor used to block higher-frequency alternating current (AC) in an electrical circuit, while passing lower-frequency or direct current (DC).
- Determine the inductance of choke coil to exceed 8000Ω at 60Hz and above.

$$X_L = \omega L = 2\pi f L$$
$$L \geq \frac{X_L}{2\pi f} = \frac{8000}{2\pi * 60} \approx 21.22 [H]$$

C under AC

- How do we calculate V?

$$C = \frac{\epsilon \cdot A}{d} \rightarrow Q = CV \rightarrow I = \frac{\Delta Q}{\Delta t} \rightarrow I_c = C \cdot \frac{d}{dt} V_c \rightarrow V_c = \frac{1}{C} \int I_c dt$$


$$v = \frac{1}{C} \int I_m \sin \omega t dt$$

$$= -\frac{1}{\omega C} I_m \cos \omega t$$

$$= \frac{1}{\omega C} I_m \sin(\omega t - 90^\circ) \text{ [V]}$$



$$i = I_m \sin \omega t \text{ [A]}$$

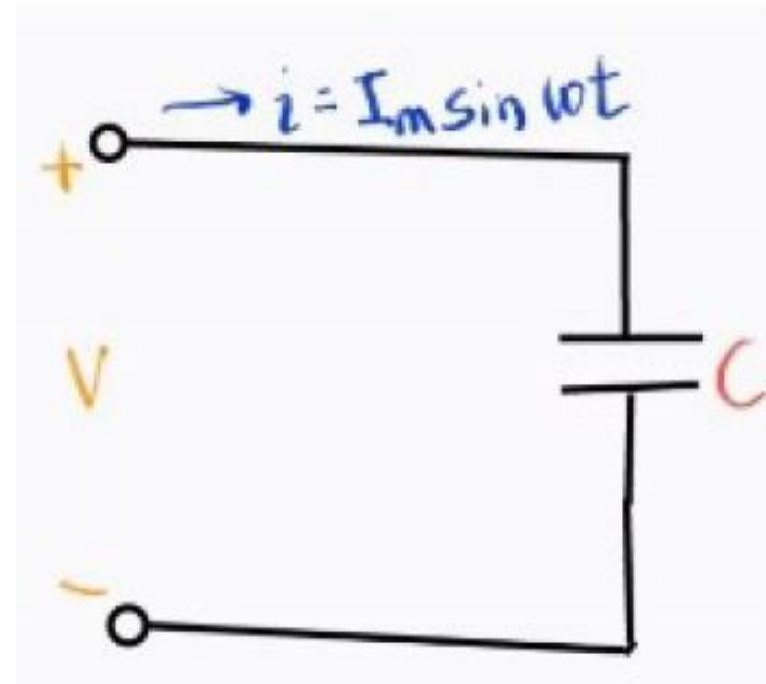


$$\cos(\omega t + \phi) = \sin(\omega t + \phi + 90^\circ)$$

$$\sin(\omega t + \phi) = \cos(\omega t + \phi - 90^\circ)$$

$$-\sin(\omega t) = \sin(\omega t \pm 180^\circ)$$

$$-\cos(\omega t) = \cos(\omega t \pm 180^\circ)$$

$$-\cos(\omega t) = \sin(\omega t \pm 270^\circ)$$

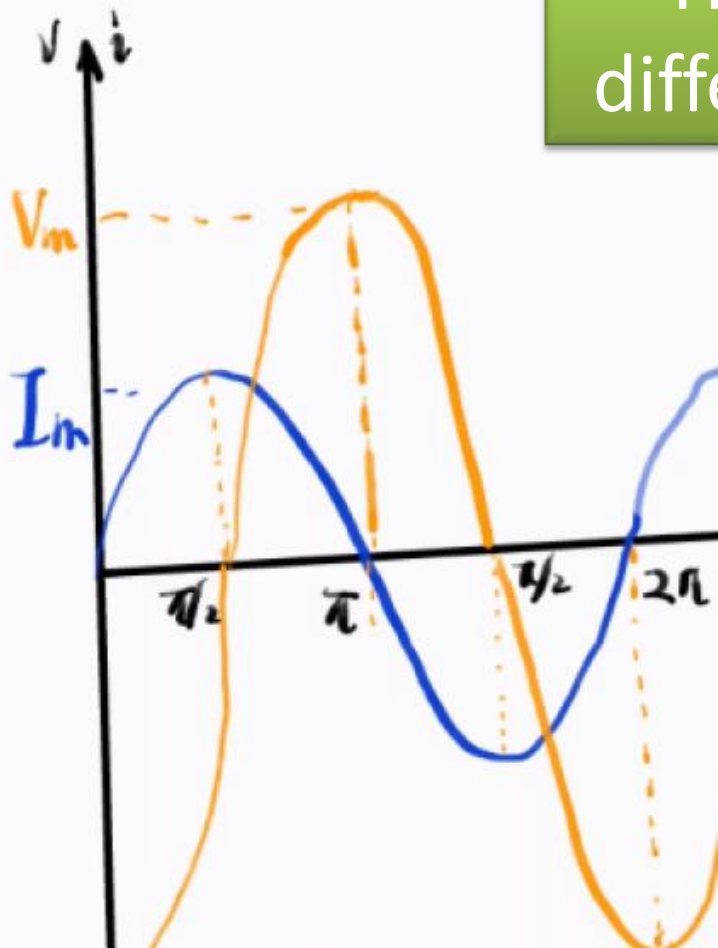

$$-\sin(\omega t) = \sin(-\omega t)$$

$$\cos(\omega t) = \cos(-\omega t)$$

$$i = I_m \sin \omega t [A],$$

$$V = \frac{1}{\omega C} I_m \sin(\omega t - 90^\circ) [V]$$

Here we have another phase difference between the V and I!!!



- ω is same for both V and I, but affects magnitude of V
- The V period is shifted $\frac{\pi}{2}$ from the I (to the right)
- The max V (V_m) is multiplied by $\frac{1}{\omega C}$ from the max I (I_m)

$\frac{-1}{\omega C}$ or $\frac{1}{\omega C}$: Capacitive reactance X_C

- Imag. Coeffic. of impedance Z with a unit of Ω -ohm
 - $Z=R+jX$ [Ω], where Z: impedance
 - R: resistance (real part), X: reactance (imaginary part) where units for both R and X are Ω
- Basically **it is a resistance (disturbing current flows)** but **depends on the frequency**

- Therefore if *frequency ($\omega=2\pi f$) decreases*,

$$\frac{1}{\omega C} \text{ *increases* .}$$

– A capacitor: **Blocking low** frequency signals.

– At DC status, $f=0 \rightarrow \omega =0$:

- Basically infinity capacitive reactance in the circuit, as $X_C=\infty$, current can't flow this path.
- A capacitor behaves Just like disconnected wires (O.C.)

LL pass
CH pass

Summary on the impedance

- An impedance (Z) is a concept to be defined for (in) the frequency domain
 - It is a sum of resistance (R) and reactance (X)
 - $Z=R+jX \rightarrow$ unit: “Ohm” \rightarrow a measure of restiveness of the circuit \rightarrow if Z is high, electrons are hard to flow (low current)
- A resistor (R)
 - has an impedance form of $R \rightarrow$ resistance
- An inductor (L)
 - has an impedance form of $j\omega L \rightarrow$ reactance
- A Capacitor (C)
 - Has an impedance for of $\frac{1}{j\omega C} \rightarrow$ reactance

Please, Do remember..

- Capacitive reactance $X_c: 1/(\omega C)$
 - between V and I , ωt : no change only -90 phase diff.
- Inductive reactance $X_L: \omega L$
 - between V and I , ωt : no change only $+90$ phase diff.
- Impedance $Z=R+jX$ [Ω], where
 - Series $Z_{eq}=Z_1+Z_2+Z_3....$
 - $\text{Re}\{Z_{eq}\}$: from resistors, $\text{Im}\{Z_{eq}\}$: inductors and caps
 - Parallel $1/Z_{eq}=1/Z_1+1/Z_2+1/Z_3....$
 - $\text{Re}\{Z_{eq}\}$ and $\text{Im}\{Z_{eq}\}$: combination of R, C, L

$$\sin(a + b) = \sin(a)\cos(b) + \cos(a)\sin(b)$$

$$\sin\left(\frac{\pi}{2} + x\right) = \sin\left(\frac{\pi}{2}\right) \cdot \cos(x) + \cos\left(\frac{\pi}{2}\right) \cdot \sin(x)$$

$$\sin\left(\frac{\pi}{2}\right) = 1$$

$$\cos\left(\frac{\pi}{2}\right) = 0$$

So we have :

$$\sin\left(\frac{\pi}{2} + x\right) = \cos(x)$$

$$\begin{aligned}\cos x &= \sin\left(\frac{\pi}{2} - x\right) = \sin\left(-\left(x - \frac{\pi}{2}\right)\right) \\ &= -\sin\left(x - \frac{\pi}{2}\right)\end{aligned}$$

R under AC

$$i = I_m \sin \omega t [A], V = V_m \sin \omega t [V]$$



Max values!!!




L under AC

$$i = I_m \sin \omega t [A], V = \omega L I_m \sin(\omega t + 90^\circ) [V]$$

C under AC

$$i = I_m \sin \omega t [A], V = \frac{1}{\omega C} I_m \sin(\omega t - 90^\circ) [V]$$

R L C

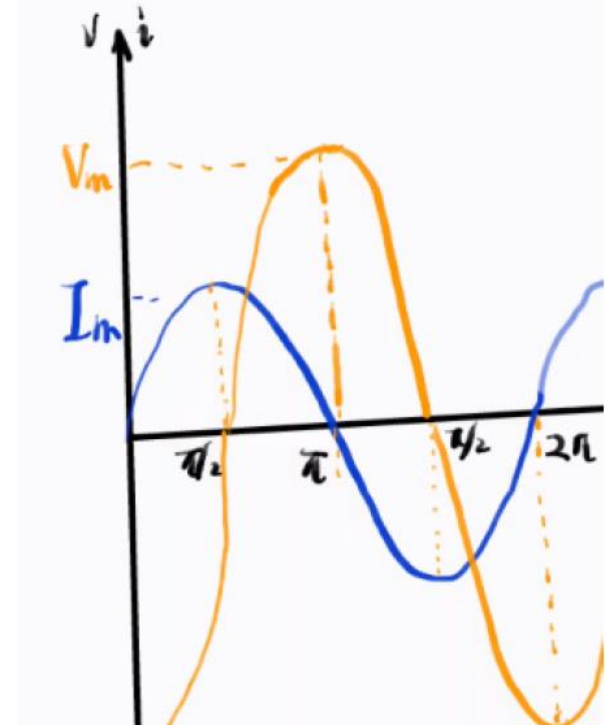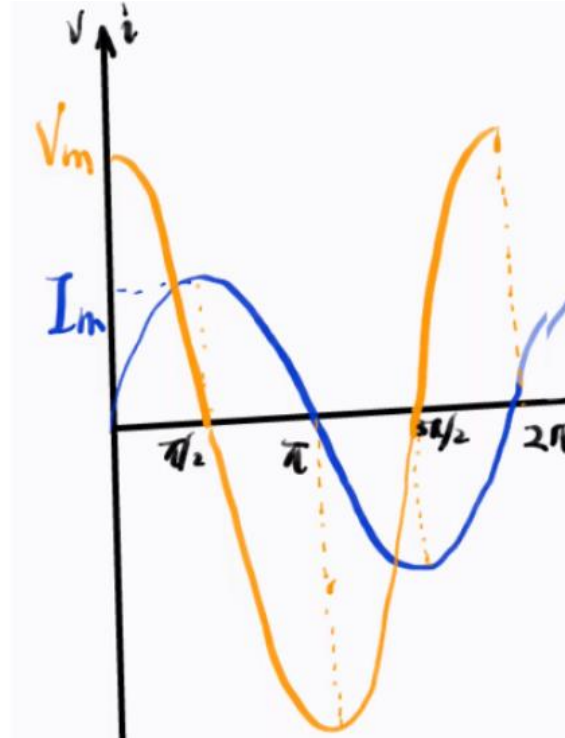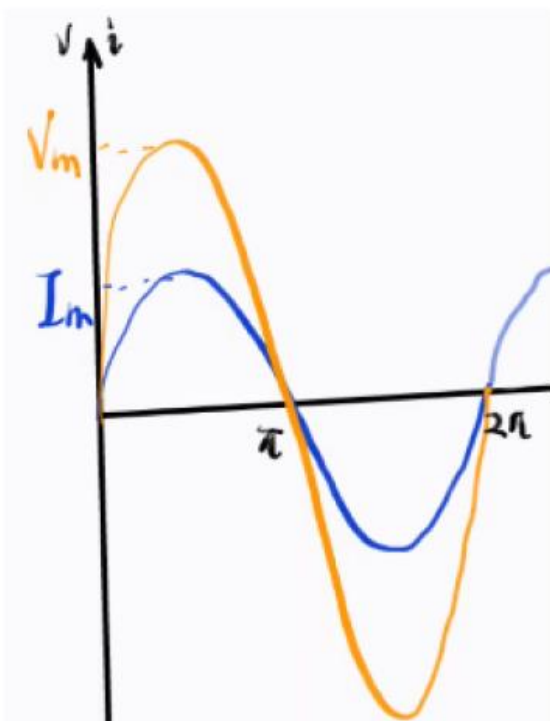

To the frequency domain

COMPLEX PLANE AND PHASOR

- Before learning phasor, we need to review the complex plane
- There are two methods to represent complex numbers
 - Rectangular (Cartesian) coordinate
 - Polar (angular) coordinate
- **$y = a + jb \rightarrow \text{Re}\{Y\} = a$ and $\text{Im}\{Y\} = jb$**
 - $\rightarrow |y| = \sqrt{a^2 + b^2} = r, \text{angle}\{y\} = \tan^{-1} \frac{b}{a} = \theta$
 - $\rightarrow y = r e^{j\theta}$
 - $\rightarrow y = r(\cos \theta + j \sin \theta)$

Euler's formula: $e^{jx} = \cos x + j \sin x$


VIF: very important formula

Euler's formula: $e^{jx} = \cos x + j \sin x$

Along with i_c and v_L


Rectangular (Cartesian) coordinate

- $y = a + jb$

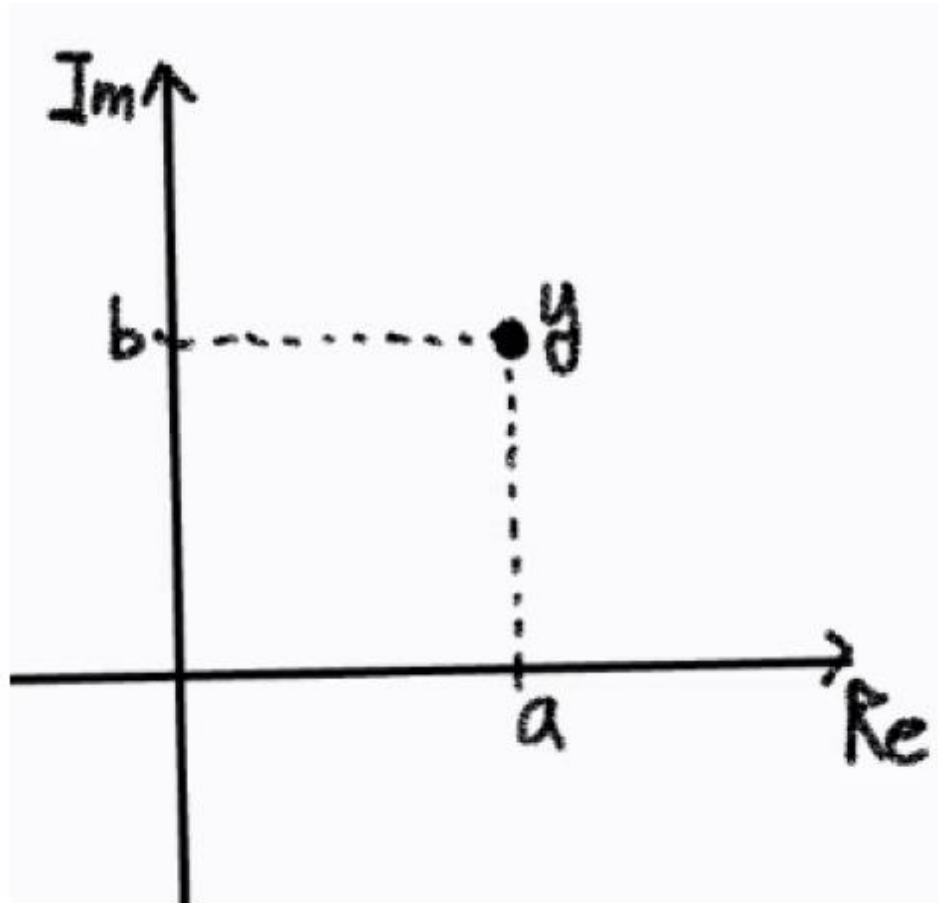

Polar (angular) coordinate

- $y = a + jb$

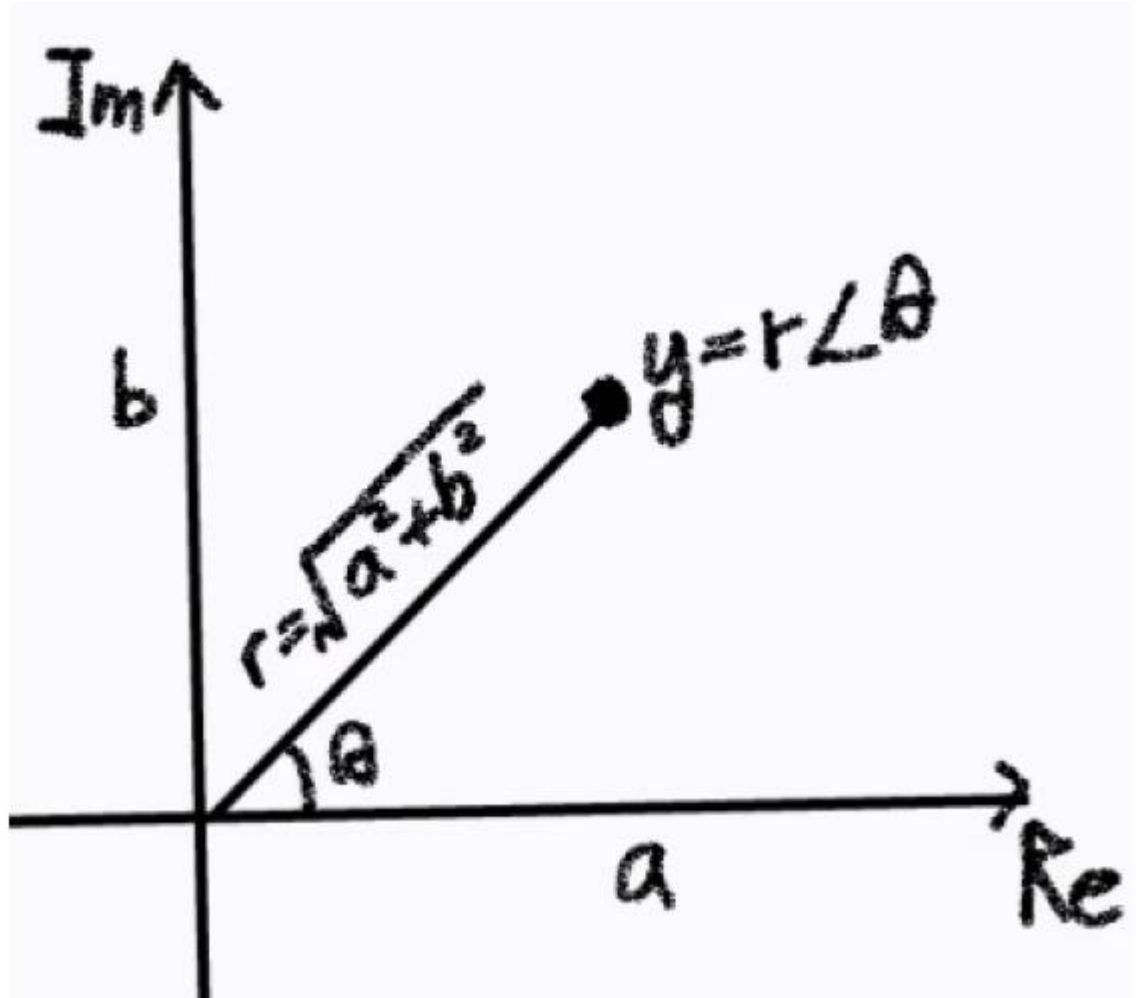

A phasor

- A complex number, representing a sinusoidal function, whose
 - Amplitude M
 - Angular frequency ω
 - Initial phase θ
- Example
 - A sinusoidal function $x(t)$
$$x(t) = M \cos(\omega t + \theta), \quad -\infty < t < \infty$$
 - A phasor form of $x(t)$, namely \bar{X}
$$\bar{X} = M e^{j\theta} = M \cos \theta + jM \sin \theta$$

Let's investigate the situation from $x(t) \rightarrow \bar{X}$ or vice versa

$$\mathbf{x(t)} = \text{Re}\{\bar{X}e^{j\omega t}\} \text{ proof!!}$$

$$x(t) = M \cos(\omega t + \theta) \longleftrightarrow \bar{X} = Me^{j\theta} = M \cos \theta + jM \sin \theta$$

- $\text{Re}\{\bar{X}e^{j\omega t}\}$

$$= \text{Re}\{Me^{j\theta}e^{j\omega t}\}$$

$$= \text{Re}\{Me^{j(\theta+\omega t)}\}$$

$$= \text{Re}\{M \cos(\theta + \omega t) + jM \sin(\theta + \omega t)\}$$

$$= M \cos(\theta + \omega t)$$

$$= \mathbf{x(t)} = \text{Re}\{\bar{X}e^{j\omega t}\}$$
- The sinusoidal signal **$\mathbf{x(t)}$ is the real part of phasor** taking back its original angular frequency
- When we **represent a sinusoidal signal in phasor form,** the complex exponential **$e^{j\omega t}$ factors out!!!**

- Apply this to the sum of two sinusoidal **at the same frequency**

$$\begin{aligned} & A \cos(\omega t + \theta) + B \cos(\omega t + \varphi) \\ &= \operatorname{Re}\{Ae^{j(\omega t + \theta)}\} + \operatorname{Re}\{Be^{j(\omega t + \varphi)}\} \\ &= \operatorname{Re}\{Ae^{j(\omega t + \theta)} + Be^{j(\omega t + \varphi)}\} \\ &= \operatorname{Re}\{e^{j\omega t}(Ae^{\theta} + Be^{\varphi})\} \end{aligned}$$


- Why do we learn this?
 - Do you remember V and I for L and C cases?


Recall

- Capacitive reactance $X_c: 1/(\omega C)$
 - between V and I , **ωt : no change** only -90 phase diff.
- Inductive reactance $X_L: \omega L$
 - between V and I , **ωt : no change** only $+90$ phase diff.

The phasor looks like a very
useful tool for circuit
analysis!!

Graphically, (reusing gif.)

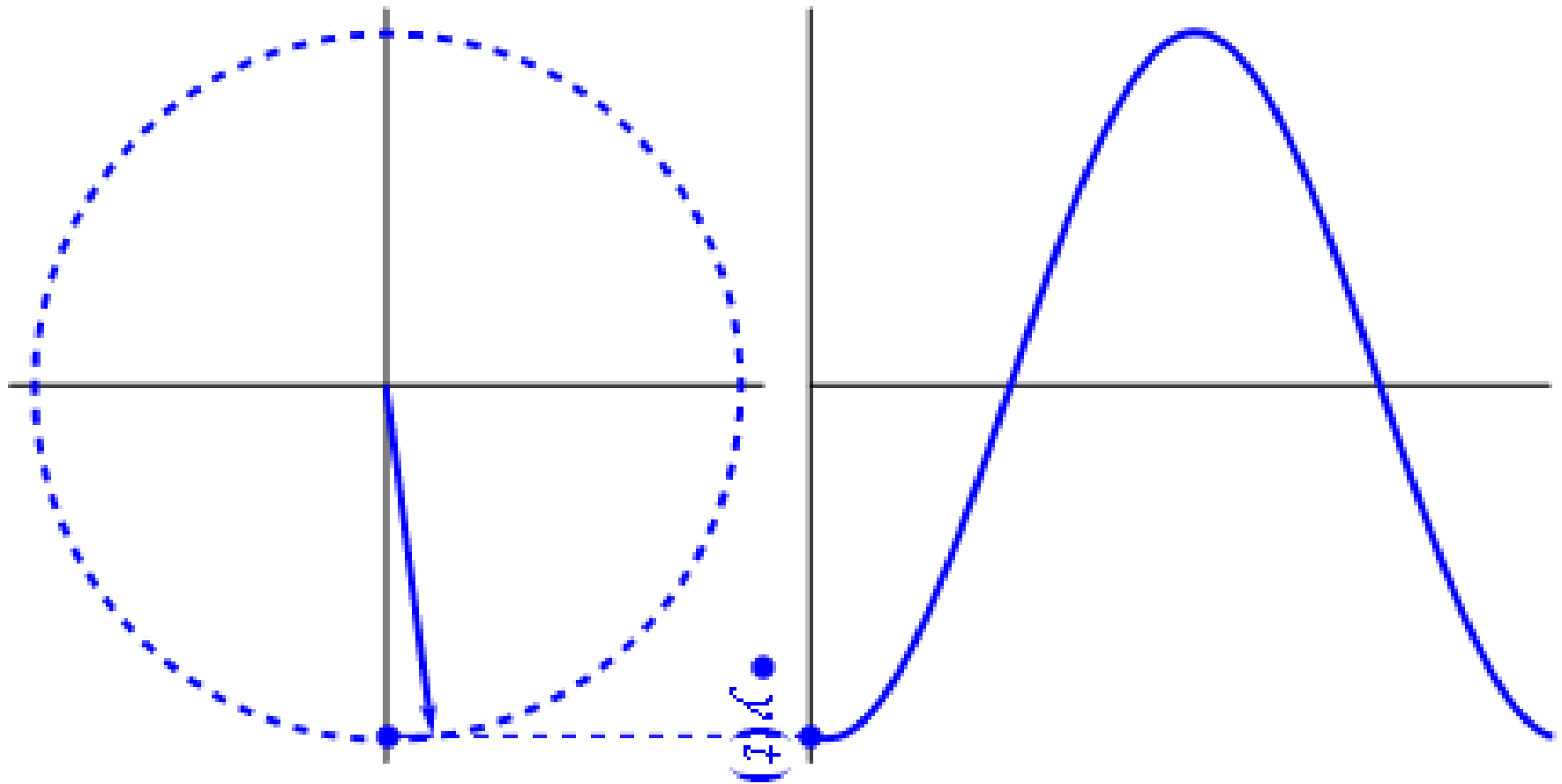

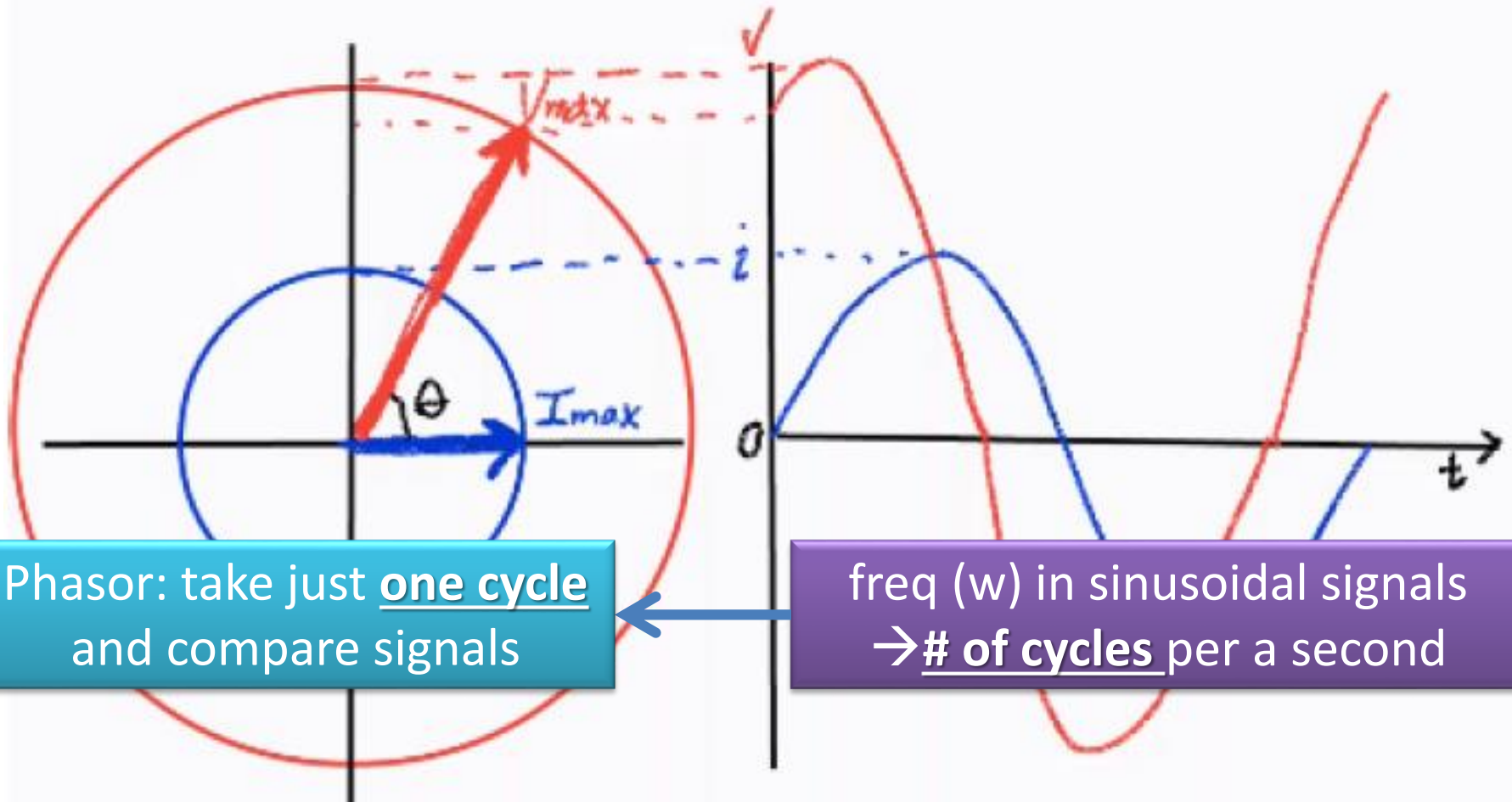

Phasor: take just one cycle and compare signals

freq (ω) in sinusoidal signals
 \rightarrow # of cycles per a second



Phasor graph, at $t=0$


Sinusoidal graph

$t=0$

A phasor is meant to represent the magnitude and phase between V and I

$t=\pi/2$

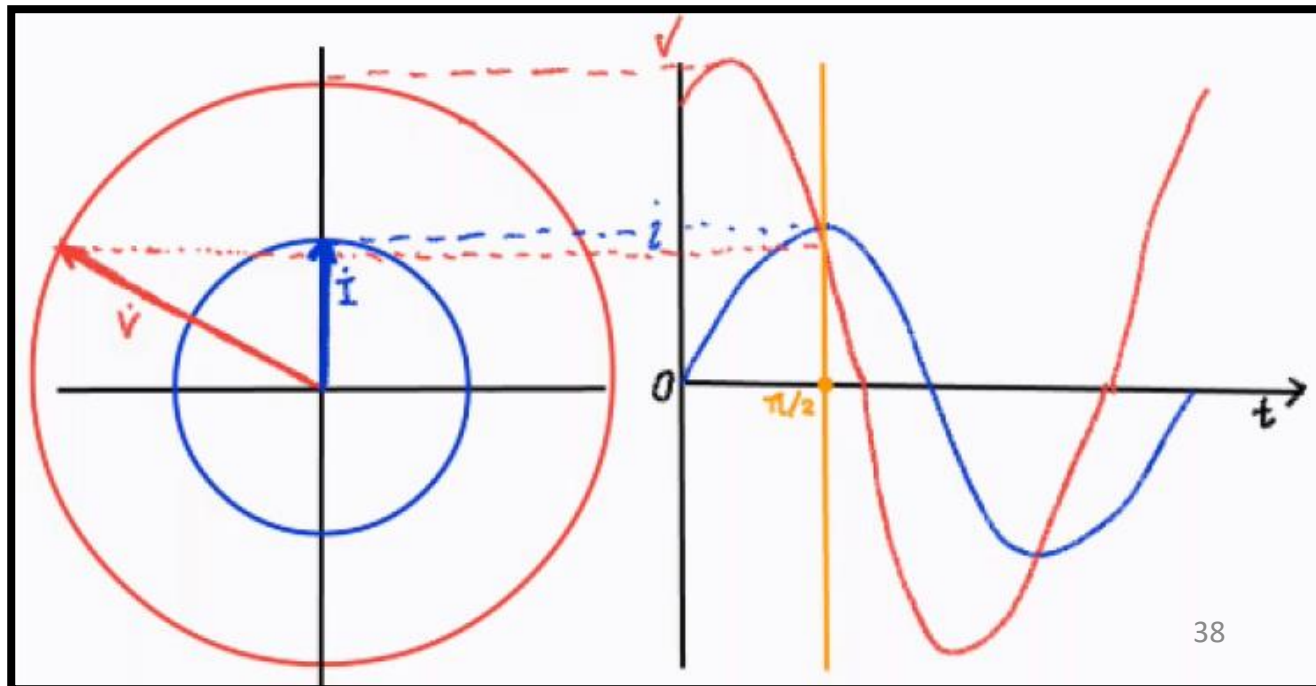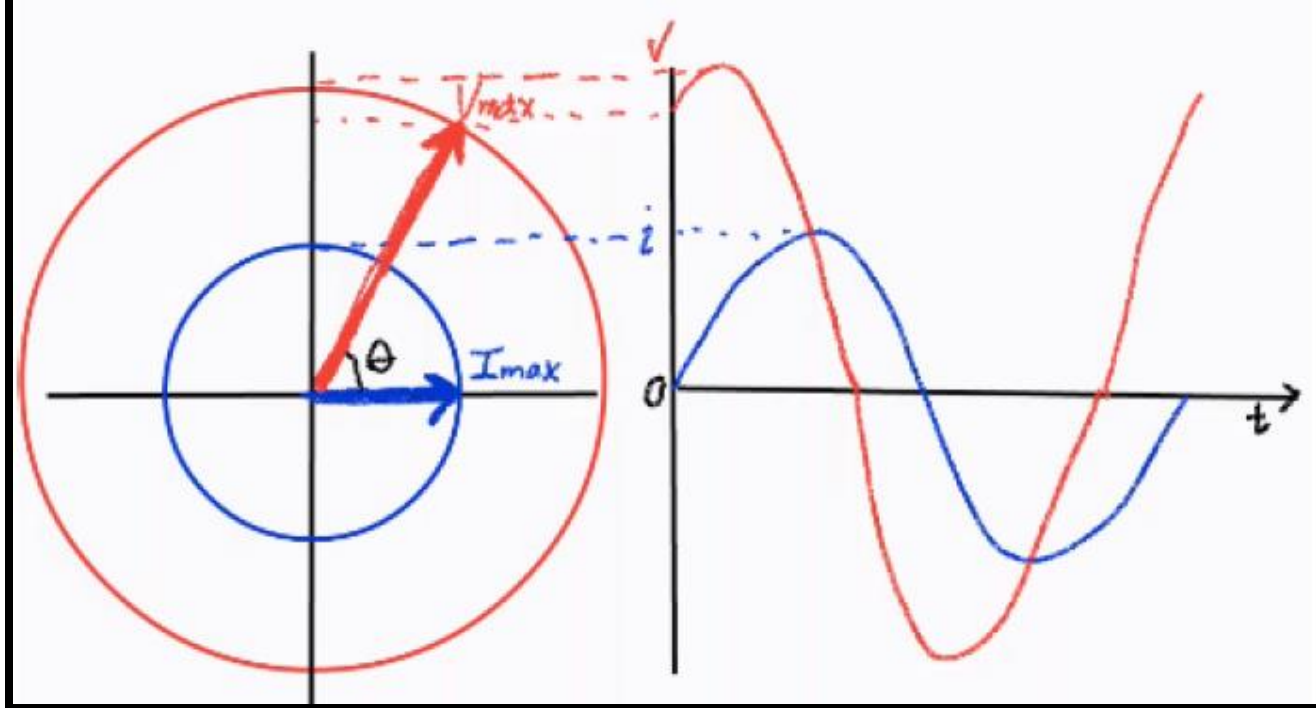

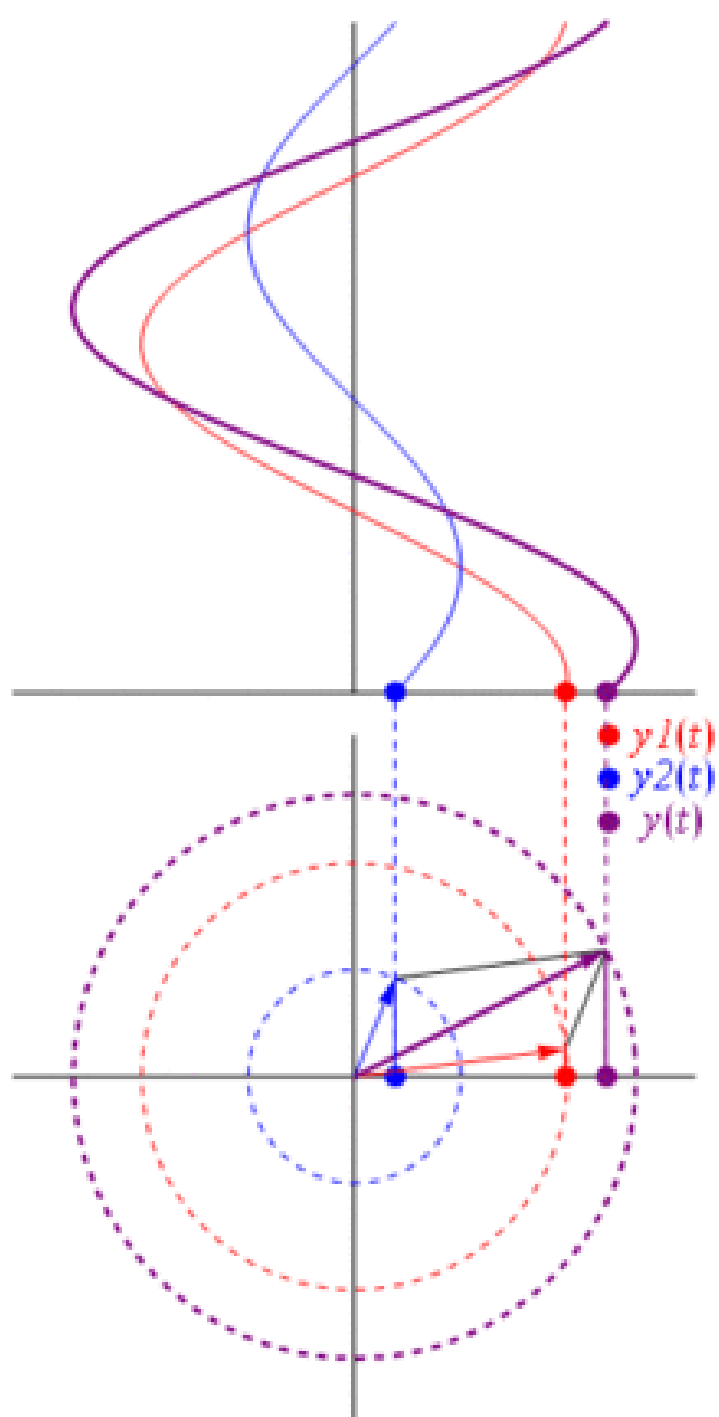


Phasor Ratio of y_1 and y_2 or y_3 will be the same regardless of $t \rightarrow$ impedance

Summary of Phasor

Phasor Definition

Time function : $v_1(t) = V_1 \cos(\omega t + \theta_1)$

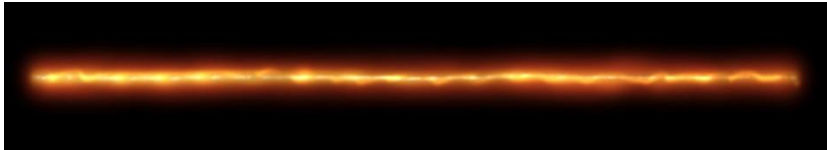Phasor : $\mathbf{V}_1 = V_1 \angle \theta_1 = V_1 e^{j\theta_1}$



Phasor



Euler's Formula

$$e^{j\theta} = \cos(\theta) + j \sin(\theta)$$

$$e^{-j\theta} = \cos(\theta) - j \sin(\theta)$$

$$\cos(\theta) = \operatorname{Re}(e^{j\theta})$$

$$\sin(\theta) = \operatorname{Im}(e^{j\theta})$$

$$|e^{j\theta}| = \sqrt{\cos^2(\theta) + \sin^2(\theta)} = 1$$

$$e^{j\theta} = 1 \angle \theta$$

$$e^{j\theta} = \cos(\theta) + j \sin(\theta)$$

$$e^{j\pi} = \cos(\pi) + j \sin(\pi) = -1$$

$$e = 2.718281828459045235360287\dots = \lim_{n \rightarrow \infty} \left(1 + \frac{1}{n} \right)^n$$

$$\pi = 3.141592653589793238462643\dots$$

$$j = \sqrt{-1}$$

$$e^{j\pi} = -1$$

$$\begin{aligned} \sin \omega t &= \cos \omega t - 90^\circ \\ \cos \omega t &= \sin \omega t + 90^\circ = -\sin \omega t - 90^\circ \end{aligned}$$

$$\sin \omega t = \cos(\omega t - 90^\circ)$$