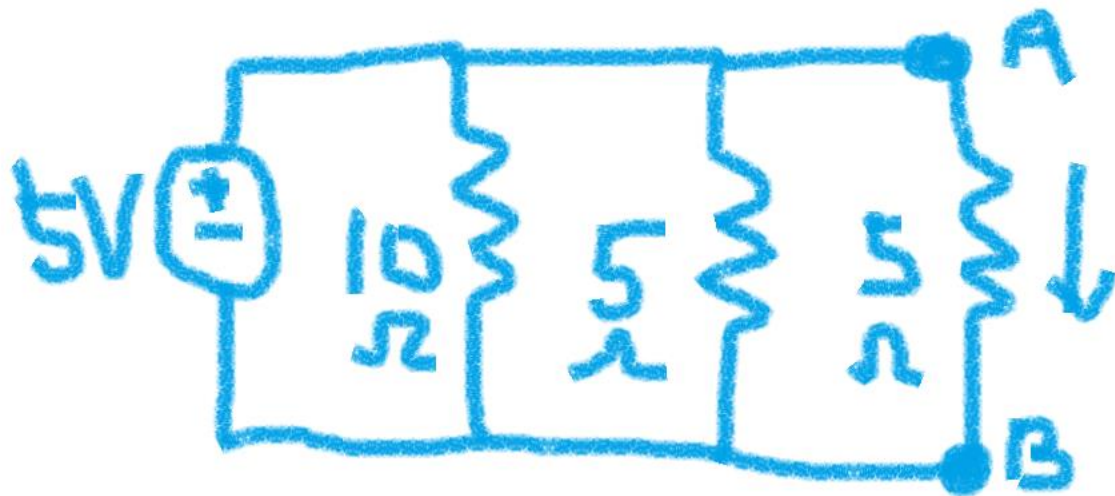



CET 141: Day 2

Dr. Noori KIM

Warm up ourselves




$V_{AB}?$
 $I_{AB}?$

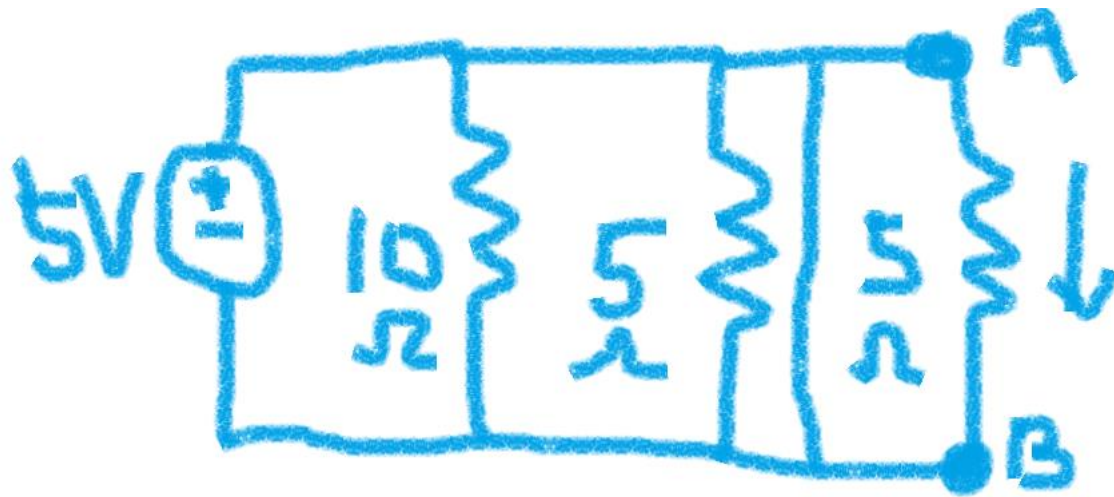


$V_{AB}?$
 $I_{AB}?$

- Find the value of v_o

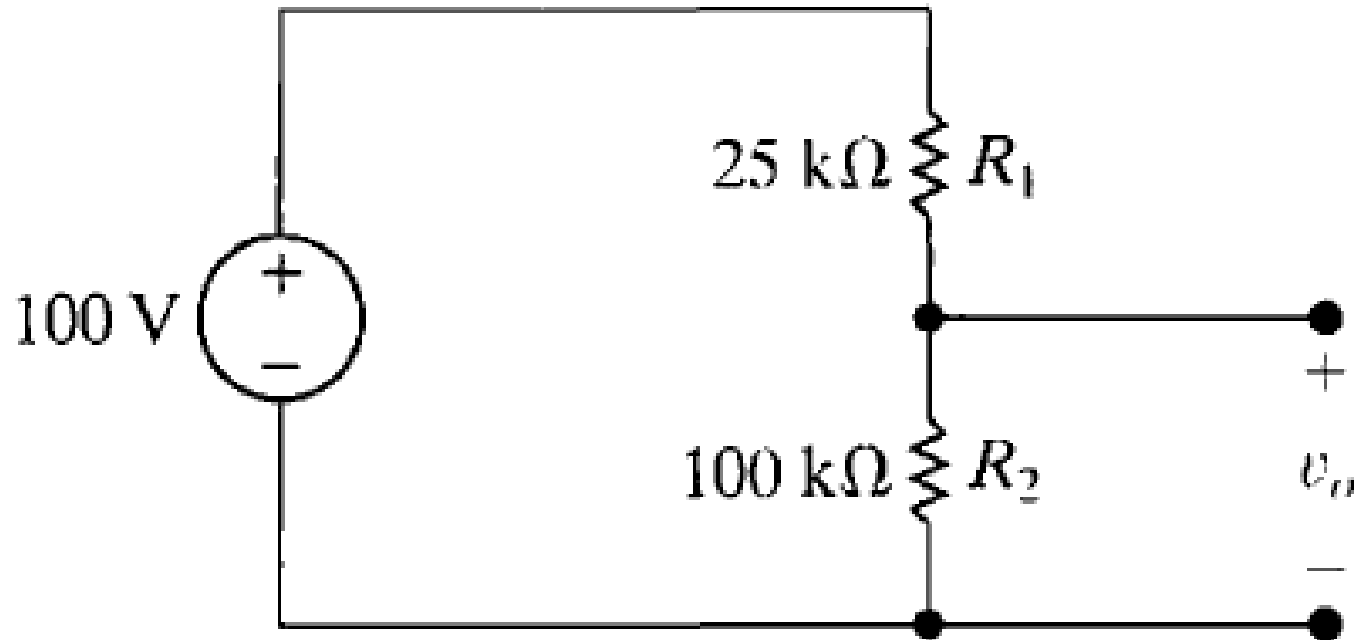

$$v_o = 100V \frac{100k}{100k + 25k} = 80V$$

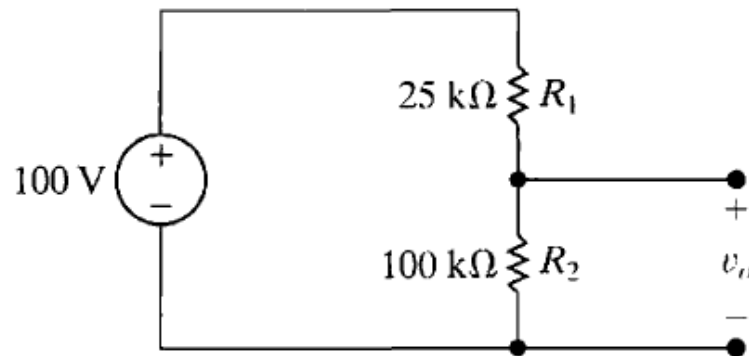- The resistors used in the voltage-divider circuits have a tolerance of $\pm 10\%$. Find the maximum and minimum value of v_o







- The maximum value of v_o occurs when R_2 is 10% high and R_1 is 10% low
- The minimum value of v_o occurs when R_2 is 10% low and R_1 is 10% high

$$v_o(\text{max}) = \frac{(100)(110)}{110 + 22.5} = 83.02 \text{ V.} \quad v_o(\text{min}) = \frac{(100)(90)}{90 + 27.5} = 76.60 \text{ V}$$


Thus, in making the decision to use 10% resistors in this voltage divider, we recognize that the no-load output voltage will lie between 76.60 and 83.02 V.


Electrical Sources

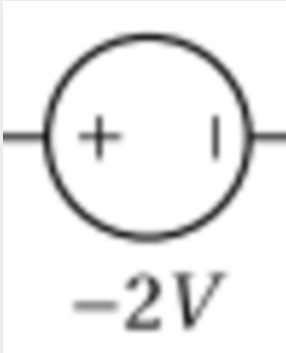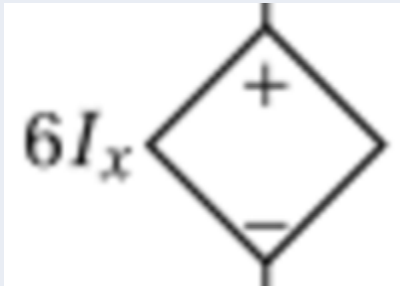	Independent (Circle)	Dependent (Diamond)
Current (Arrow)		
Voltage (Polarity)		

Dependent sources

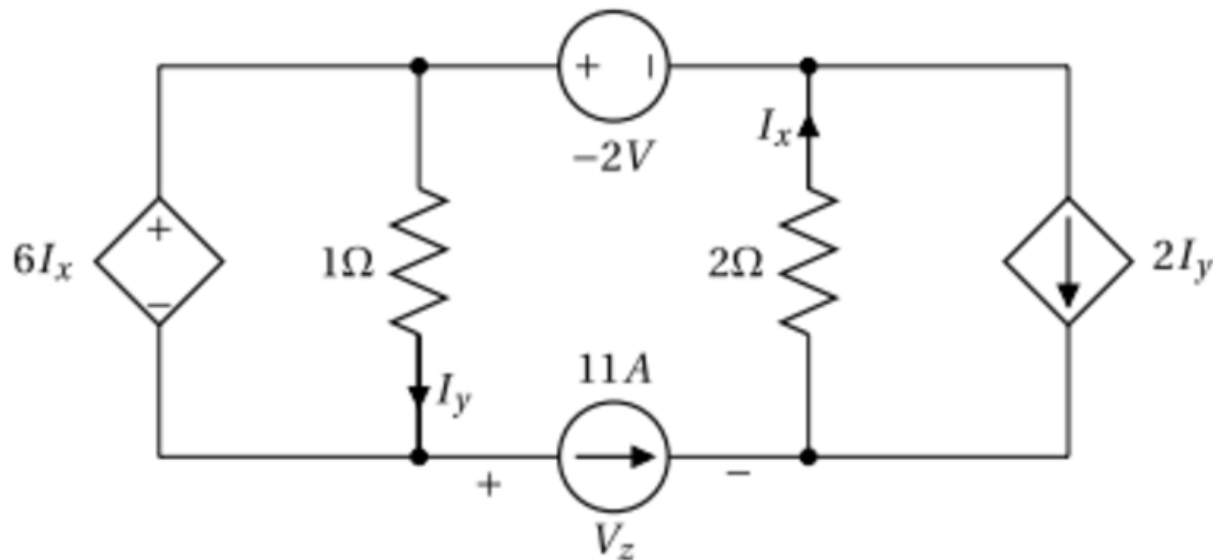- **A dependent source**
 - a voltage **source** or a current **source**
 - whose value depends on a voltage or current somewhere else in the network.



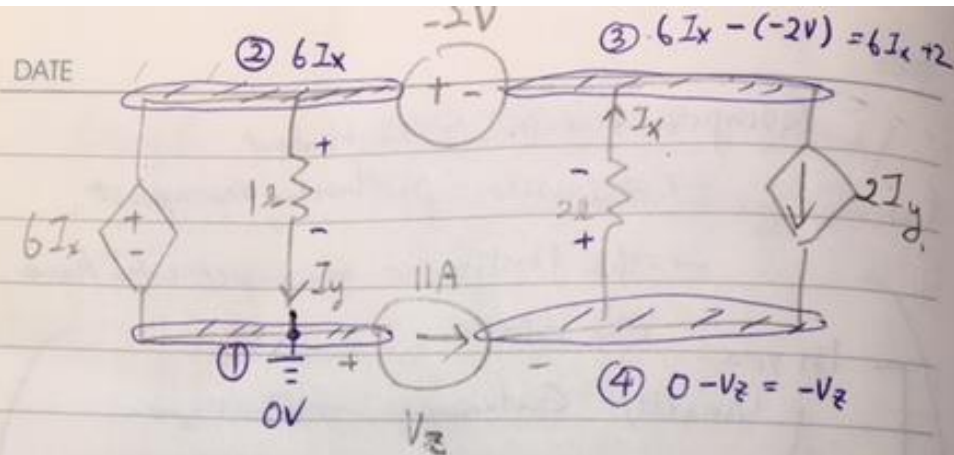

I_x, I_y, V_z ?


From (3), (4)

$$(5) \quad I_x = \frac{-V_z - (6I_x + 2)}{2}$$

$$2I_x = -V_z - 6I_x - 2$$

$$8I_x + V_z = -2$$

(6) at (4)

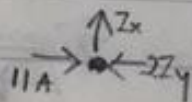

$$I_x = 11 + 2I_y$$

(7) at (2)

$$I_y = \frac{6I_x - 0}{12} = 6I_x$$

From (5), (6), (7)

$$I_x = 11 + 2(6I_x)$$

$$\Rightarrow I_x = -1A$$

$$-1 = 11 + 2I_y - 12 \cdot 2I_y$$

$$I_y = -6A$$


$$8 \cdot (-1) + V_z = -2$$

$$\Rightarrow V_z = 6V$$

Wheatstone bridge


- A device which is used to measure the electrical resistance by comparison method
- To measure an unknown resistance by passing current through the unknown resistor
- Brief History:
 - First founded by Samuel Hunter Christie in 1833
 - Sir Charles **Wheatstone** claimed the various applications of the device and showed its importance to the people (the device name after him)

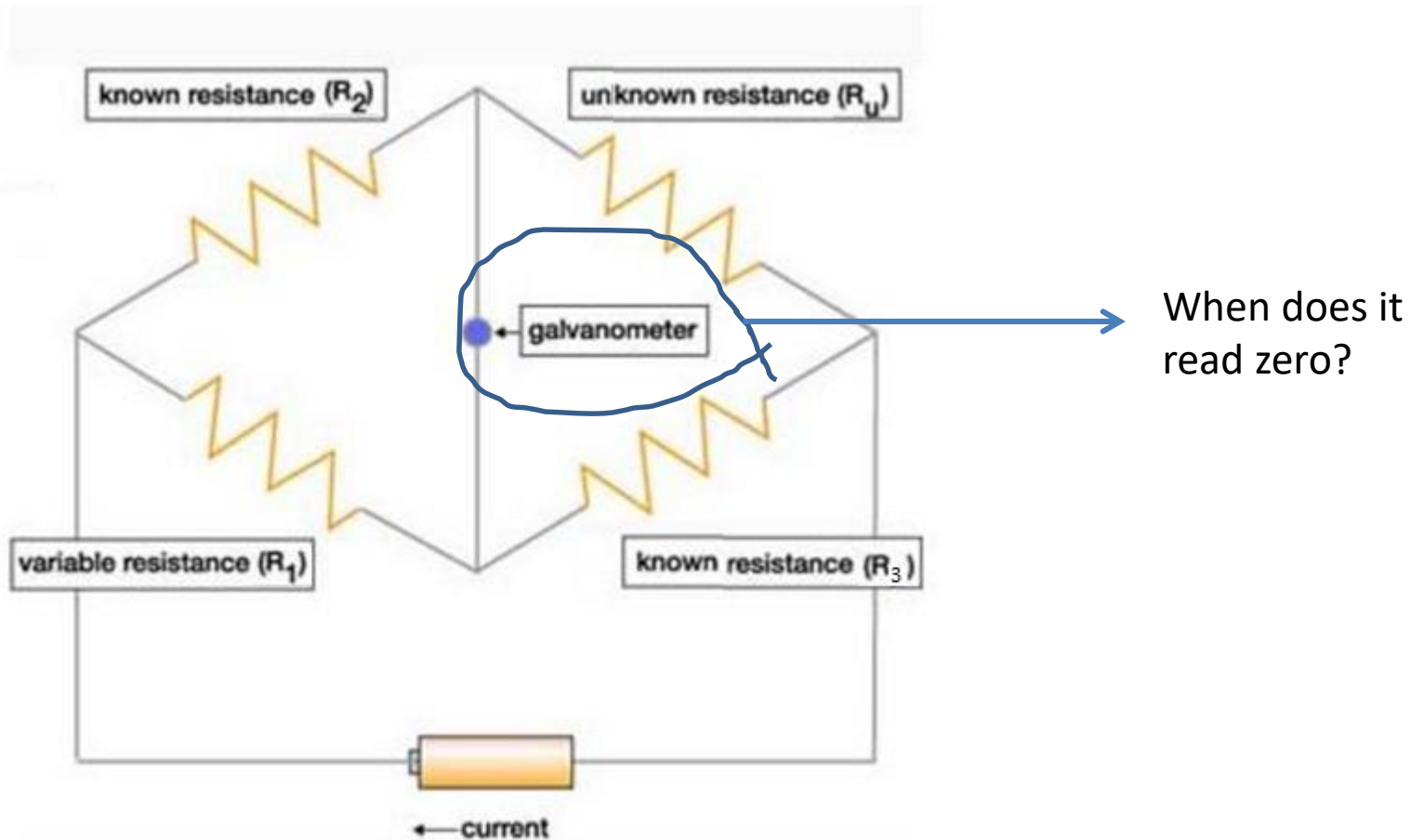- R_1 , R_2 , R_3 and R_u
- R_u is the resistor whose resistance is to be found and R_1 is the only adjustable resistor (in this setting)




=



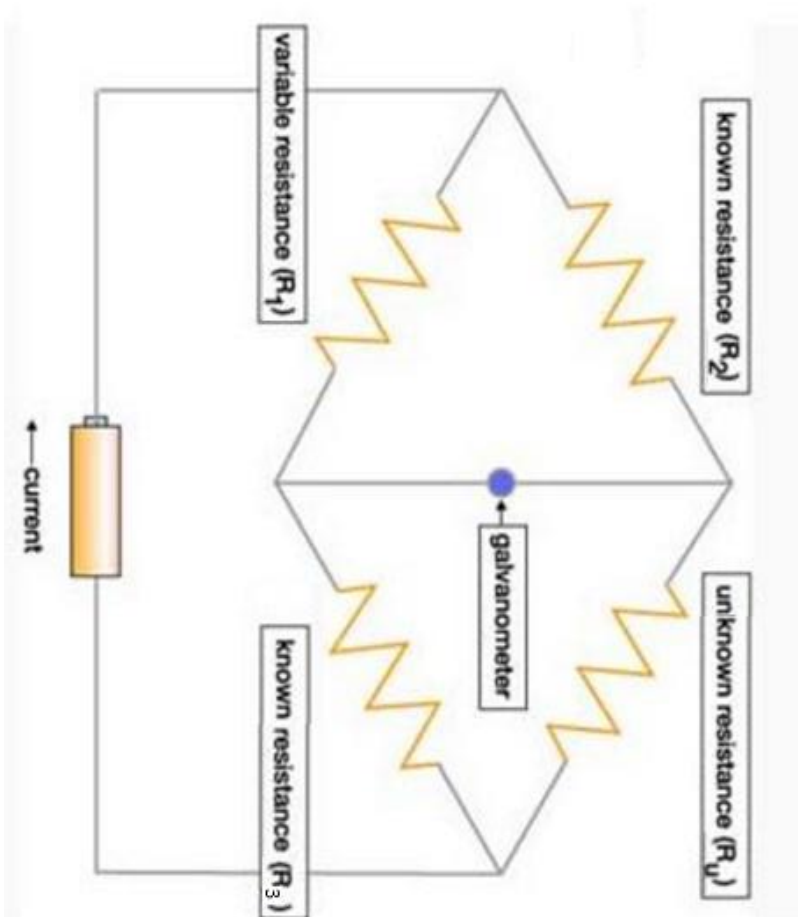

- Known path: R_2, R_3 = Unknown path: R_u, R_1
 - The reading current at the galvanometer = 0
 - Varying R_1 to find R_u : **$R_u = (R_3 * R_2) / R_1$**
 - **Or varying one of variable resistors among R_1, R_2 , or R_3**

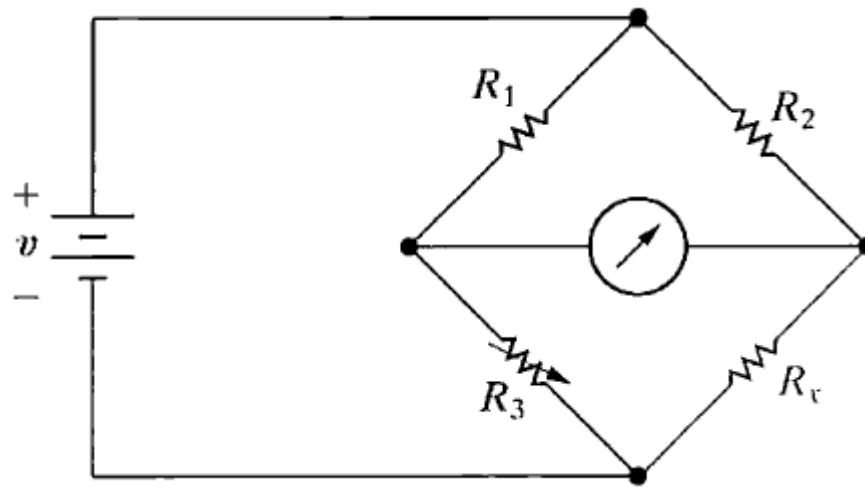- The bridge circuit shown is balanced when $R_1 = 100\Omega$, $R_2 = 1000\Omega$, and $R_3 = 150\Omega$. The bridge is energized from a 5 V dc source. What is the value of R_x ?




$$100R_x = (1000)(150) \quad \text{so} \quad R_x = \frac{(1000)(150)}{100} = 1500\Omega = 1.5\text{ k}\Omega$$


- Suppose each bridge resistor is capable of dissipating 250 mW. Can the bridge be left in the balanced state without exceeding the power-dissipating capacity of the resistors (without damaging the bridge)?

Hint>>

➤ Calculate dissipating power for each resistor and compare it to 250mW

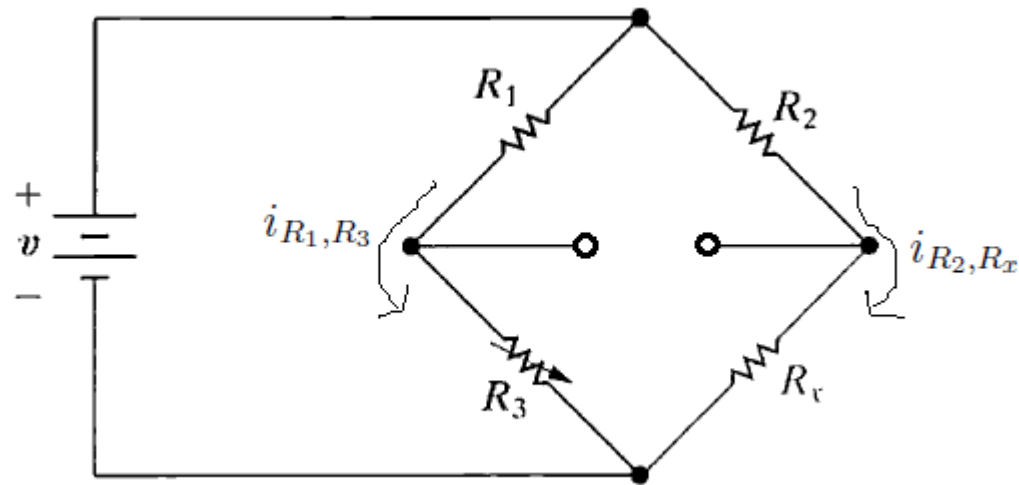➤ When the bridge is balanced, there is no current flowing through the meter, so the meter acts like an open circuit.



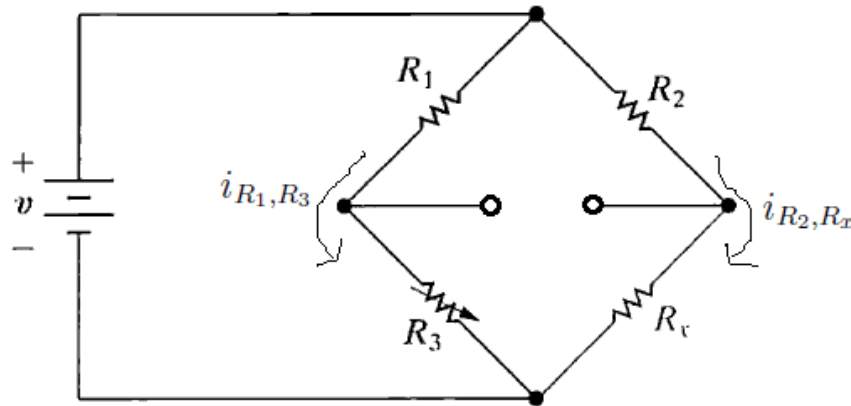

$$i_{R_1, R_3} = \frac{5 \text{ V}}{100 \Omega + 150 \Omega} = 20 \text{ mA} \quad i_{R_2, R_4} = \frac{5 \text{ V}}{1000 + 1500} = 2 \text{ mA}$$

$$p = Ri^2:$$

$$p_{100\Omega} =$$

$$p_{150\Omega} =$$

$$p_{1000\Omega} =$$


$$p_{1500\Omega} =$$

} << 250 mW

The bridge can be left in the balanced state without exceeding the power-dissipating capacity of the resistors

Delta-to-Wye Equivalent Circuits

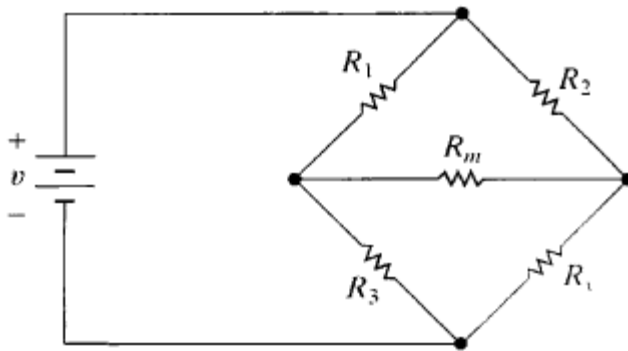
- From the Wheatstone bridge, we **replace the galvanometer** with its equivalent resistance R_m ,



delta (Δ) interconnection

or

Pi (π) interconnection

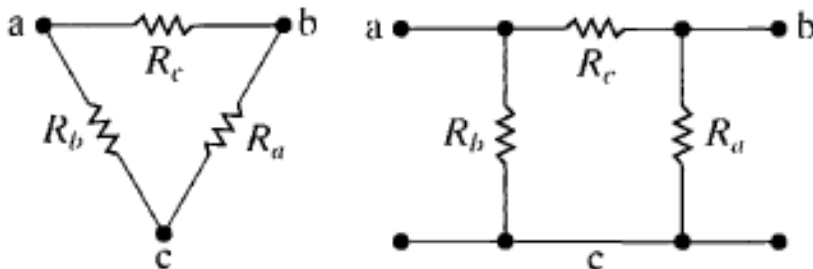

as the Δ can be shaped into a π without disturbing the electrical equivalence of each node

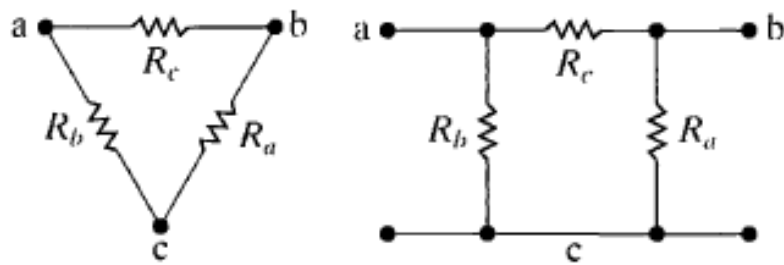


Figure 3.29 ▲ A Δ configuration viewed as a π configuration.

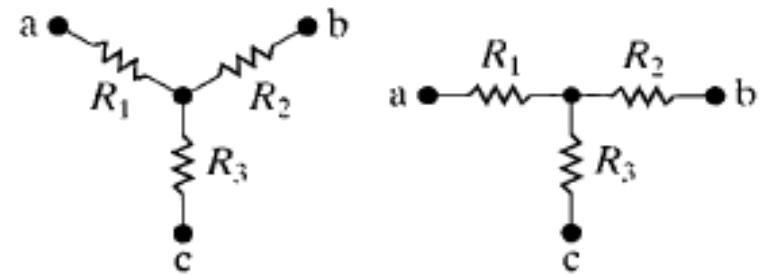


Figure 3.30 ▲ A Y structure viewed as a T structure.

Transformations without disturbing the electrical equivalence

Then, how about this?



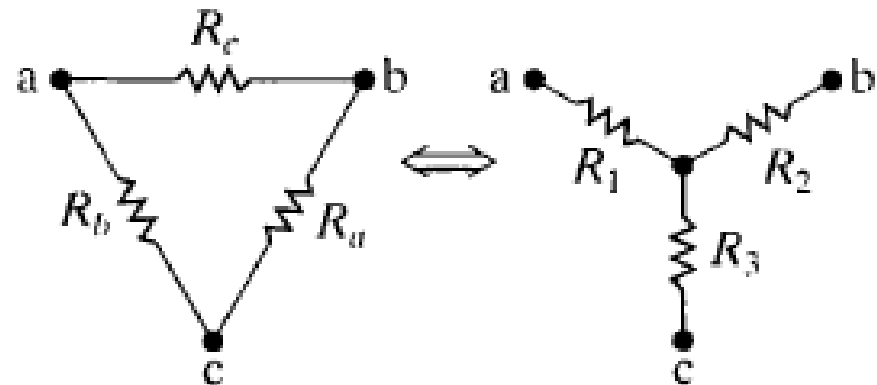


Figure 3.31 ▲ The Δ -to-Y transformation.

Basic idea of the transformation

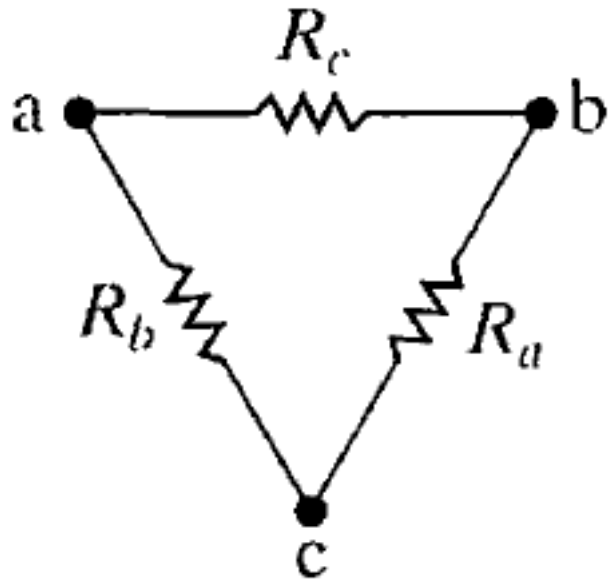

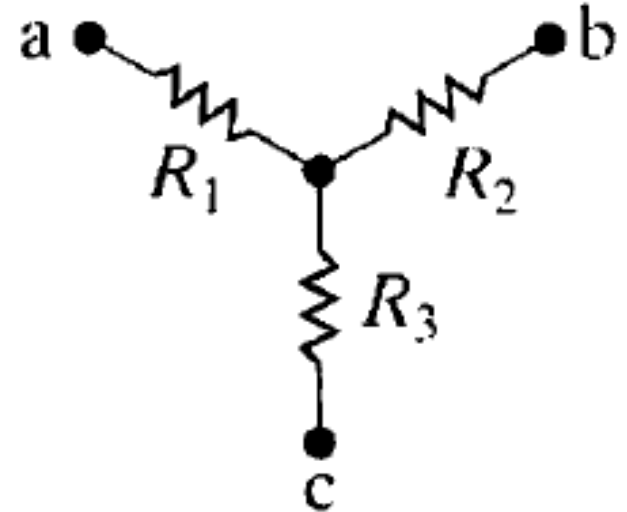Two parallel resistors viewed as two series resistors





$$R_{ab} = \frac{R_c(R_a + R_b)}{R_a + R_b + R_c} = R_1 + R_2$$

$$R_{bc} = \frac{R_a(R_b + R_c)}{R_a + R_b + R_c} = R_2 + R_3$$

$$R_{ca} = \frac{R_b(R_c + R_a)}{R_a + R_b + R_c} = R_1 + R_3$$

Preserve node a, b, c voltages

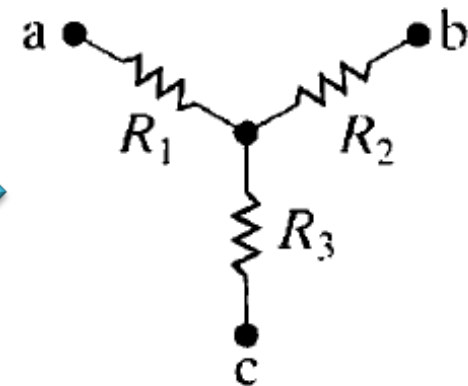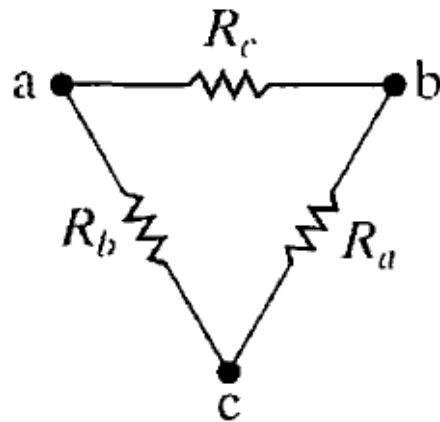Solve for R_1 , R_2 , and R_3 in terms of R_a , R_b , and R_c



$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1},$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2},$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}.$$







$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c},$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c},$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}.$$

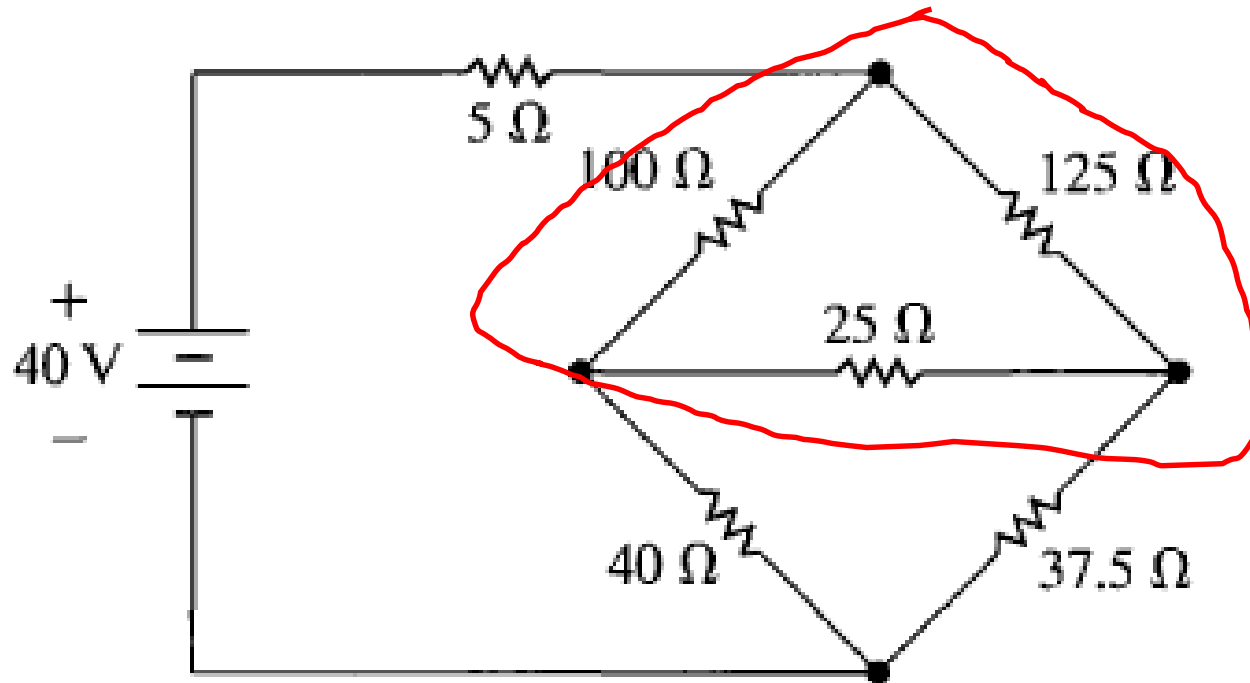- Find the current and power supplied by the 40V source





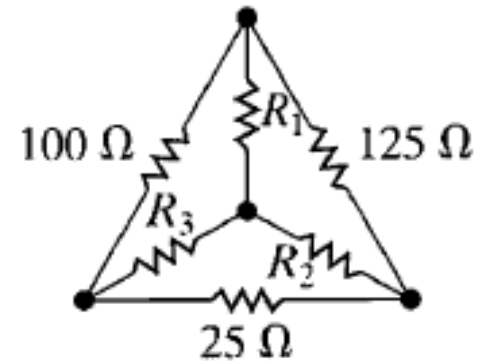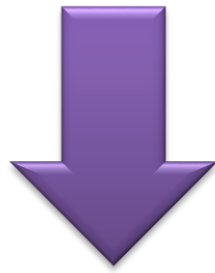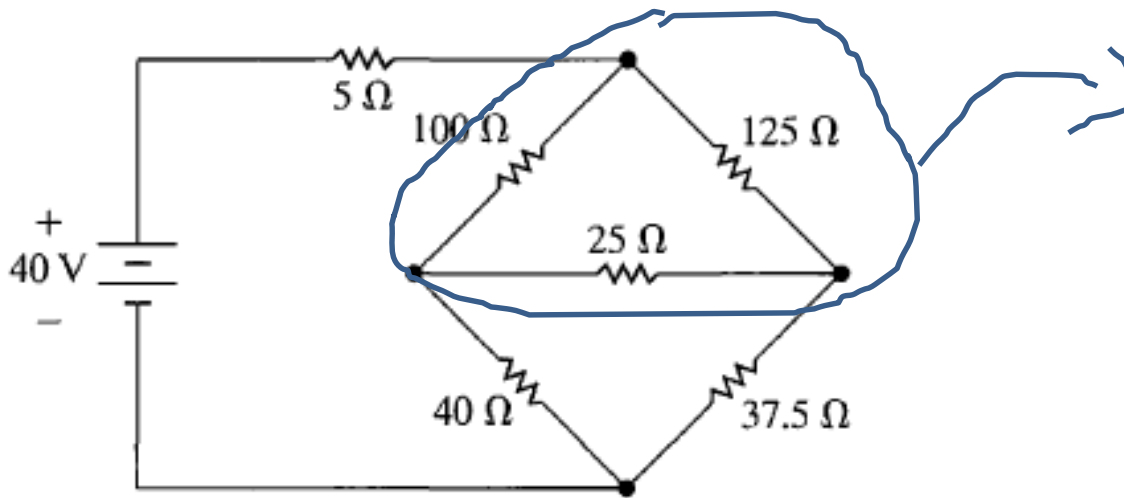

$$R_1 = \frac{100 \times 125}{250} = 50 \, \Omega,$$


$$R_2 = \frac{125 \times 25}{250} = 12.5 \, \Omega,$$
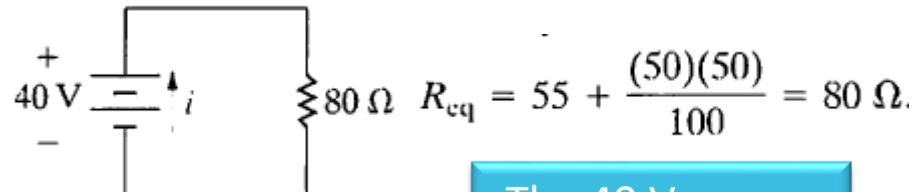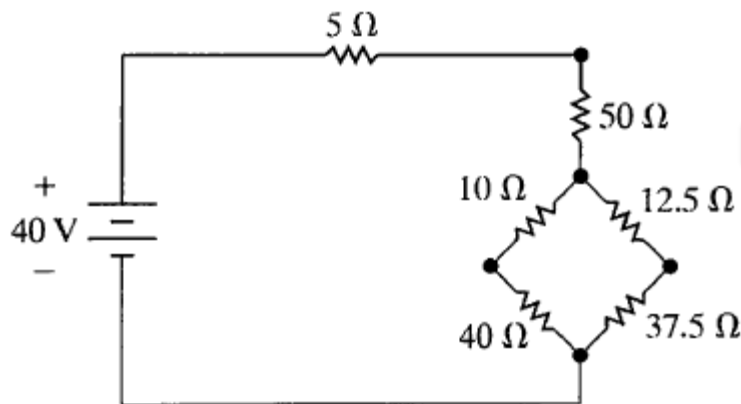
$$R_3 = \frac{100 \times 25}{250} = 10 \, \Omega.$$




The 40 V source delivers 0.5 A and 20 W to the circuit.

Source transformation

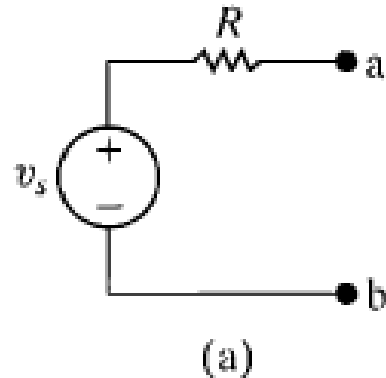

$$V_{ab} = V_s * R_L / (R + R_L)$$


Where $i_s = v_s / R$ \Updownarrow

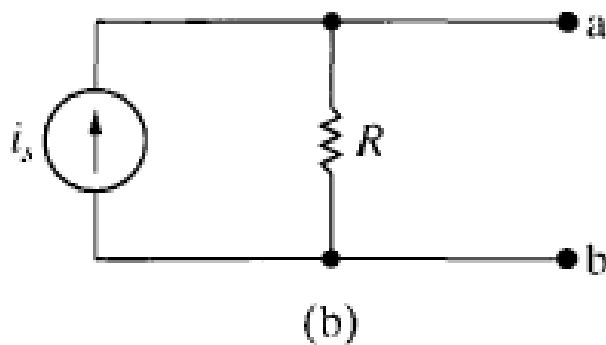

$$V_{ab} = I_s * (R_L * R) / (R + R_L)$$


Figure 4.36 ▲ Source transformations.

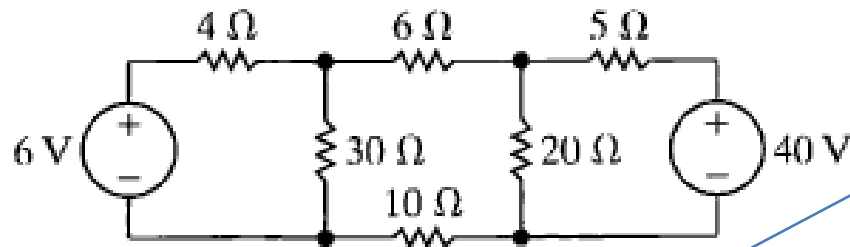- Find the power associated with the 6 V source.




$$20 \parallel 5 = \frac{20 \cdot 5}{20 + 5} = 4 \text{ ohm}$$

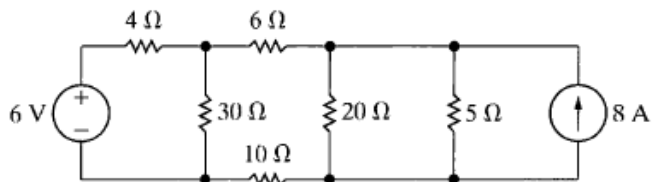
$$4 \text{ ohm} \cdot 8 \text{ A} = 32 \text{ V (S.Trans)}$$




(a) First step

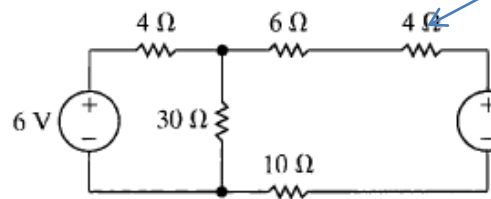

(b) Second step

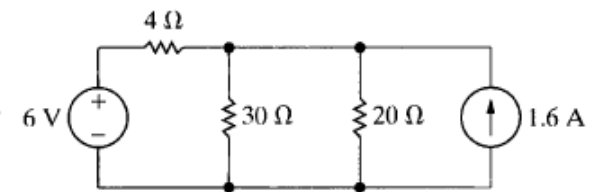


(c) Third step

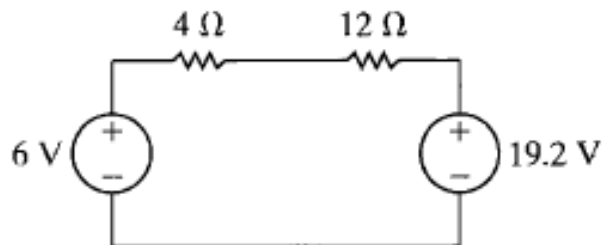

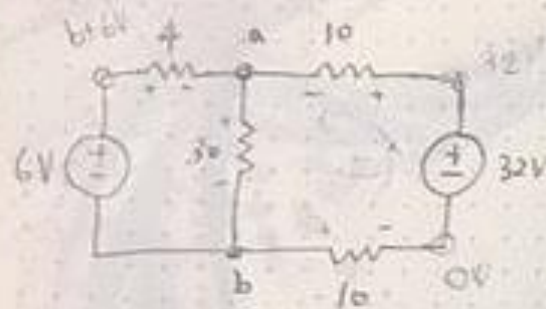
(d) Fourth step

The current in the direction of the voltage drop across the 6 V source is $(19.2 - 6)/16$, or 0.825 A

$$p_{6V} = (0.825)(6) = 4.95 \text{ W.}$$



$$V_{ab} \stackrel{?}{=} V_{a'b'}$$

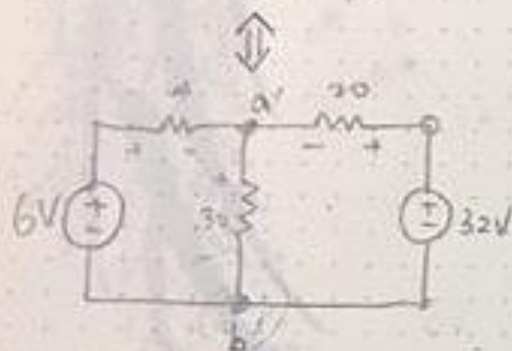

$$V_{ab} \Rightarrow \begin{matrix} \rightarrow a \leftarrow \\ \downarrow \end{matrix}$$

$$\frac{1652}{908} = \frac{144}{144}$$

$$\frac{6+b-a}{4} + \frac{32-a}{10} = \frac{a-b}{30}$$

$$\frac{b-0}{10} = \frac{32-a}{10} \quad \langle b=32-a \rangle$$

$$\frac{6+32-a-a}{4} + \frac{32-a}{10} = \frac{a-32+a}{30}$$

$$(32-2a)30 + (32-a)12 = 4(2a-32)$$

$$1140 - 60a + 384 - 12a = 8a - 128$$

$$80a = 1140 + 384 + 128$$

$$a = \frac{1652}{80} = \frac{413}{20}$$

$$V_{ab} = \frac{1652}{80} - \frac{908}{80} = \frac{744}{80} V$$

$$= \frac{186}{20} = \frac{93}{10}$$

$$V_{a'b'} = 0$$

$$\left(\frac{6-a'}{4} + \frac{32-a'}{20} = \frac{a'}{30} \right) \times 120$$

$$30(6-a') + 6(32-a') = 4a'$$

$$180 - 30a' + 192 - 6a' = 4a'$$

$$372 = 40a'$$

$$a' = \frac{372}{40} = \frac{93}{10}$$

$$V_{a'b'} = \frac{93}{10}$$