


# CET 141: Day 5

Dr. Noori KIM
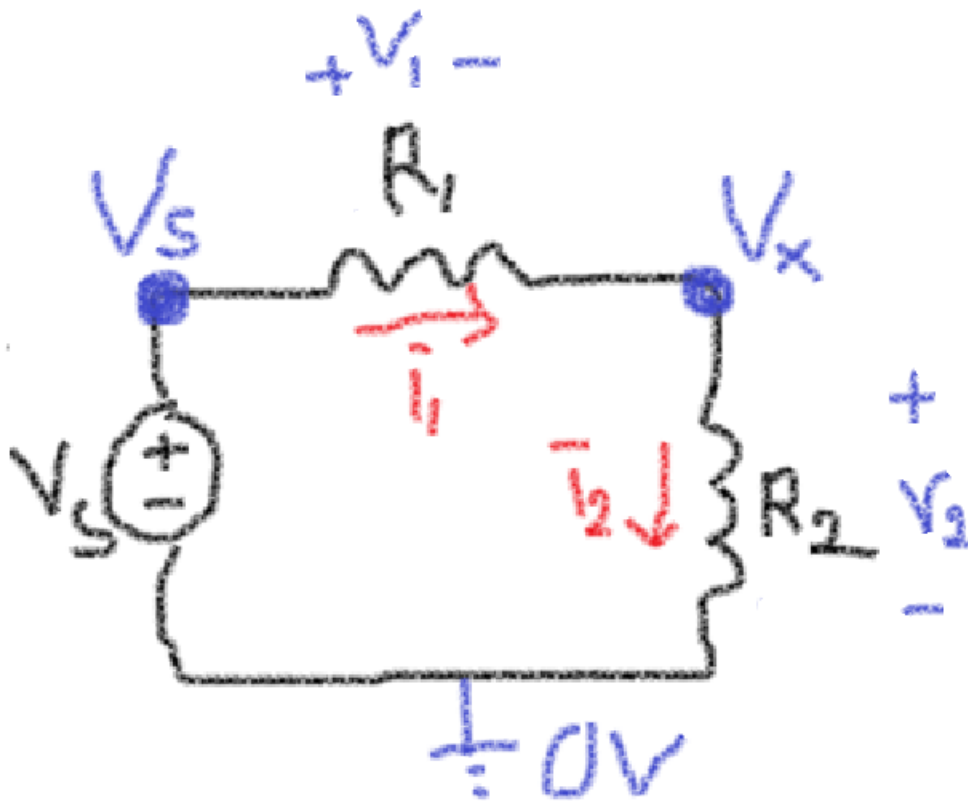
# AC vs. DC

- <https://www.youtube.com/watch?v=BcIDRet787k> (1min~)

What we did (and should  
have done) so far...



- Ohm's law
- KCL/KVL
- Nodal analysis

- Ohm's law:  
 $V_1 = R_1 \cdot i_1$ ,  $V_2 = R_2 \cdot i_2$
- KVL:  $V_s = V_1 + V_2$
- KCL:  $i_1 = i_2 (=i)$
- Nodal analysis:  
 $(V_s - V_x)/R_1 = (V_x - 0)/R_2$


Note that  $v_1 = V_s - V_x$

$$i = V_s / (R_1 + R_2) = i_1 = V_1 / R_1 = i_2 = V_2 / R_2$$

- Thevenin/Norton equivalents




Source transformation

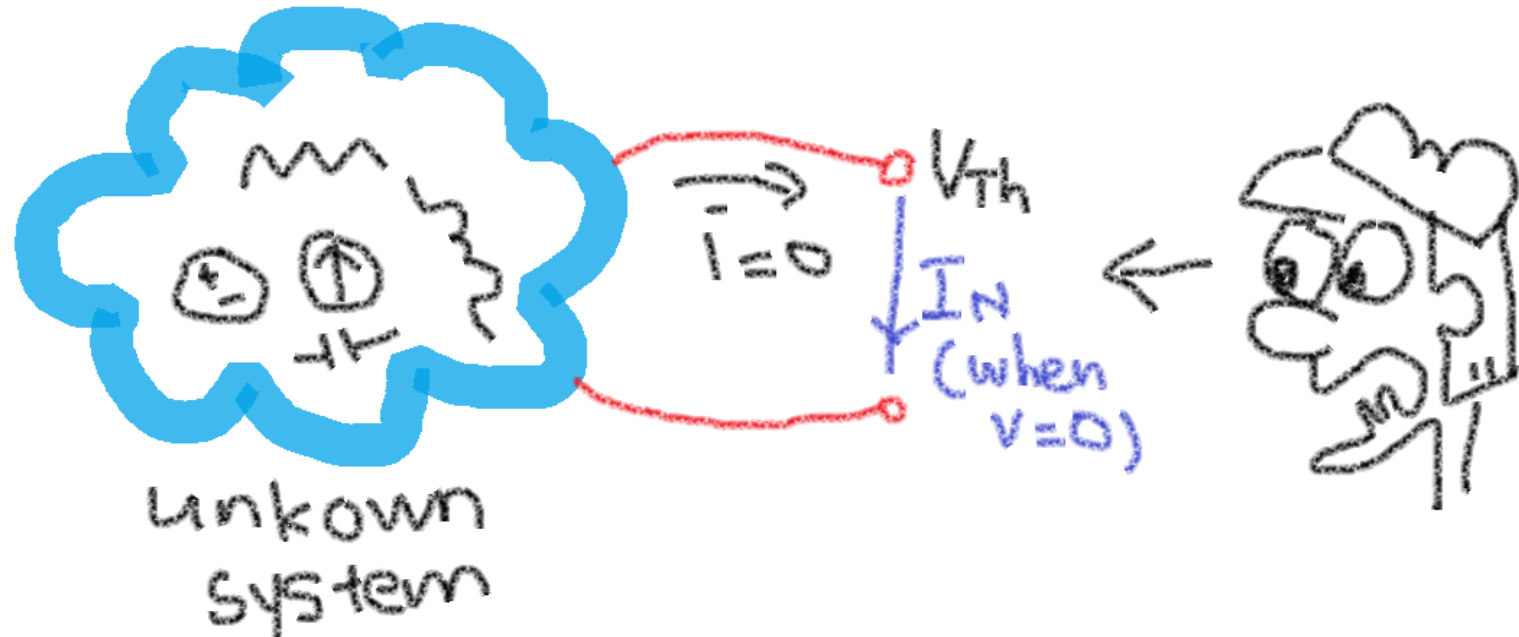

$R_{th}$

- Only independent sources:  $V$  short,  $I$  open
- With dependent sources: take a ratio ( $V_{th}/I_N$ )

- Op amp analysis

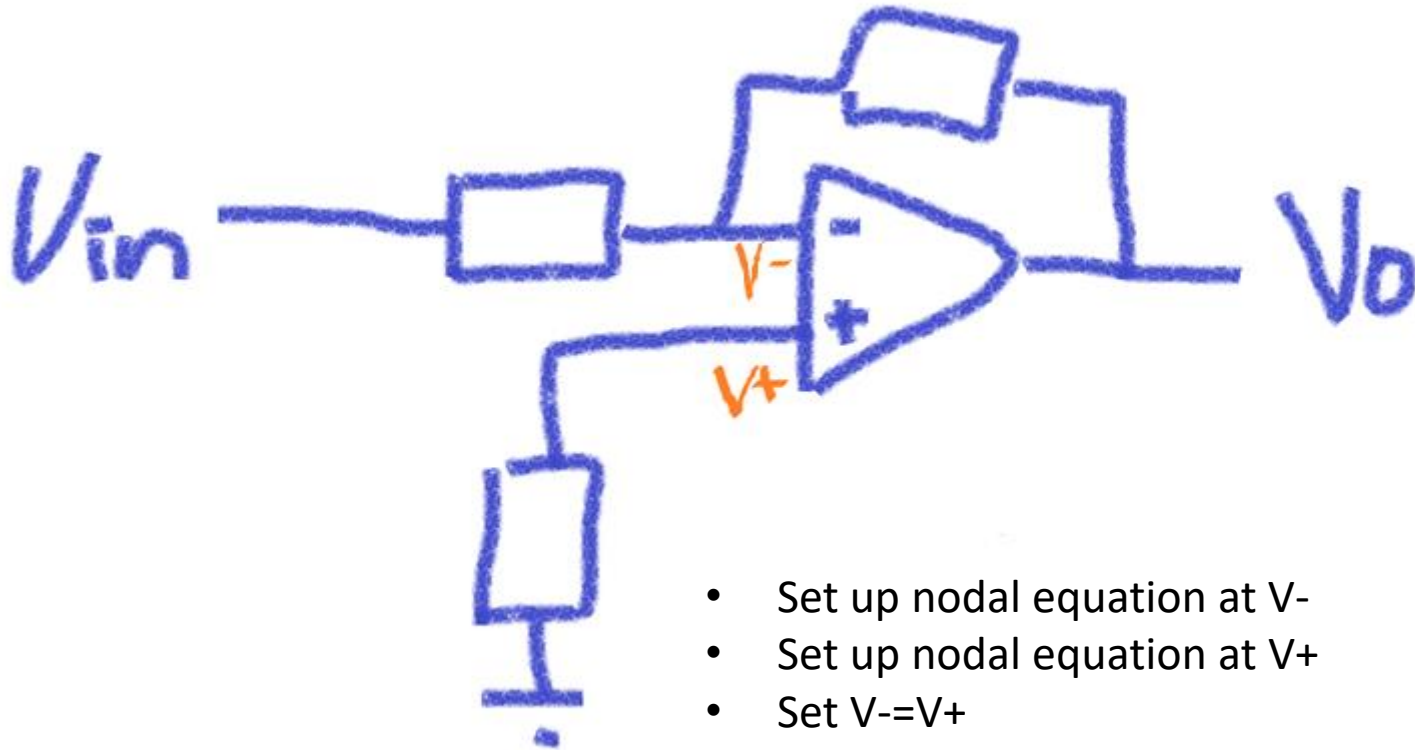

- Set up nodal equation at  $V_-$
- Set up nodal equation at  $V_+$
- Set  $V_- = V_+$

- We will learn Caps and Inds components


a flow of electric charge



$$\Phi_B = N \quad B \quad A$$

$$\Phi_B = N \frac{\mu_0 N I}{\ell} A$$

$$\Phi_B = \frac{\mu_0 A N^2}{\ell} I$$

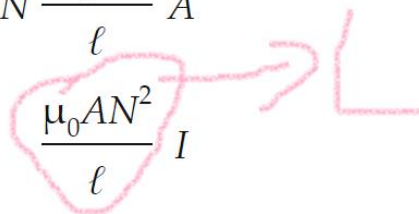

# Inductance and Capacitance

Dr. Noori Kim




# Chap. 6, Capacitors and Inductors

- Introduction
- Capacitors
- Series and Parallel Capacitors
- Inductors
- Series and Parallel Inductors


# Introduction

- Resistor: a passive element which dissipates energy only
- Two other important **passive** linear circuit elements:
  - 1) Capacitor
  - 2) Inductor
- Ideal capacitors and inductors can **store energy** only and they can **neither generate nor dissipate energy**. They are not active.

# Michael Faraday (1791-1867)

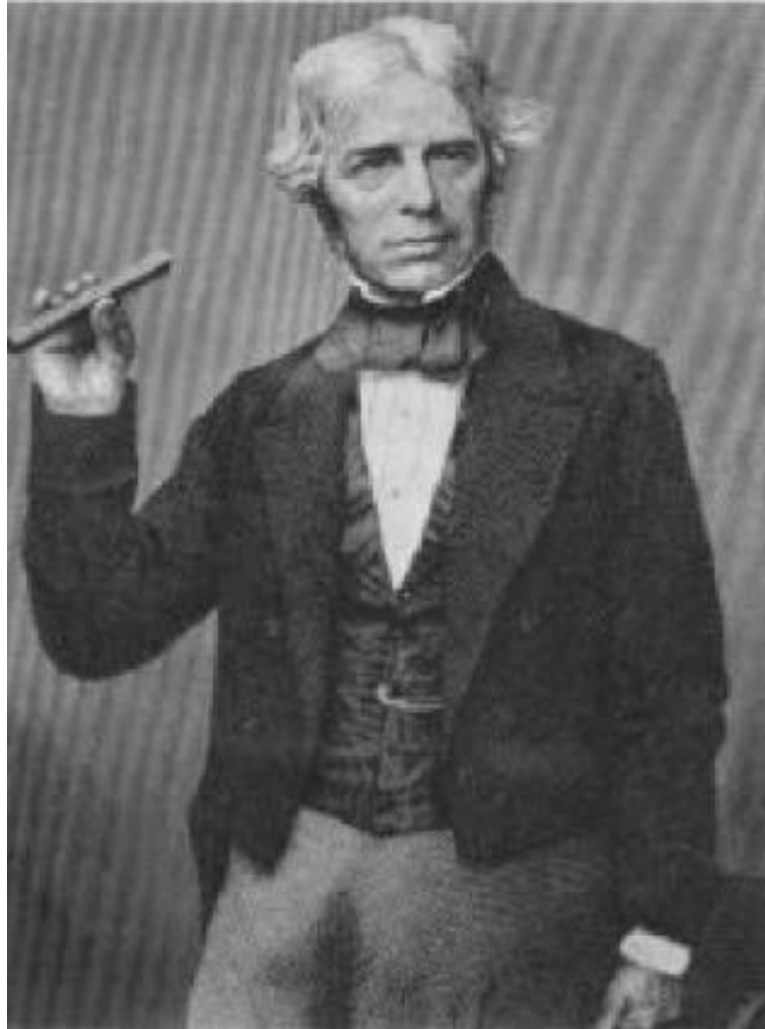


→ Capacitors

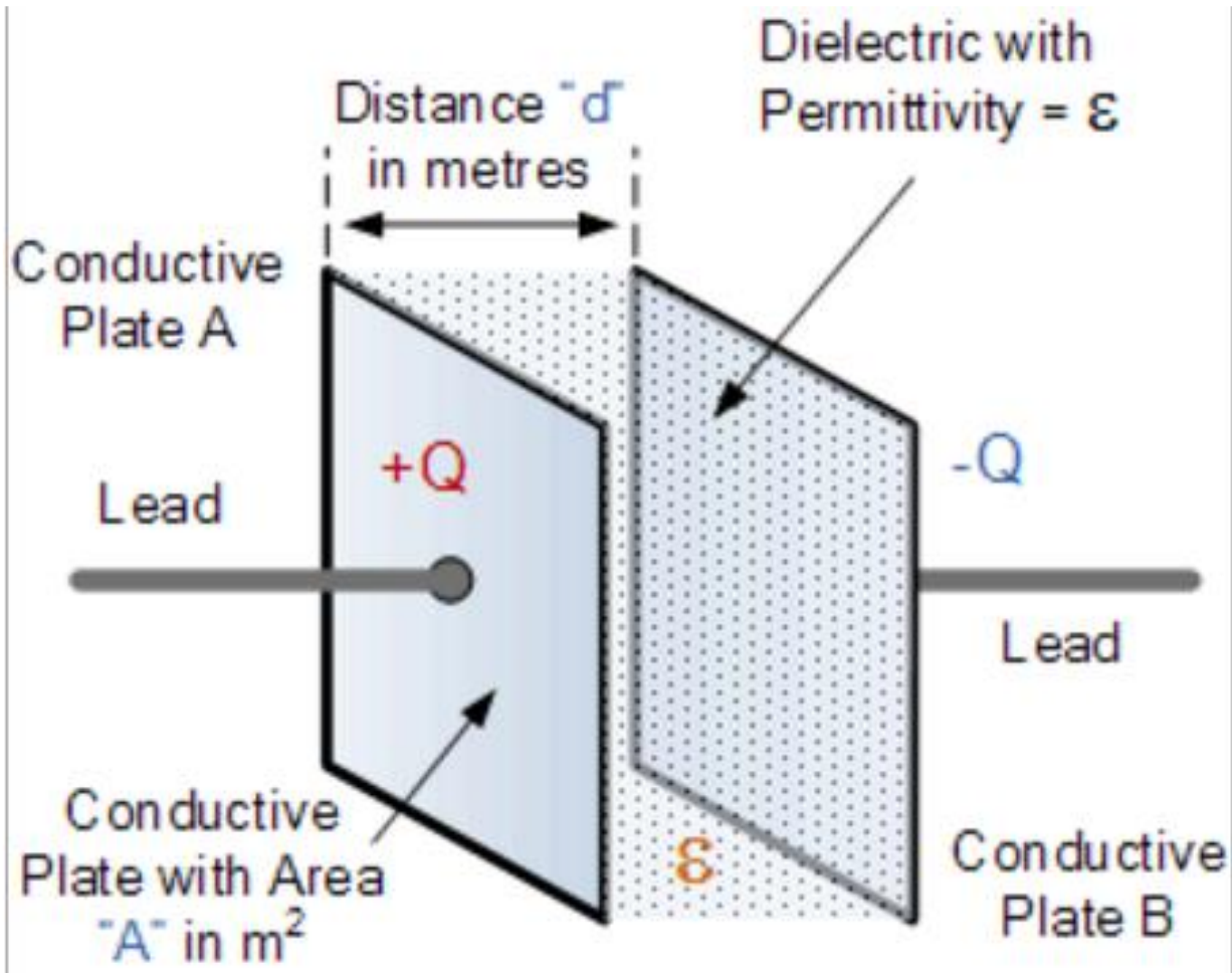
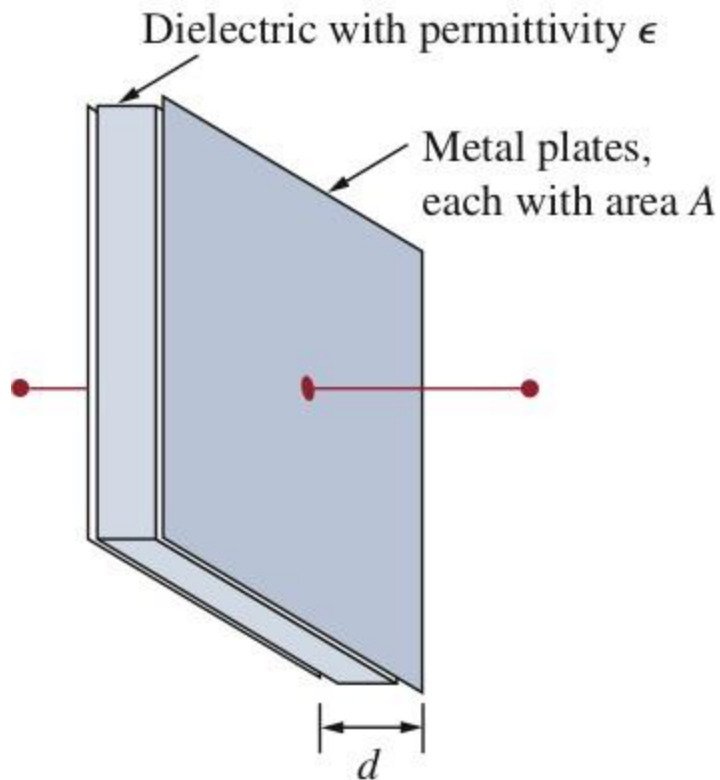
# Capacitors


- A **capacitor** consists of two **conducting plates** separated by **an insulator** (or dielectric).




$$C = \frac{\epsilon A}{d}$$

$$\epsilon = \epsilon_r \epsilon_0$$

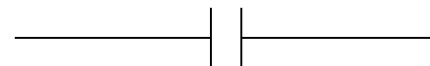
$$\epsilon_0 = 8.854 \times 10^{-12} \text{ (F/m)}$$



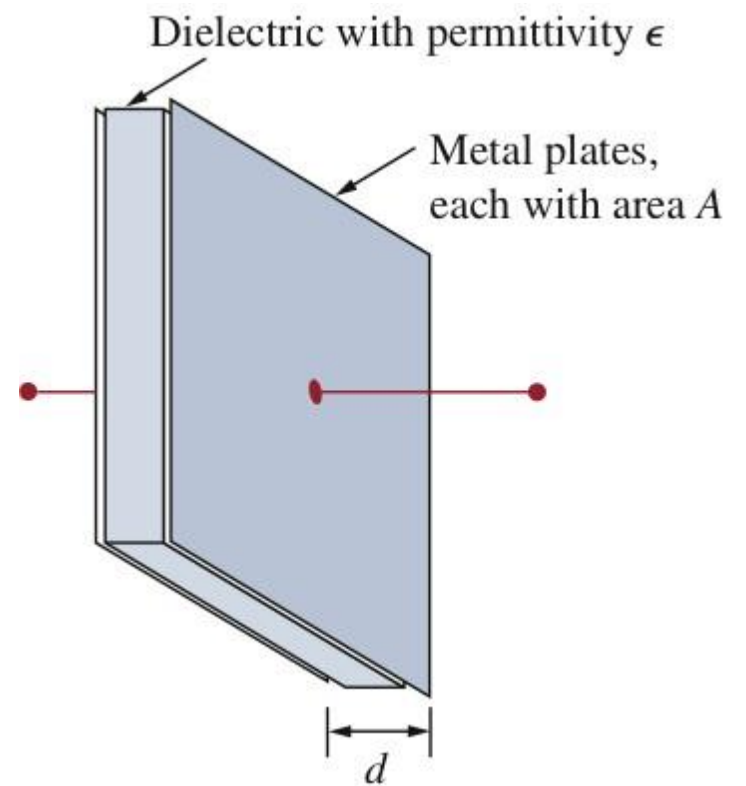

$$C = \frac{\epsilon A}{d}$$

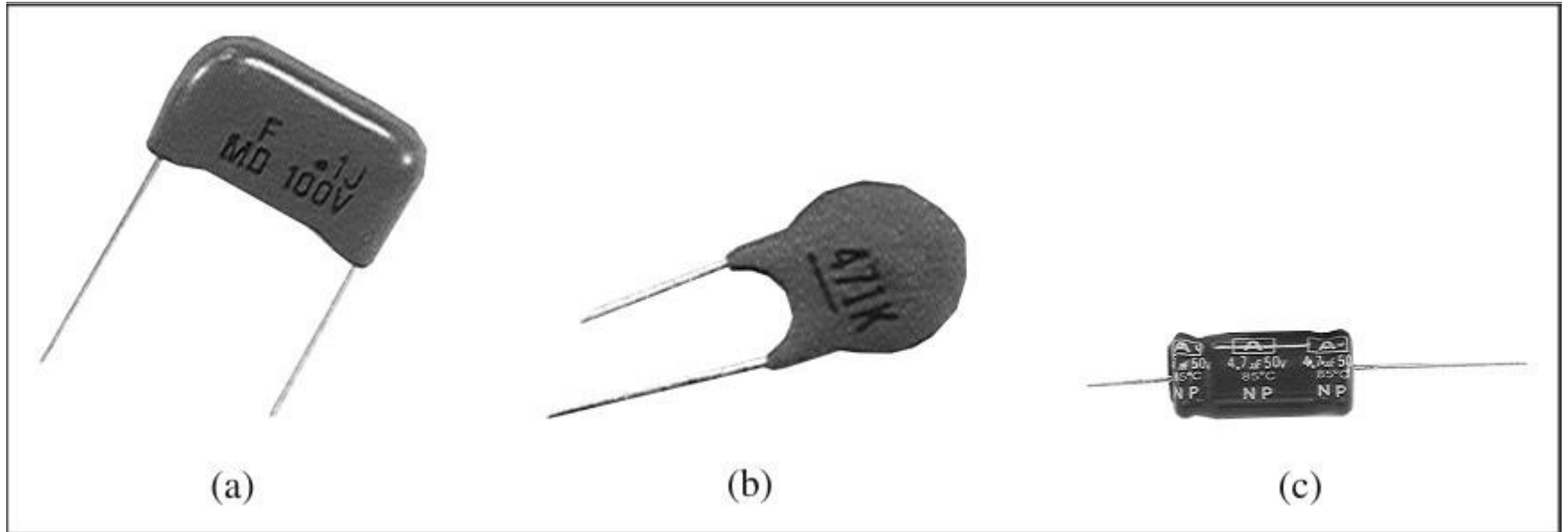- Three factors affecting the value of capacitance:
  1. Area: the larger the area, the greater the capacitance.
  2. Spacing between the plates: the smaller the spacing, the greater the capacitance.
  3. Material permittivity: the higher the permittivity, the greater the capacitance.



(a)

(b)

(c)

(a) Polyester capacitor, (b) Ceramic capacitor, (c) Electrolytic capacitor






(a)



(b)


Variable capacitors

# Basic of Caps

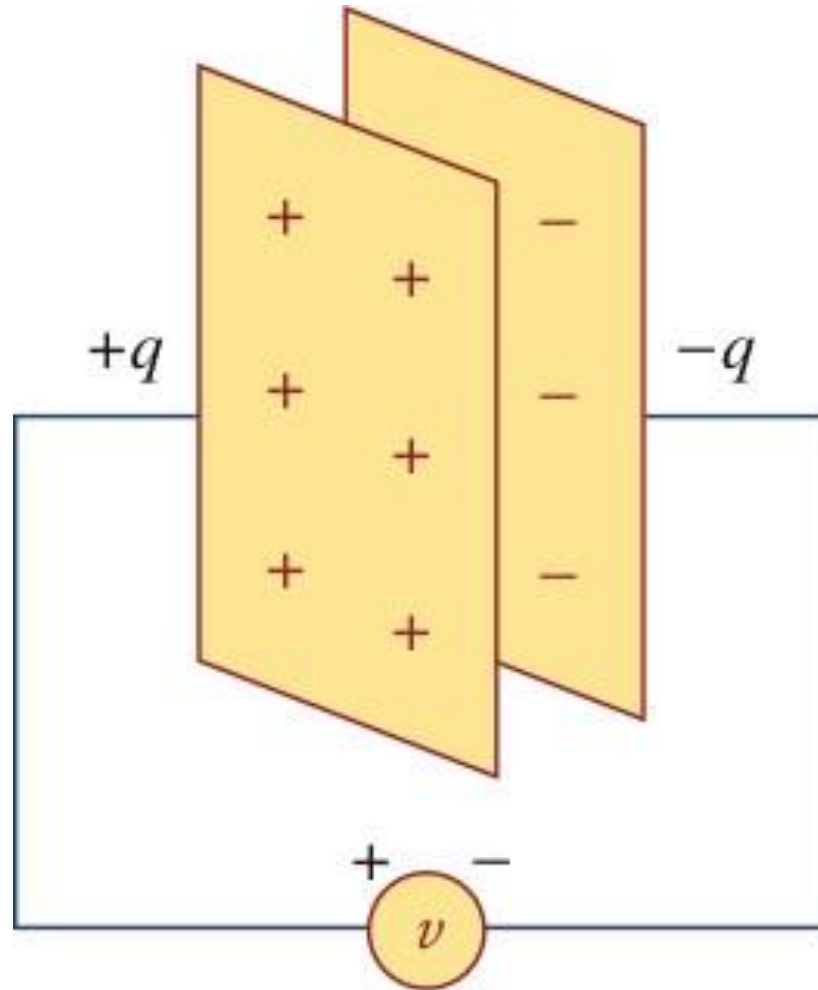
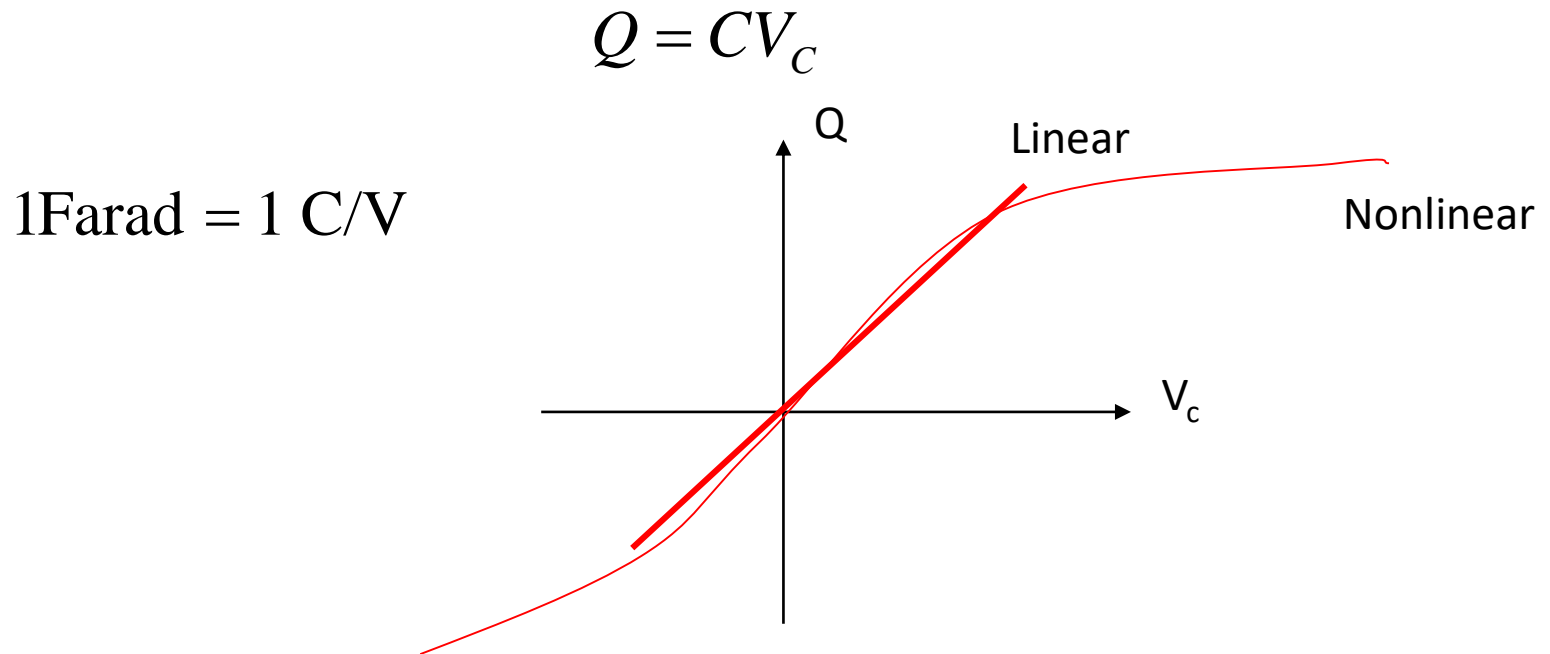
# Charge in Capacitors


- The relation between the **charge** in plates and the **voltage** across a capacitor:




# Voltage Limit on a Capacitor

- Since  $Q=Cv$ , the plate charge increases as the voltage increases. The electric field intensity between two plates increases.
- If the voltage across the capacitor is so large that the field intensity is large enough to **break down** the insulation of the dielectric, the capacitor is out of work.
- Hence, every practical capacitor has a **maximum limit on its operating voltage.**

# I-V Relation of Capacitor

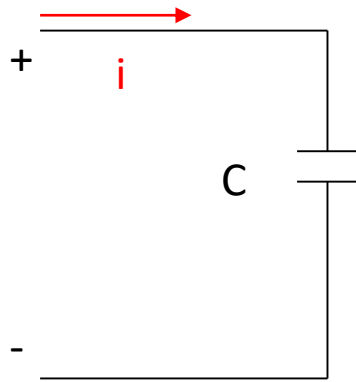

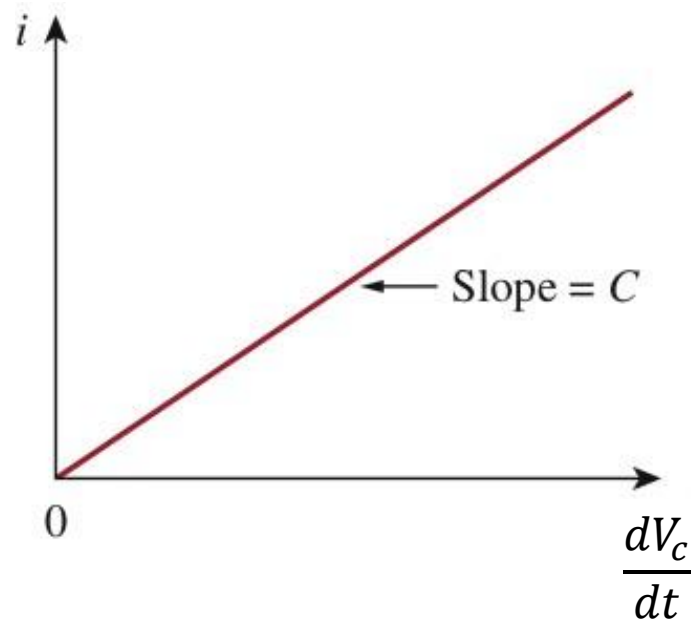
$$Q = CV_c, i = \frac{dQ}{dt} = C \frac{dV_c}{dt}$$


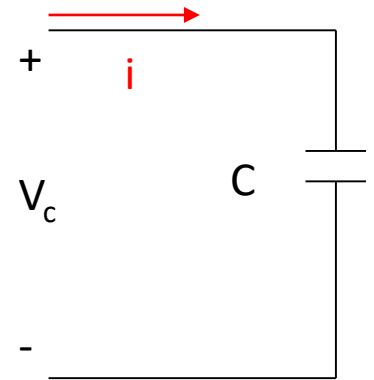
# Physical Meaning

$$i = \frac{dQ}{dt} = C \frac{dV_c}{dt}$$



- $V_c$ : a constant voltage across a capacitor
- When  $V_c = 0$ 
  - The same potential between capacitor's two inner plates create no current through the capacitor,
  - the capacitor in this case: an **open circuit**.
- If voltage is abruptly changed
  - $i$ : an infinite value
  - Impossible to have **an abrupt change in its voltage** except an infinite current is applied (practically impossible)

1. A capacitor is an open circuit ( $i=0$ ) at DC (direct current,  $f=0$ ,  $t=\infty$ )
2. The voltage on a capacitor cannot change abruptly.

$$V_c(t_{0+}) = V_c(t_{0-})$$


$$i = \frac{dQ}{dt} = C \frac{dV_c}{dt}$$

In other words, if this does not satisfy, current can't exist → as you can't differentiate  $V_c$

$$i = C \frac{dV_C}{dt} \quad \Longrightarrow \quad V_C(t) = \frac{1}{C} \int_{t_0}^t i dt + V_C(t_0)$$

$$\Longrightarrow \quad V_C(t) - V_C(t_0) = \frac{1}{C} \int_{t_0}^t i dt$$
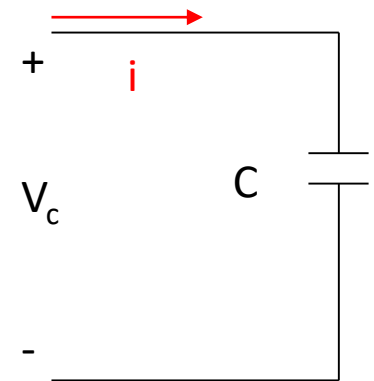
$$\Longrightarrow \quad \frac{Q(t)}{C} - \frac{Q(t_0)}{C} = \frac{1}{C} \int_{t_0}^t i dt$$



The charge on a capacitor is an integration of current through the capacitor (which makes sense)



# Energy Storing in Capacitor


$$p = vi = CV_C \frac{dV_C}{dt}$$

$$i = C \frac{dV_C}{dt}$$

$$w = \int_{-\infty}^t p dt = C \int_{-\infty}^t V_C \frac{dV_C}{dt} dt = C \int_{V_C(-\infty)}^{V_C(t)} V_C dV_C = \frac{1}{2} CV_C^2 \Big|_{V_C(-\infty)}^{V_C(t)}$$


$$w(t) = \frac{1}{2} CV_C^2(t) \quad (V_C(-\infty) = 0)$$

$$w(t) = \frac{Q^2(t)}{2C}$$

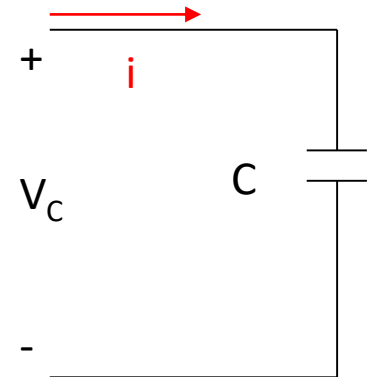


Eventually two plates potential will become same


# Model of Practical Capacitor

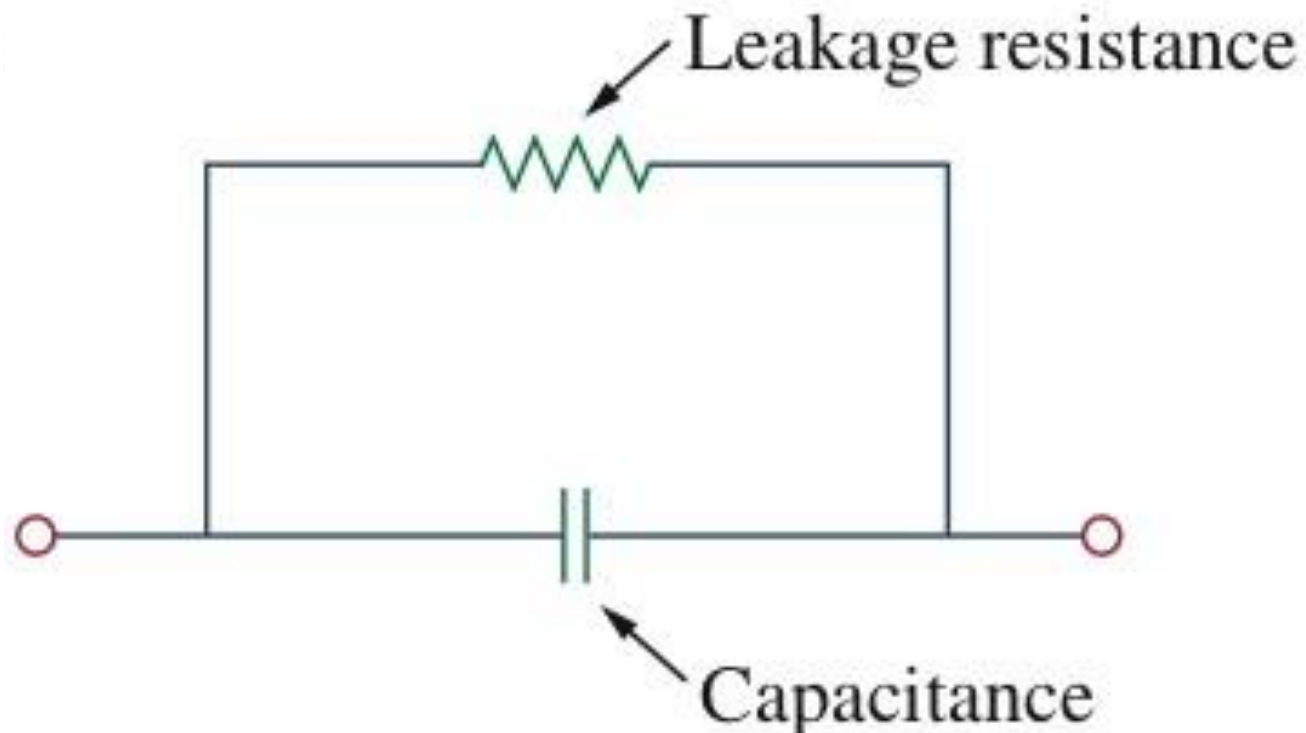

# Series and Parallel Capacitors

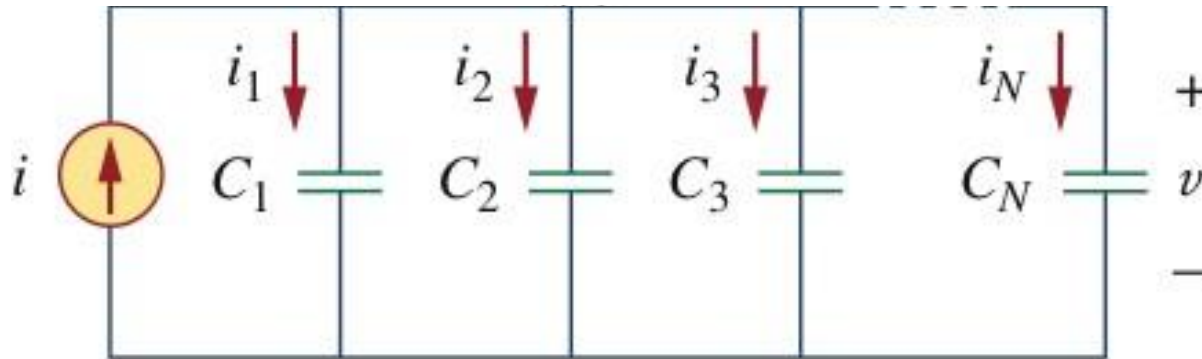

(a)

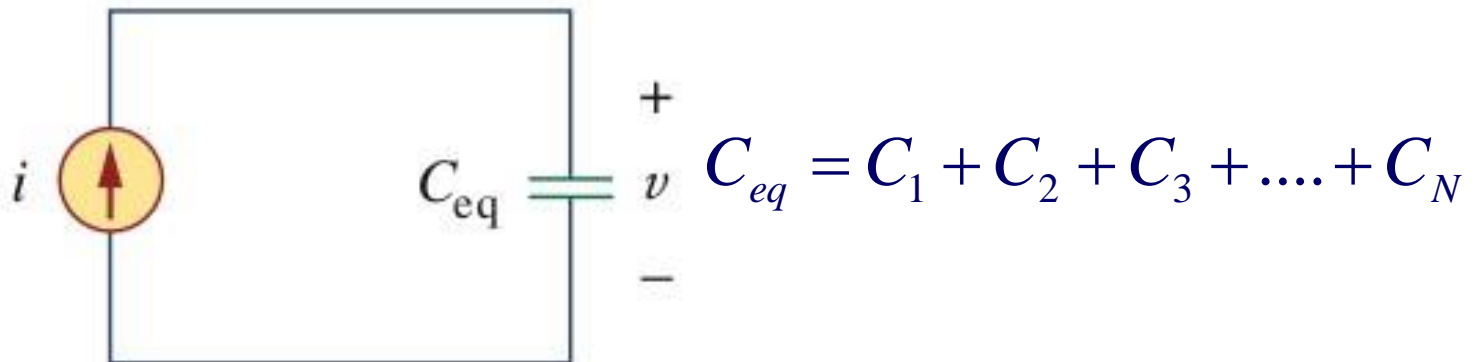

(b)

$$C_{eq} = C_1 + C_2 + C_3 + \dots + C_N$$

$$i = i_1 + i_2 + i_3 + \dots + i_N$$


$$i = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + C_3 \frac{dv}{dt} + \dots + C_N \frac{dv}{dt}$$

$$= \left( \sum_{k=1}^N C_K \right) \frac{dv}{dt} = C_{eq} \frac{dv}{dt}$$


$$C_{eq} = C_1 + C_2 + C_3 + \dots + C_N$$

- The **equivalent capacitance** of  $N$  parallel-connected capacitors is the sum of the individual capacitance.

# Series Capacitors

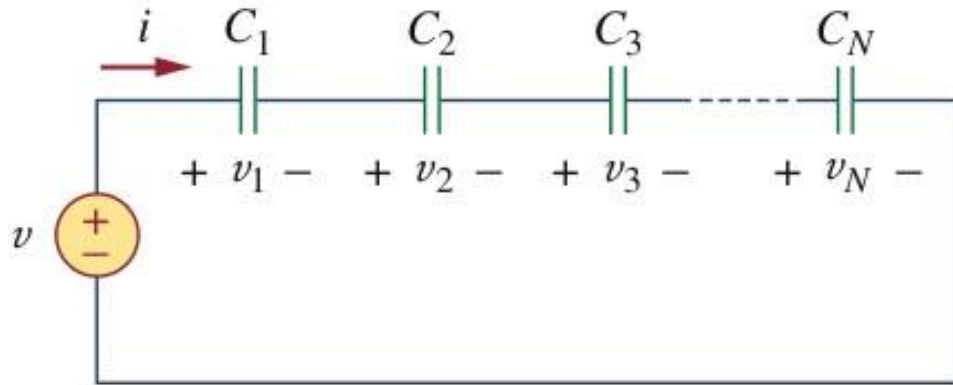

(a)

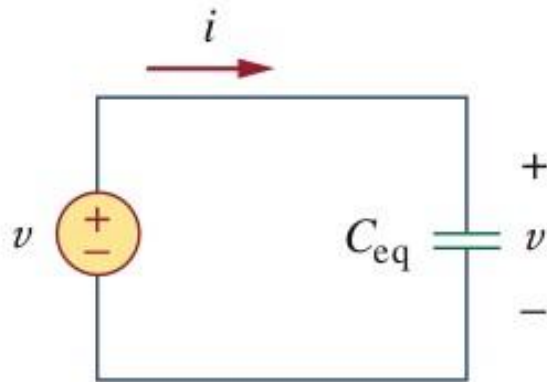



(b)

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_N}$$

$$v(t) = v_1(t) + v_2(t) + \dots + v_N(t)$$

$$\frac{1}{C_{eq}} \int_{-\infty}^t i d\tau = \left( \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_N} \right) \int_{-\infty}^t i d\tau$$
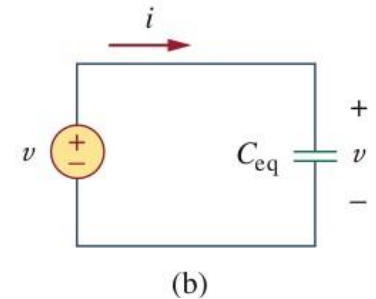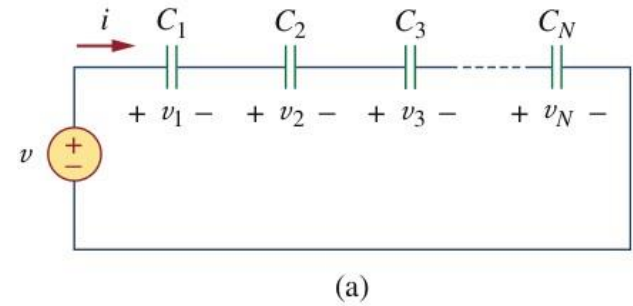
$$\frac{q(t)}{C_{eq}} = \frac{q(t)}{C_1} + \frac{q(t)}{C_2} + \dots + \frac{q(t)}{C_N}$$



- The **equivalent capacitance** of series-connected capacitors is the reciprocal of the sum of the reciprocals of the individual capacitances.


$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

# Summary-Capacitor

- These results enable us to look the capacitor in this way:  **$1/C$  has the equivalent effect as the eqv. resistance** calculation
- The equivalent capacitor of capacitors connected in parallel or series can be obtained via this point of view, so is the Y- $\Delta$  connection and its transformation


# Inverting Integrator

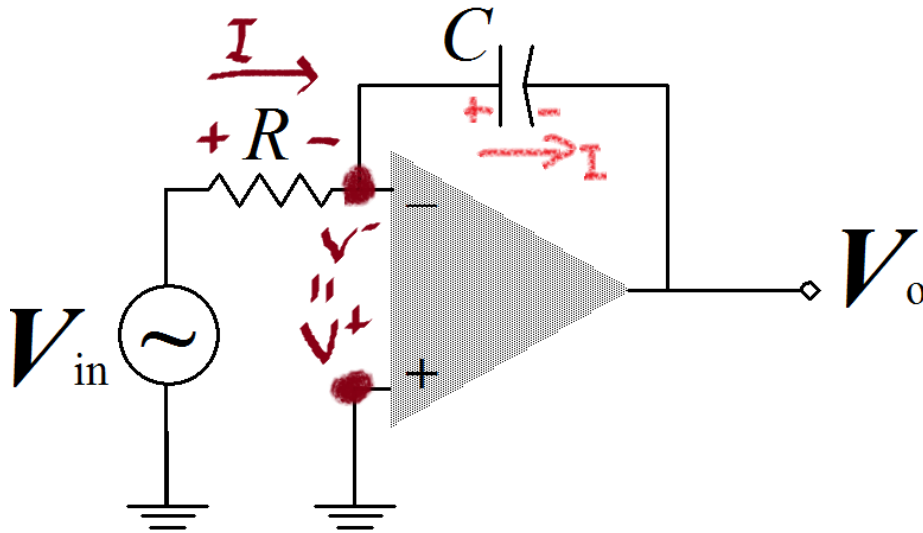

$V_o$  in terms of  $V_{in}$ ?




# Op-Amp Differentiator

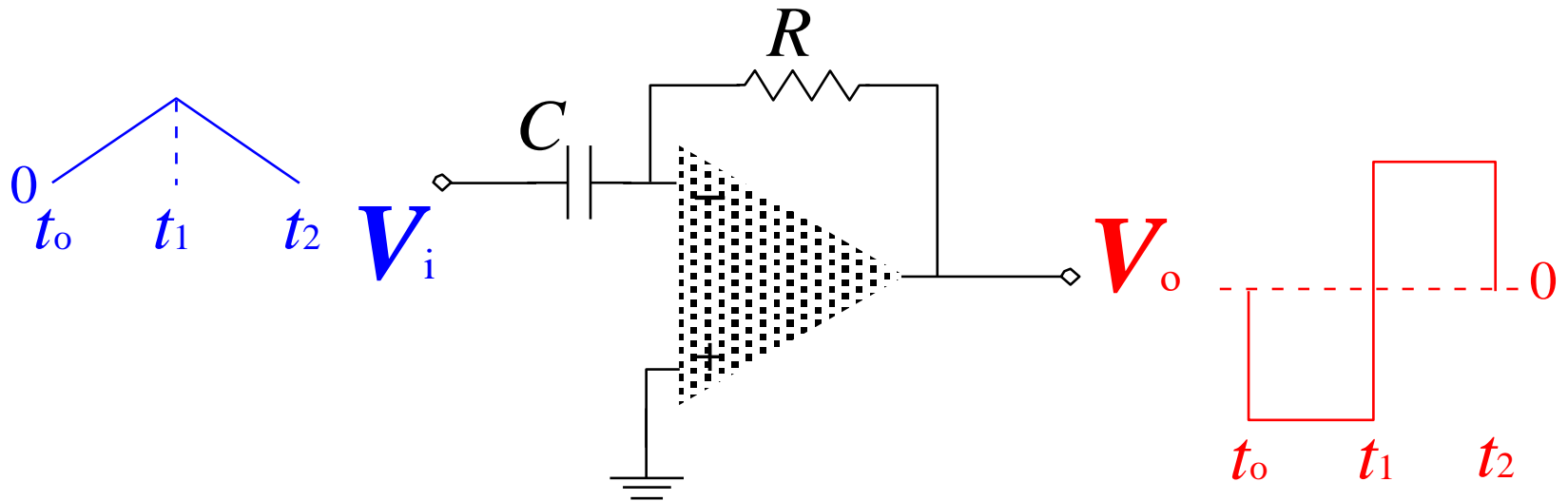

$V_o$  in terms of  $V_{in}$ ?


# Joseph Henry (1779-1878)



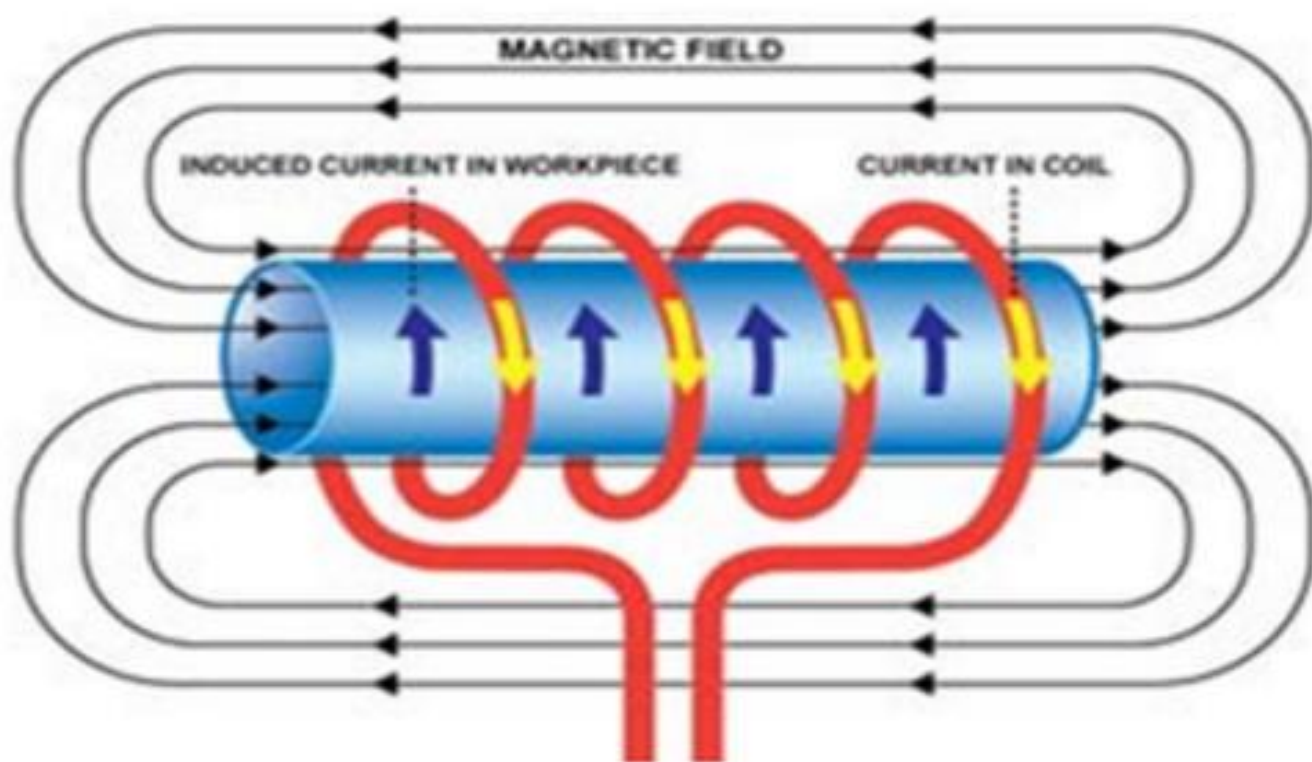


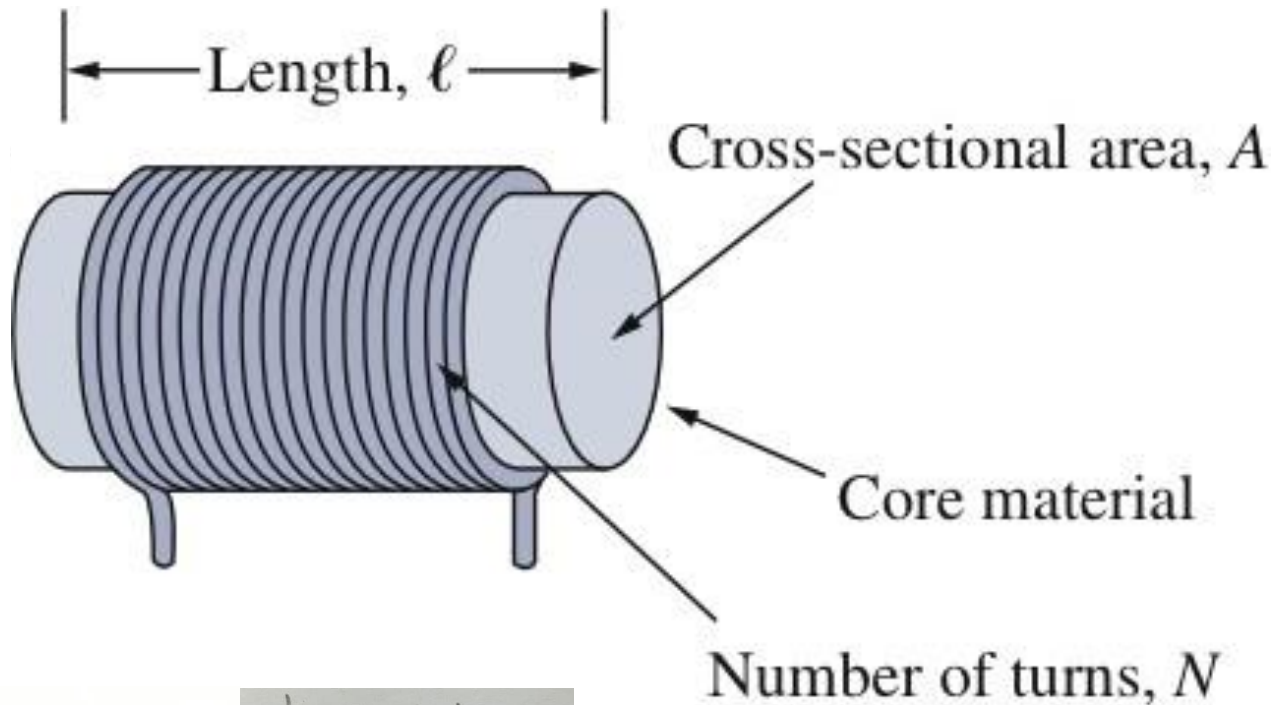
# Inductors

- An inductor is made of a coil of conducting wire



$$L = \frac{N^2 \mu A}{\ell}$$

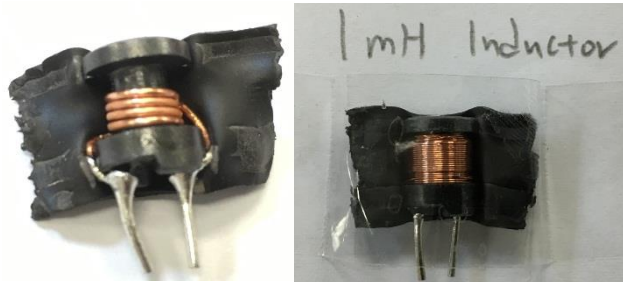

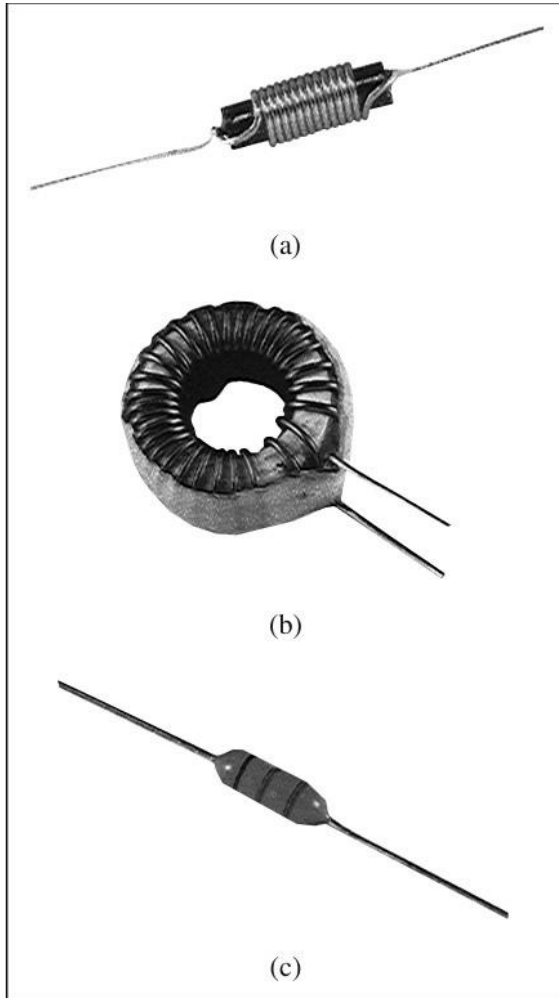

$$L = \frac{N^2 \mu A}{l}$$

$$\mu = \mu_r \mu_0$$


$$\mu_0 = 4\pi \times 10^{-7} \text{ (H/m)}$$

$N$ : number of turns.


$l$ : length.

$A$ : cross – sectional area.


$\mu$ : permeability of the core

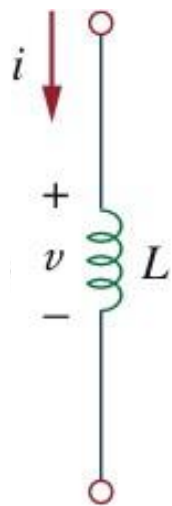

(a)

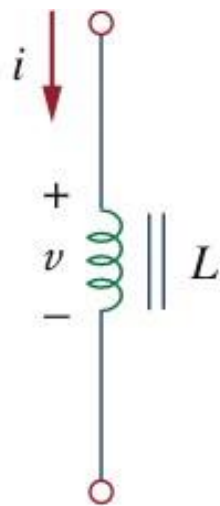

(b)

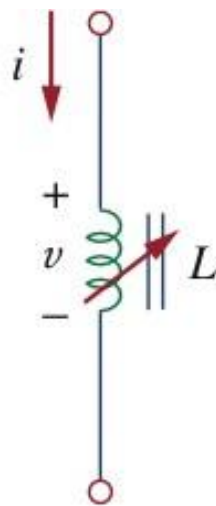

(c)


- (a) air-core
- (b) iron-core
- (c) variable iron-core

# Flux in Inductors

- The relation between the flux in inductor and the current through the inductor:

$$\phi = Li$$

1H = 1 Weber/A

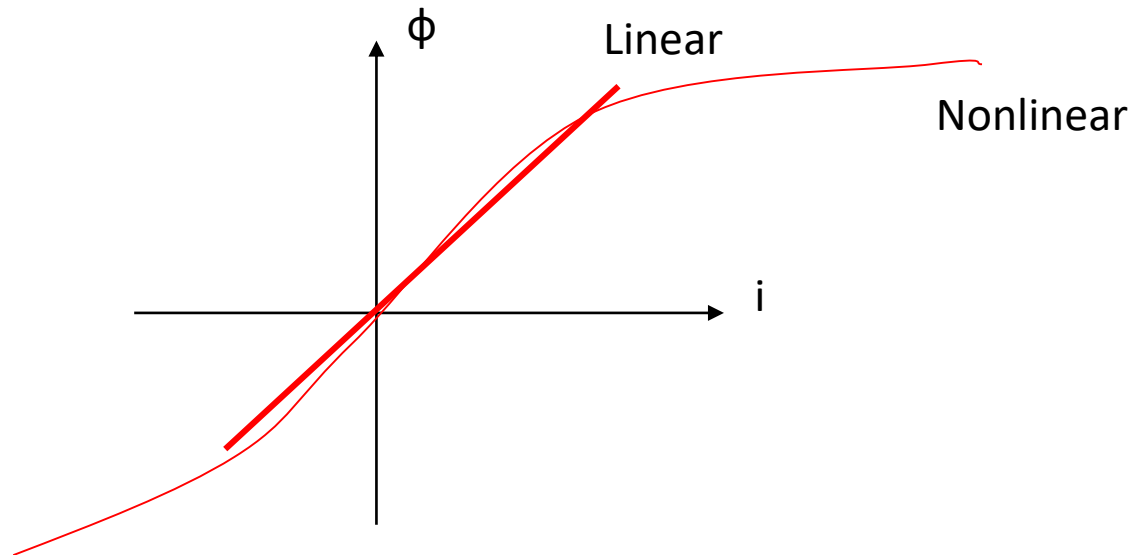

# Energy Storage Forms: Cap vs. Ind



- An inductor is a passive element designed to store energy in the **magnetic** field while a capacitor stores energy in the **electric** field.


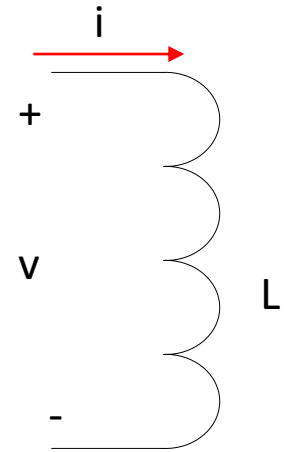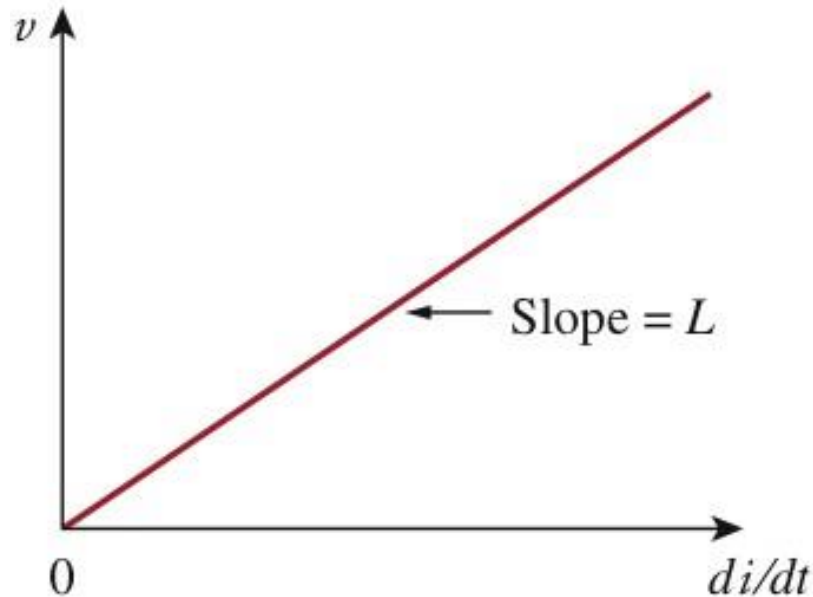
# I-V Relation of Inductors

- An **inductor** consists of a coil of conducting wire.


$$v = \frac{d\phi}{dt} = L \frac{di}{dt}$$


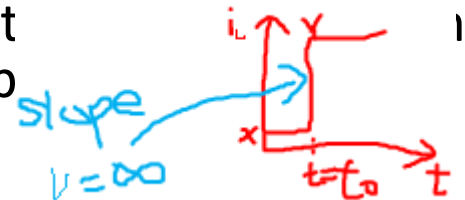
# Physical Meaning

$$V = \frac{d\phi}{dt} = L \frac{di_L}{dt}$$

- $i_L$  : a constant current through an inductor
- When  $i_L=0$ 
  - There is no electron's flow through the inner inductor's spiral coil
  - The inductor in this case nothing but just a wire: **a short circuit** →  **$V=0$**
- If current ( $i_L$ ) is **abruptly changed**
  - $V$ : and infinite value
  - Impossible to have an abrupt change in it (infinite voltage across the inductor is app impossible)



1. An inductor is a short circuit ( $V=0$ ) at DC (direct current,  $f=0$ ,  $t=\infty$ )
2. The current through an inductor cannot change instantaneously.


$$i_L(t_{0+}) = i_L(t_{0-})$$

$$V = \frac{d\phi}{dt} = L \frac{di_L}{dt}$$

In other words, if this does not satisfy, voltage can't exist → as you can't differentiate  $i_L$

$$V(t) = L \frac{di_L}{dt}$$

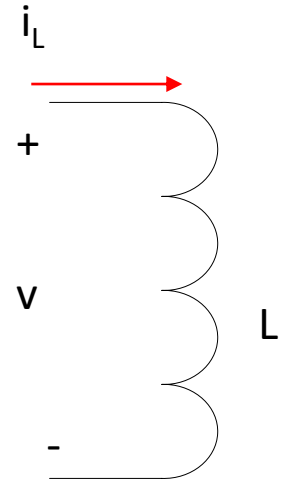
$$\Rightarrow i_L(t) = \frac{1}{L} \int_{t_0}^t v(t) dt + i_L(t_0)$$


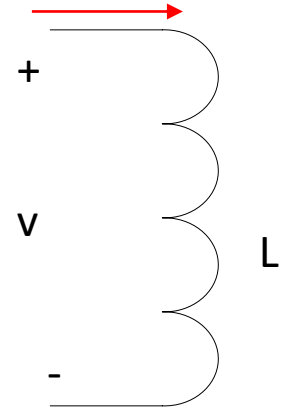
# Energy Stored in an Inductor

$$P = vi = \left( L \frac{di}{dt} \right) i$$


$$\begin{aligned} w &= \int_{-\infty}^t p dt = \int_{-\infty}^t \left( L \frac{di}{dt} \right) i dt \\ &= L \int_{i(-\infty)}^{i(t)} i di = \frac{1}{2} Li^2(t) - \frac{1}{2} Li^2(-\infty) \quad i(-\infty) = 0, \end{aligned}$$




- The energy stored in an inductor

$$w(t) = \frac{1}{2} Li^2(t)$$

# Model of a Practical Inductor

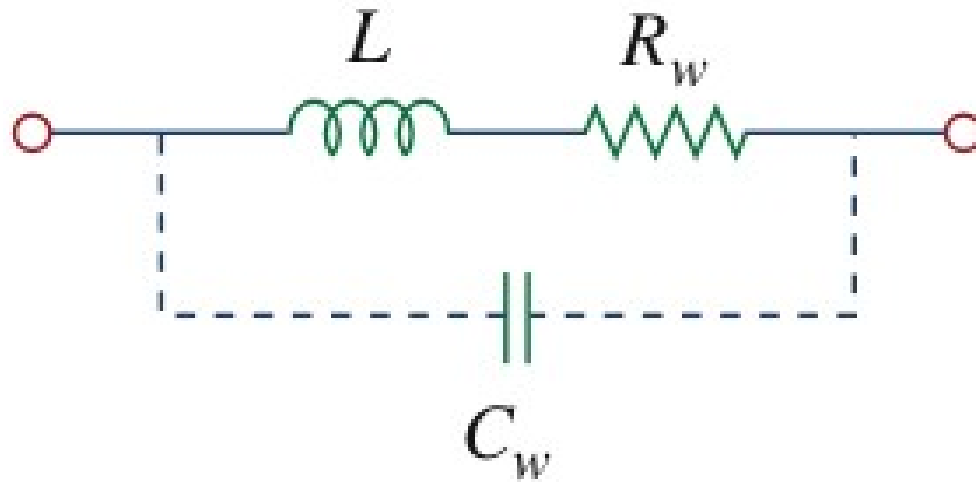


# Inductors in Series

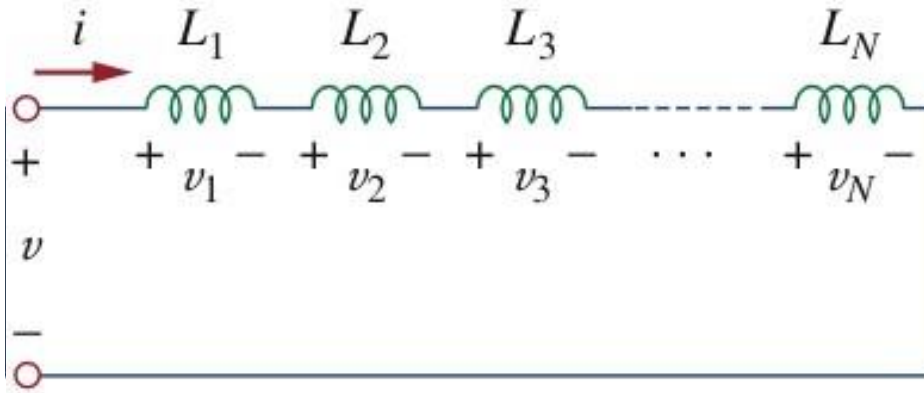

(a)
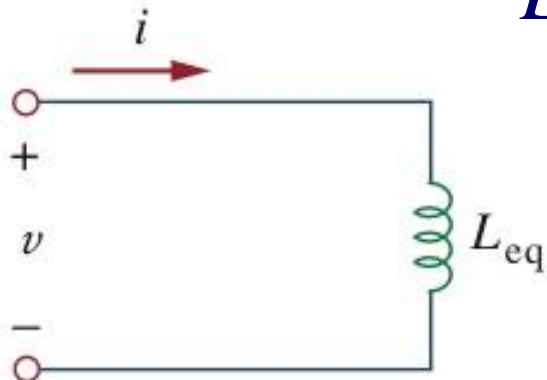
$$L_{eq} = L_1 + L_2 + L_3 + \dots + L_N$$



(b)

- Applying KVL to the loop,

$$v = v_1 + v_2 + v_3 + \dots + v_N$$


- Substituting  $v_k = L_k di/dt$  results in

$$\begin{aligned} v &= L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt} + \dots + L_N \frac{di}{dt} \\ &= (L_1 + L_2 + L_3 + \dots + L_N) \frac{di}{dt} \\ &= \left( \sum_{K=1}^N L_K \right) \frac{di}{dt} = L_{eq} \frac{di}{dt} \end{aligned}$$


$$L_{eq} = L_1 + L_2 + L_3 + \dots + L_N$$



# Inductors in Parallel

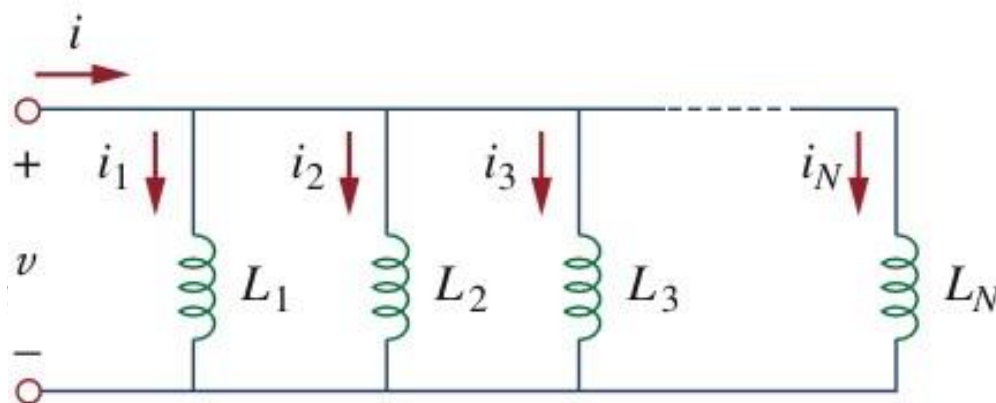

(a)

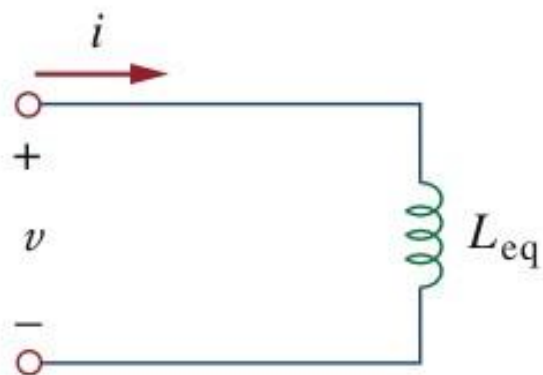

(b)

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}$$

- Using KCL,  $i = i_1 + i_2 + i_3 + \dots + i_N$

- But  $i_k = \frac{1}{L_k} \int_{t_0}^t v dt + i_k(t_0)$

$$\therefore i = \frac{1}{L_1} \int_{t_0}^t v dt + i_1(t_0) + \frac{1}{L_2} \int_{t_0}^t v dt + i_2(t_0) + \dots + \frac{1}{L_N} \int_{t_0}^t v dt + i_N(t_0)$$

$$= \left( \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N} \right) \int_{t_0}^t v dt + i_1(t_0) + i_2(t_0) + \dots + i_N(t_0)$$

$$= \left( \sum_{k=1}^N \frac{1}{L_k} \right) \int_{t_0}^t v dt + \sum_{k=1}^N i_k(t_0) = \frac{1}{L_{eq}} \int_{t_0}^t v dt + i(t_0)$$

- The inductor in various connection has the same effect as the resistor. Hence, the Y- $\Delta$  transformation of inductors can be similarly derived.

Relation	Resistor ( $R$ )	Capacitor ( $C$ )	Inductor ( $L$ )
$v-i$ :	$v = iR$	$v = \frac{1}{C} \int_{t_0}^t i \, dt + v(t_0)$	$v = L \frac{di}{dt}$
$i-v$ :	$i = v/R$	$i = C \frac{dv}{dt}$	$i = \frac{1}{L} \int_{t_0}^t v \, dt + i(t_0)$
$p$ or $w$ :	$p = i^2 R = \frac{v^2}{R}$	$w = \frac{1}{2} C v^2$	$w = \frac{1}{2} L i^2$
Series:	$R_{eq} = R_1 + R_2$	$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$	$L_{eq} = L_1 + L_2$
Parallel:	$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$	$C_{eq} = C_1 + C_2$	$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$
At dc:	Same	Open circuit	Short circuit
Circuit variable that cannot change abruptly:	Not applicable	$v$	$i$