

# CET 141: Day 13

Dr. Noori KIM

Current - Voltage relationship  $I = f(V)$  for two terminal devices.


Linear elements

$$I = V/R$$

$$I = C \cdot dV/dt$$

$$I = \frac{1}{L} \int V dt$$

$$I = I_s [e^{V/nV_T} - 1]$$

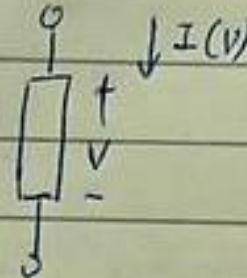

Nonlinear elements


Transistors  $\Rightarrow$  adding a third terminal

① Type 1 : BJT

$\Rightarrow$  Current - controlled current flow.

② Type 2 : FETs

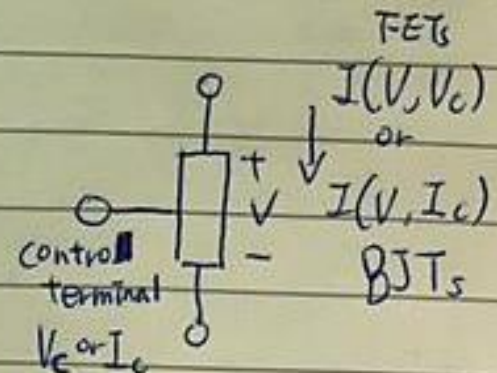$\Rightarrow$  Voltage - controlled current flow



# Transistor

- Basic: Back-to-back two diode connection
- Three terminal component
  - i.e., Gate Source Drain / Collector Base Emitter
  - Transistor as a switch: Push button, + and – terminals
  - Transistor as an amplifier

# Logic gate


- An idealized or physical device implementing a Boolean function
  - Performs a logical operation on one or more logical inputs
  - Produces a single logical output
- **Basic building elements: transistors**
  - In modern practice, most gates are made from field-effect transistors (FETs), particularly **MOSFETs**.

NOT truth table

True : 3.3V  
False : 0V

Our MCU  
V<sub>dd</sub> 3.3V

In	Out
True	False
False	True

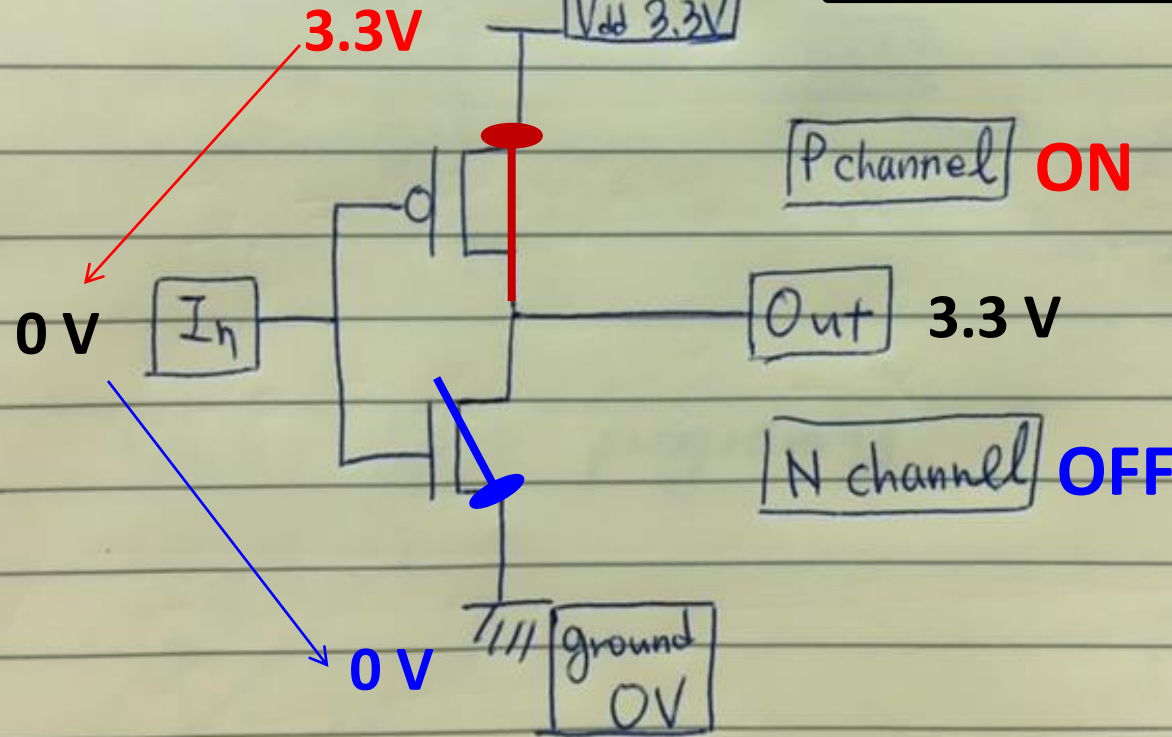

A basic element to represent a bit


This is a NOT symbol



Or an inverter

# Latch

- Basic element: Two inverters

 


- A bistable multivibrator

# Flip flop


- Basic storage elements for today's registers and memories
  - Bistable multivibrator
  - Feedback path
- Basic element: two latches (master and slave) with a forcing switch
  - Synchronous devices
  - Operates on clock edges
- Example: SR, D, T flip flops



## Digital terminologies :

 

Analog term.  
Ground : 0

 

Enable, High





- Outputs of sequential logic depend on current *and* prior input values – it has ***memory***.
- Some definitions:
  - **State**: all the information about a circuit necessary to explain its future behavior
  - **Latches and flip-flops**: **state elements** that store one bit of state
  - **Synchronous sequential circuits**: combinational logic followed by a bank of flip-flops

# More about State Elements

- The state of a circuit influences its future behavior
- State elements store state
  - Bistable circuit
  - SR Latch
  - D Latch
  - D Flip-flop
  - JK, T Flip-flops
  
# Bistable Circuit

- Fundamental building block of other state elements
- Two outputs:  $Q$ ,  $\overline{Q}$
- No inputs



# Bistable Circuit Analysis



- Consider the two possible cases:

–  $Q = 0$ :

then  $Q = 0, \bar{Q} = 1$  (consistent)

–  $Q = 1$ :

then  $Q = 1, \bar{Q} = 0$  (consistent)

  

- Stores 1 bit of state in the state variable, Q (or  $\bar{Q}$ )
- But there are **no inputs to control the state**


# A Latch

- We want to latch a bit information from input



SR Latch : NOR type ✓  
↙  
NAND type.

⇓  
It latches "0" or "1"

 


$Q \rightarrow$   
Reset means Output = 0  
Set " 0 = 1

R=1 Q=0

S=1 Q=1

# SR (Set/Reset) Latch


- SR Latch

 

- Consider the four possible cases:

- $S = 1, R = 0$  SET
- $S = 0, R = 1$  RESET
- $S = 0, R = 0$  MEMORY
- $S = 1, R = 1$  INVALID

SR Latch  
Symbol

 

A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0



0 when one of  
inputs is high




# SR Latch Analysis

–  $S = 1, R = 0$ :

then  $Q = 1$  and  $\bar{Q} = 0$


**Set the output**

 

–  $S = 0, R = 1$ :

then  $Q = 0$  and  $\bar{Q} = 1$



**Reset the output**

 

–  $S = 0, R = 0$ :

then  $Q = Q_{prev}$

**Memory!**

  


–  $S = 1, R = 1$ :

then  $Q = 0, \bar{Q} = 0$

**Invalid State**


**$Q \neq \text{NOT } Q$**

 


# SR Latch Symbol

- SR stands for Set/Reset Latch
  - Stores one bit of state ( $Q$ )
- Control what value is being stored with  $S$ ,  $R$  inputs
  - **Set:** Make the output 1  
( $S = 1, R = 0, Q = 1$ )
  - **Reset:** Make the output 0  
( $S = 0, R = 1, Q = 0$ )
- **Must do something to avoid invalid state (when  $S = R = 1$ )**

SR Latch  
Symbol

 


# Try NAND type SR latch as well

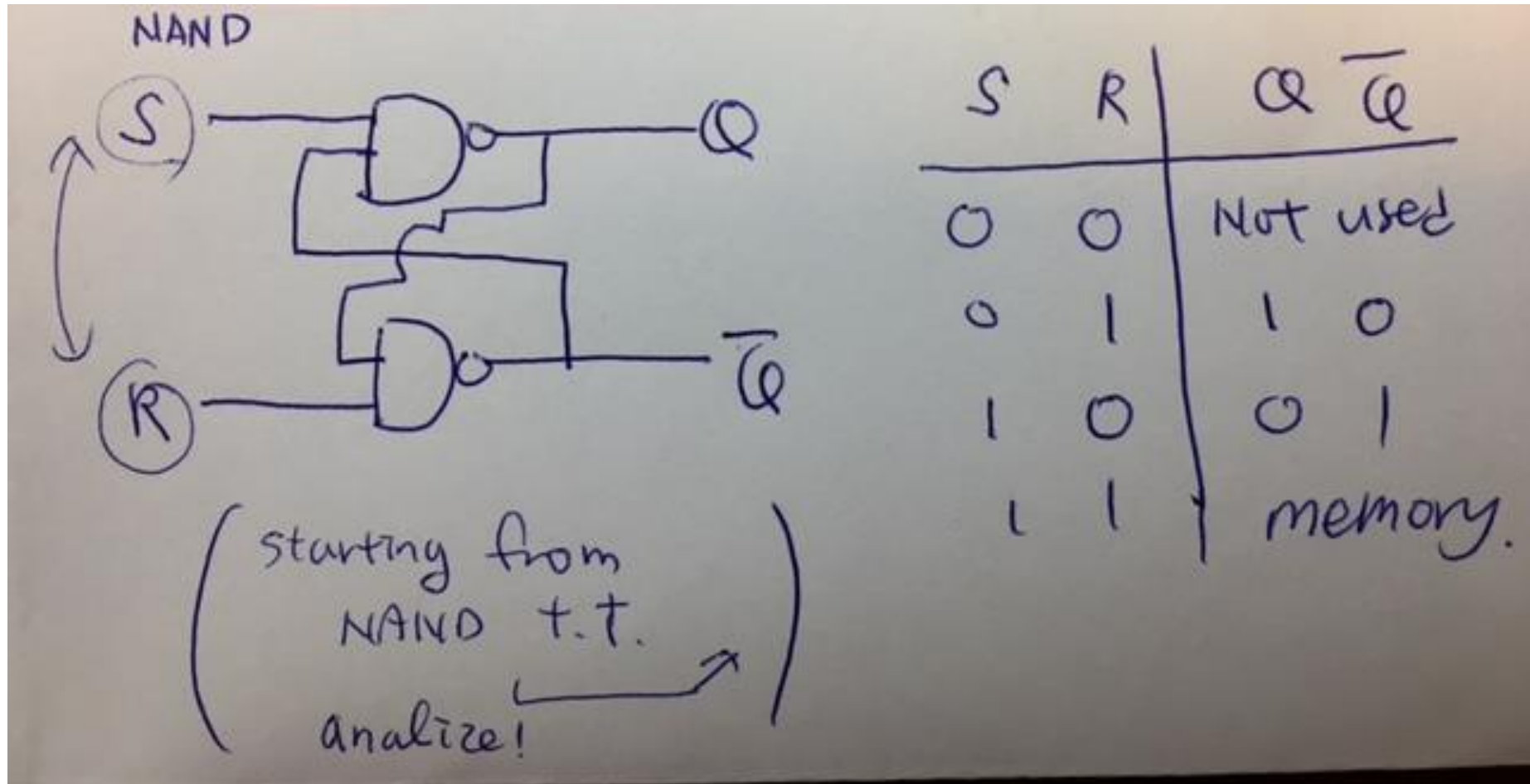


# D Latch

- Two inputs:  $CLK$ ,  $D$ 
  - $CLK$ : controls *when* the output changes
  - $D$  (the data input): controls *what* the output changes to
- Function
  - When  $CLK = 1$ ,  
 $D$  passes through to  $Q$  (*transparent*)
  - When  $CLK = 0$ ,  
 $Q$  holds its previous value (*opaque*)
- Avoids invalid case when  
 $Q \neq \text{NOT } \bar{Q}$

D Latch  
Symbol

 

# D Latch Internal Circuit

 


$CLK$	$D$	$\overline{D}$	$S$	$R$	$Q$	$\overline{Q}$
0	X					
1	0					
1	1					

# D Flip-Flop


- **Inputs:** *CLK*, *D*
- **Function**
  - Samples *D* on rising edge of *CLK*
    - When *CLK* rises from 0 to 1, *D* passes through to *Q*
    - Otherwise, *Q* holds its previous value
  - *Q* changes only on rising edge of *CLK*
- Called *edge-triggered*
- Activated on the clock edge

D Flip-Flop  
Symbols

 
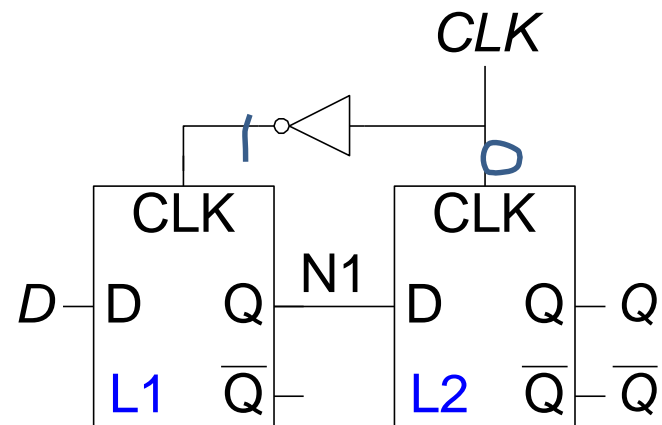
# D Flip-Flop Internal Circuit


- Two back-to-back latches (L1 and L2) controlled by complementary clocks
- When **CLK = 0**
  - L1 is transparent
  - L2 is opaque
  - $D$  passes through to N1
- When **CLK = 1**
  - L2 is transparent
  - L1 is opaque
  - N1 passes through to  $Q$
- Thus, on the edge of the clock (when **CLK rises from 0→1**)
  - $D$  passes through to  $Q$






# D flip flop vs. D latch truth tables

CLK	D	$Q_{n+1}$
0	x	$Q_n$ (No Change - memory)
1	0	0
1	1	1


 


$CLK$	$D$	$\overline{D}$	$S$	$R$	$Q$	$\overline{Q}$
0	X	X	0	0	$Q$	$\overline{Q}$
1	0	1	0	1	0	1
1	1	0	1	0	1	0

 


SAME?

# D Latch vs. D Flip-Flop

  

Level sensitive?  
Edge sensitive?


# JK Flip-Flops

 

J	K	$Q_{n+1}$
0	0	Memory, Set, Reset, Toggle
0	1	
1	0	
1	1	


$J=0, K=0$  (case I:  $Q=0$ )

		NOR
0	0	1
0	1	0
1	0	0
1	1	0

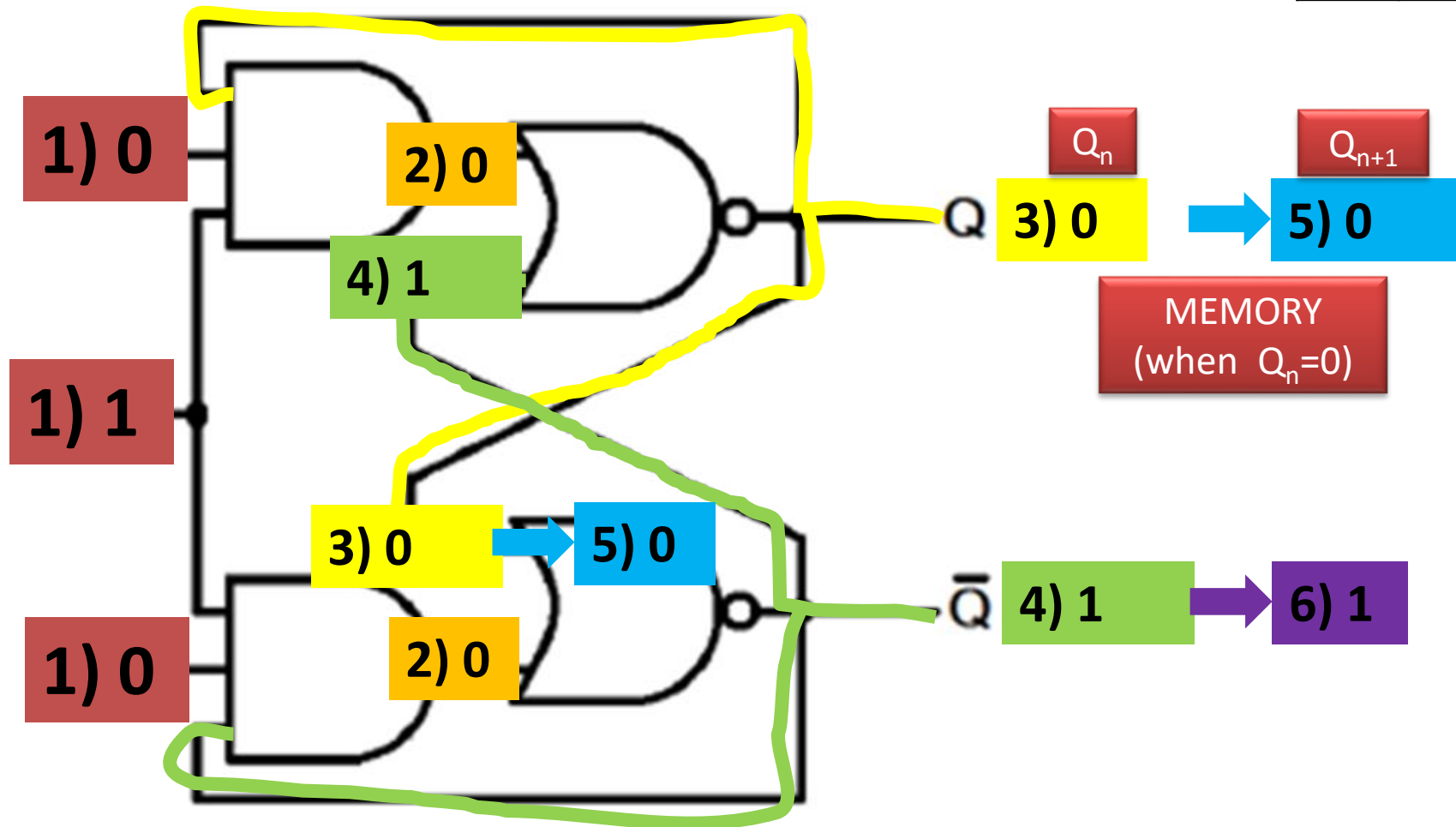



$J=0, K=0$  (case II:  $Q=1$ )

		NOR
0	0	1
0	1	0
1	0	0
1	1	0

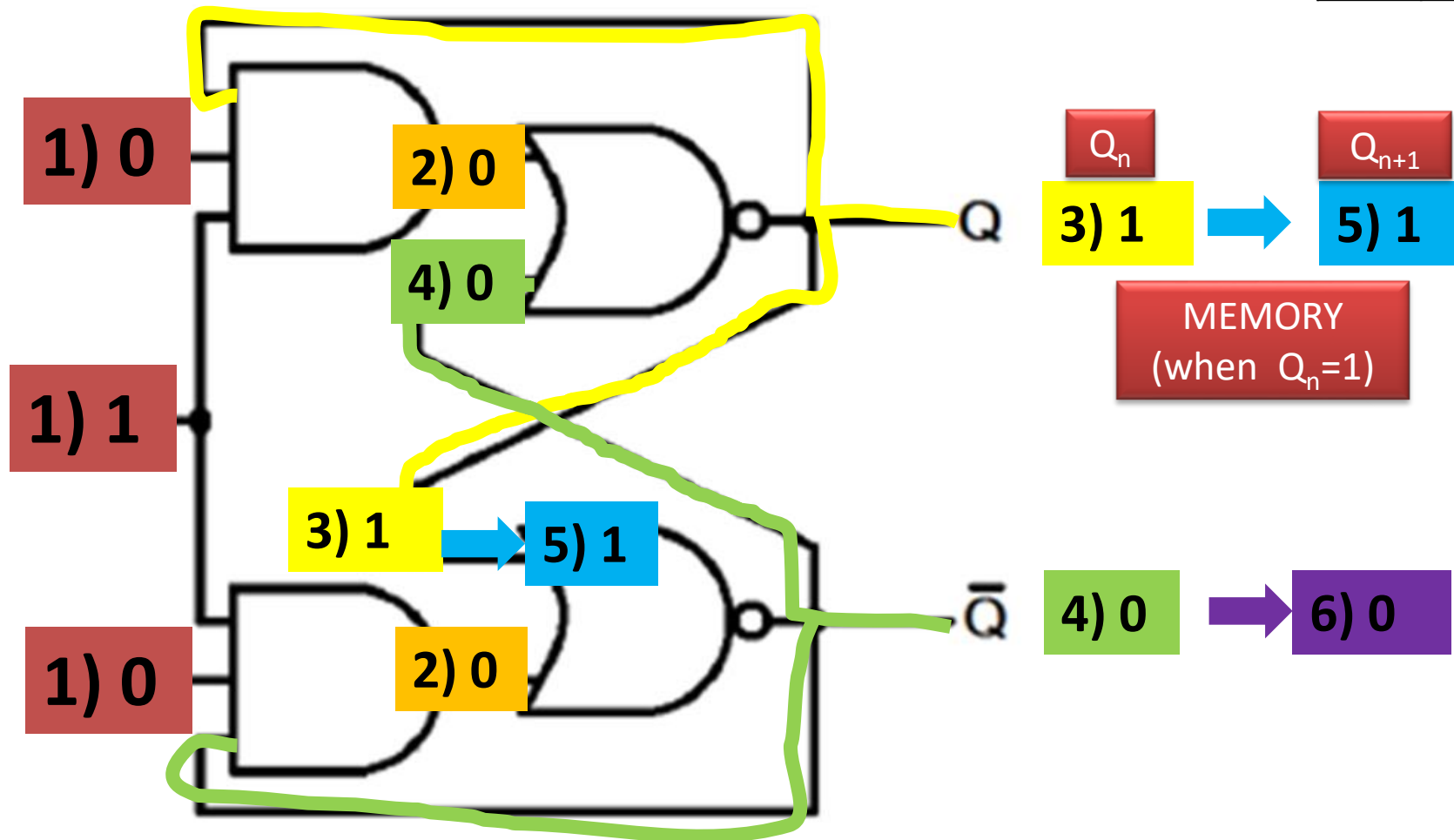

# J=0, K=1 (Case I: Q=0)


		NOR
0	0	1
0	1	0
1	0	0
1	1	0

  

Regardless of  $Q_n$ ,  $Q_{n+1}$  goes to 0 when  $J=0$ ,  $K=1$




$J=0, K=1$  (Case II:  $Q=1$ )

		NOR
0	0	1
0	1	0
1	0	0
1	1	0

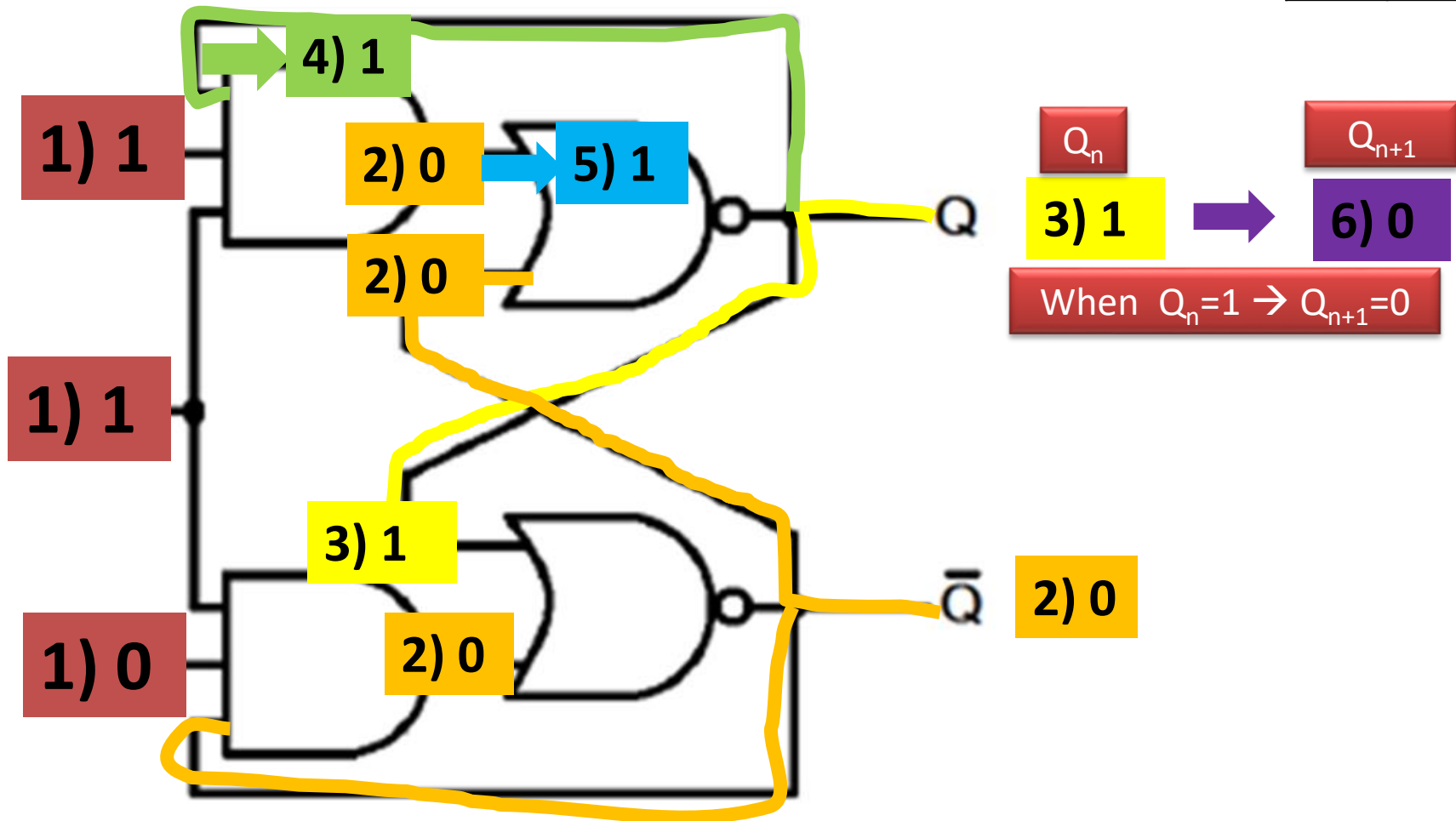

# J=1, K=0 (Case I: Q=0)


		NOR
0	0	1
0	1	0
1	0	0
1	1	0

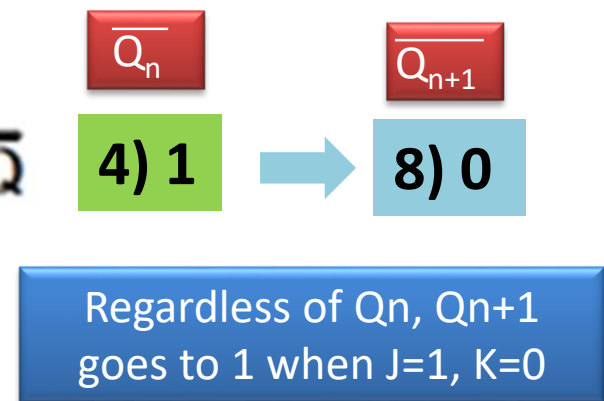  





$J=1, K=0$  (Case II:  $Q=1$ )

		NOR
0	0	1
0	1	0
1	0	0
1	1	0

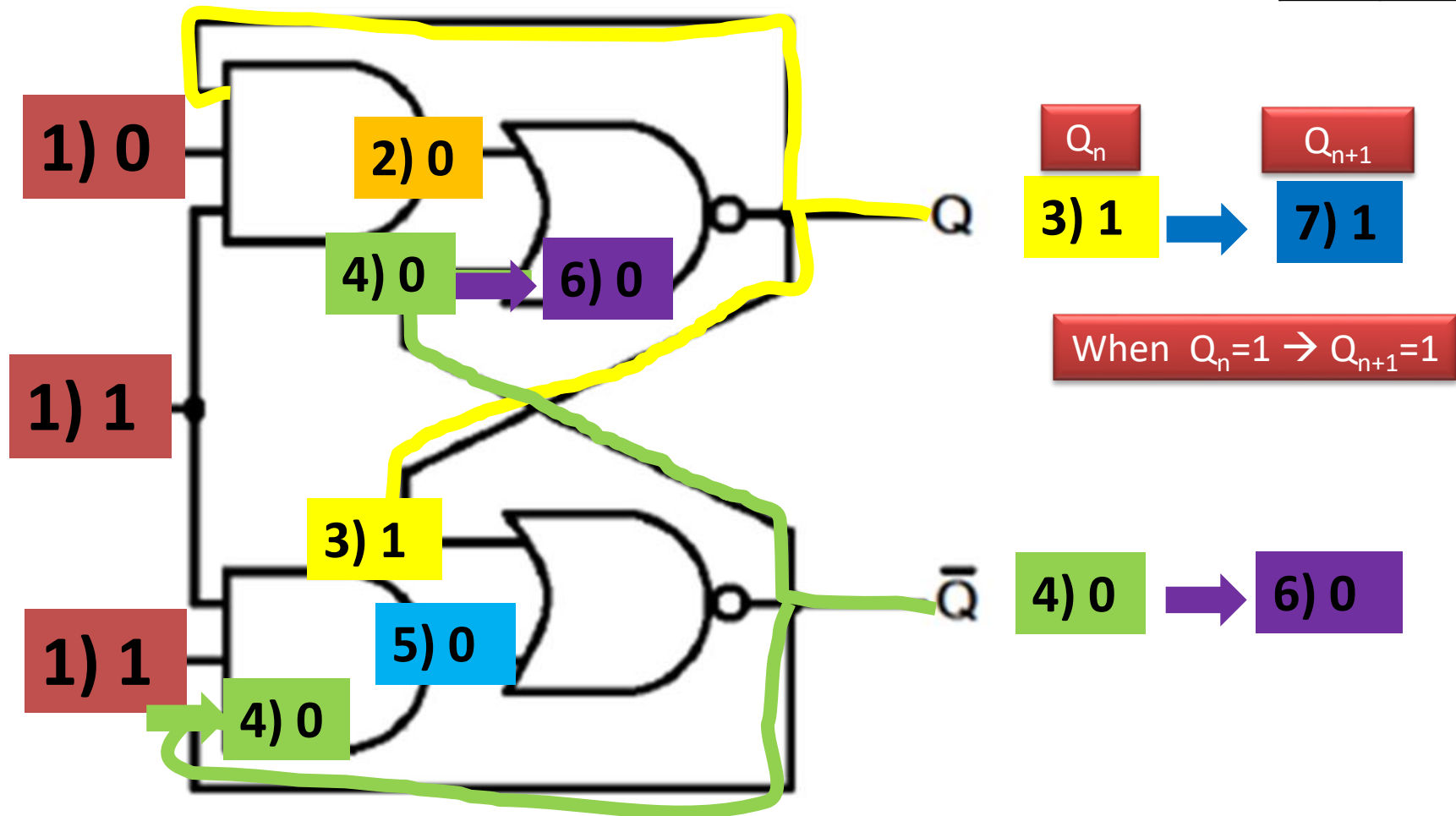


# J=1, K=1 (Case I: Q=0)

		NOR
0	0	1
0	1	0
1	0	0
1	1	0

 
 


 When  $Q_n=0 \rightarrow Q_{n+1}=1$   
(Toggle)




# J=1, K=1 (Case II: Q=1)



		NOR
0	0	1
0	1	0
1	0	0
1	1	0

  

 When  $Q_n = 1 \rightarrow Q_{n+1} = 0$   
(Toggle)



# T Flip-Flops

  

CLK	T	$Q_{n+1}$
1	0	Memory, Toggle
1	1	

SR Latch  $\rightarrow$  D Latch

2 \* D Latch  $\rightarrow$  D FF

JK FF  $\rightarrow$  T FF


# Multivibrators

- Change between two digital levels
  - Continuous (free-running)
  - On demand from an external trigger
- Three types:
  1. **Astable (free running): constantly changing states**
  2. **Monostable (one shot): single output for a specific length of time**
  3. Bistable: changes states when triggered and holds state until next trigger




Input

Output




(No input signal)

 

(a)

   

(b)

   


(c)

We need RC charging/discharging knowledge to understand the multi-vibration




# Capacitor Charge and Discharge

- RC circuit charge and discharge curves

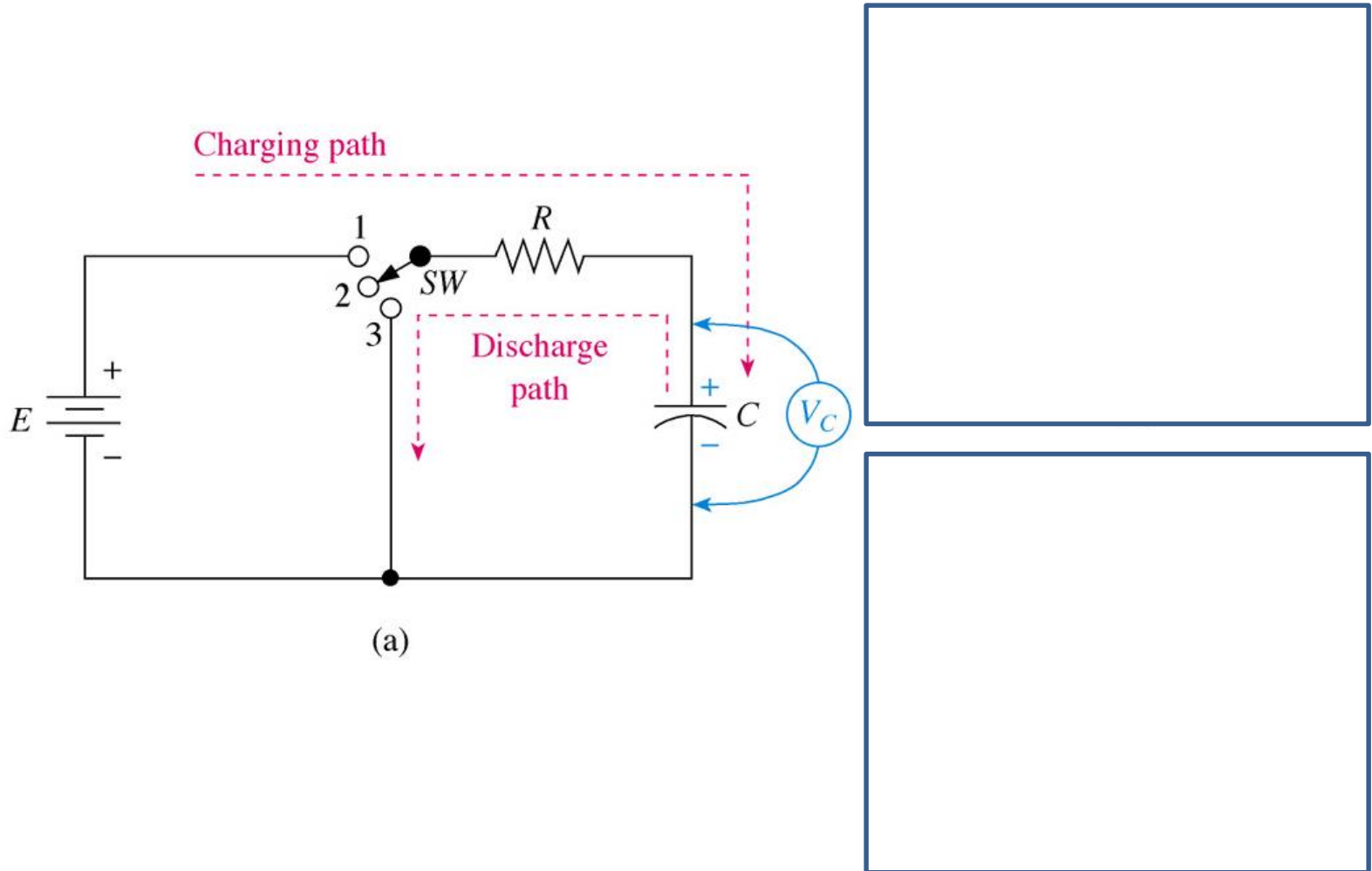
 
# 1. Astable Multivibrators (free-run)



- A Schmitt Inverter and an RC circuit produces a simple astable multivibrator
- We will study waveforms from **Schmitt inverter-based oscillator**; Free-run or auto-run



- The Schmitt trigger was invented by American scientist [Otto H. Schmitt](#) in 1934 while he was a graduate student, later described in his doctoral dissertation (1937) as a "thermionic trigger." It was a direct result of Schmitt's study of the neural impulse propagation in [squid](#) nerves. [wiki]



 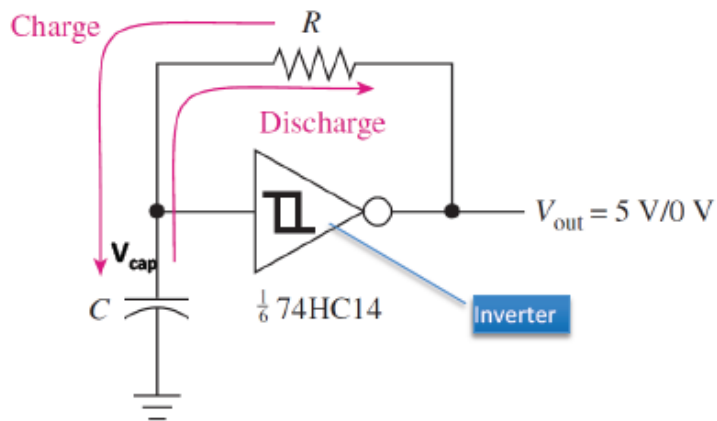
- 1) When the IC supply power is first turned on,  $V_{cap}$  is 0V, so  $V_{out}$  will be HIGH (inverter)
- 2) The capacitor will start charging toward the 5V at  $V_{out}$
- 3) When  $V_{cap}$  reaches the *positive-going threshold* ( $V_{T+}$ ) of the Schmitt trigger, the output of the trigger will change to a LOW
- 4) When  $V_{out}$  is near 0V, the capacitor will start discharging.
- 5) When  $V_{cap}$  drops below the *negative-going threshold* ( $V_{T-}$ ), the output of the Schmitt will change back to a HIGH and repeat the cycle



# 555 Timer Astable Multivibrator implementation

- 555 timer: Very popular general-purpose IC
  - Can be used as a one shot or astable oscillator
  - Also custom designs

# 555 IC Timer Pin Functions

 

The operation and function of the 555 pins are as follows:

Pin 1 (ground): System ground.

Pin 2 (trigger): Input to the lower comparator, which is used to Set the flip-flop. When the voltage at pin 2 crosses from above to below  $\frac{1}{3}V_{CC}$ , the comparator switches to a HIGH, setting the flip-flop.

Pin 3 (output): The output of the 555 is driven by an inverting buffer capable of sinking or sourcing 200 mA. The output voltage levels are dependent on the output current but are approximately  $V_{OH} = V_{CC} - 1.5 \text{ V}$  and  $V_{OL} = 0.1 \text{ V}$ .


Pin 4 (Reset): Active-LOW Reset, which forces  $\overline{Q}$  HIGH and pin 3 (output) LOW.

Pin 5 (control): Used to override the  $\frac{2}{3}V_{CC}$  level, if required. Usually, it is connected to a grounded  $0.01\text{-}\mu\text{F}$  capacitor to bypass noise on the  $V_{CC}$  line.

- Pin 6 (threshold): Input to the upper comparator, which is used to Reset the flip-flop. When the voltage at pin 6 crosses from below to above  $\frac{2}{3}V_{CC}$ , the comparator switches to a HIGH, resetting the flip-flop.
- Pin 7 (discharge): Connected to the open collector of the *NPN* transistor. It is used to short pin 7 to ground when  $\overline{Q}$  is HIGH (pin 3 LOW), which will discharge the external capacitor.
- Pin 8 ( $V_{CC}$ ): Supply voltage.  $V_{CC}$  can range from 4.5 to 18 V.



# Astable 555 IC Timer Block Diagram

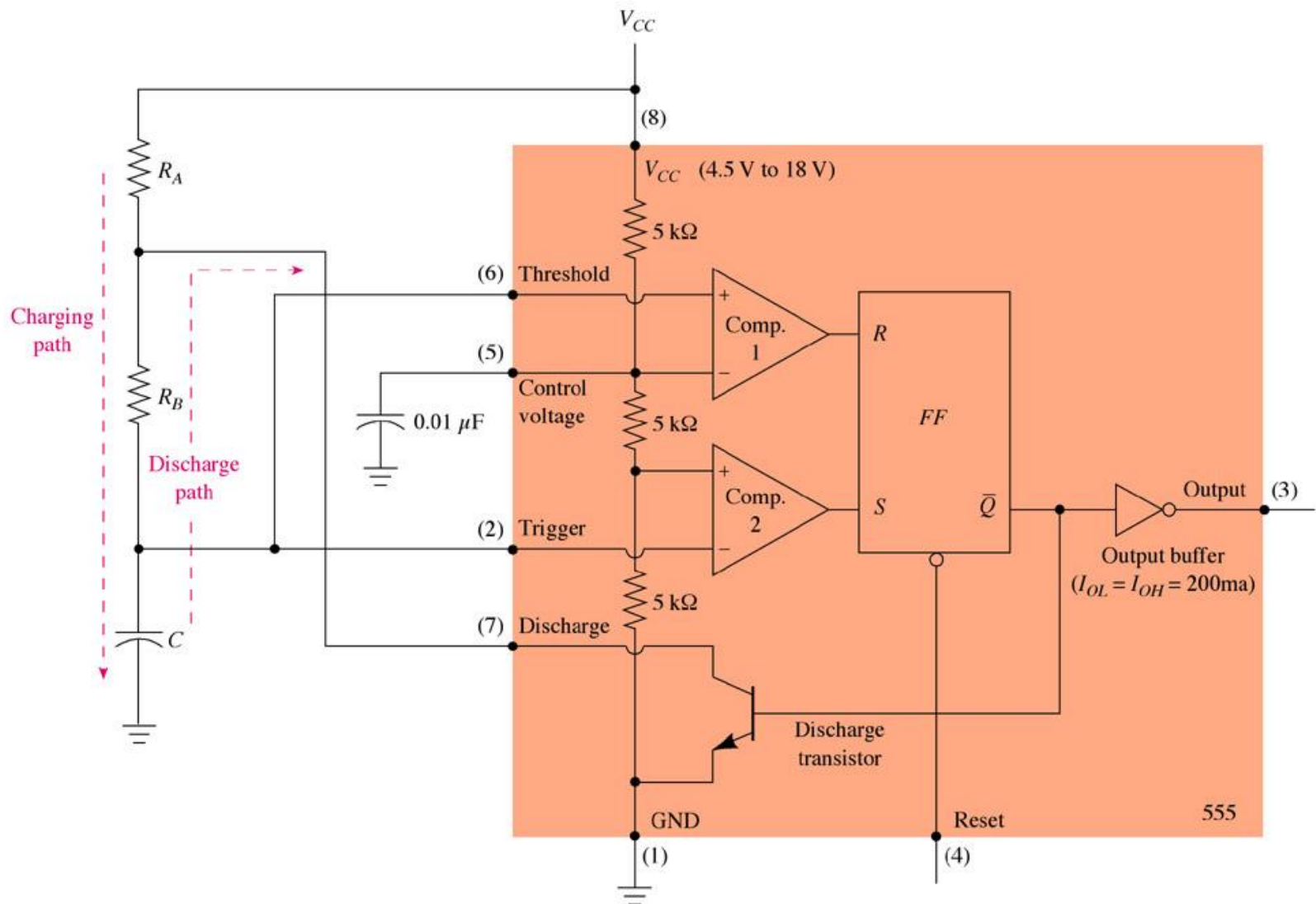


As we are learning this chip (555timer), we have to learn how this chip works


This chip basically consists of 5 components

- 3 internal 5k resistors (555?)
- Two comparators
- One SR flip-flop
- One transistor (BJT- Source/Drain/Gate: on-off is determined by voltage between S and G)
- One inverter


# 555 timer

 

 : The 555 timer connected as an astable multivibrator (oscillator).



*Looks very complicated!*

 


To understand this system fully, you will need the following knowledge (background)

1. Capacitor charging/ discharging circuits
2. How a comparator works?
3. SR Flip-flop/Latch (truth table)
4. How a transistor works? How can we turn it on?

Based on all of the above, you should be able to analyze the 555 internal circuits. Timing graphs/truth table for the voltage across the capacitor ( $V_c(t)$ ),  $Q$ , and  $V_{out}$
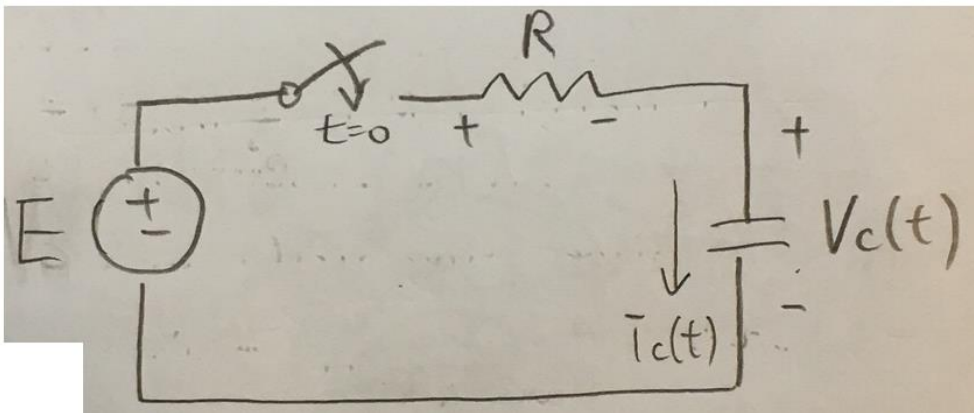
# 1. Capacitor charging/ discharging circuits

- A capacitor (a cap)  $\rightarrow$  capacitance  $C$ 
  - The current through the cap:  $i_c(t) = C \frac{d}{dt} v_c(t)$
- A capacitor charging circuit



Voltage  
across R

$$E = R \cdot \bar{i}_c(t) + V_c(t)$$

$$E = R \cdot C \cdot \frac{d}{dt} V_c(t) + V_c(t) \quad (I)$$

Solve for  $I$  means find  $V_c(t)$

$$(*) \quad V_c(t) = E \left( 1 - e^{-\frac{t}{RC}} \right) \rightarrow \text{plug into } (I)$$

$$(*) \quad V_c(t) = E(1 - e^{-t/RC}) \rightarrow \text{plug into (I)}$$


$$E = R \cdot C \cdot \frac{d}{dt} V_c(t) + V_c(t) \quad (I)$$

$$R \cdot C \cdot \left[ \frac{d}{dt} (E(1 - e^{-t/RC})) \right] + E(1 - e^{-t/RC})$$

$$\cancel{RC} \left( -E \cdot \left( -\frac{1}{RC} \right) \right) e^{-t/RC} + (E - \cancel{E} e^{-t/RC}) = E$$

Done.

 
- A graph for this case, assuming  $V_c(0)=0$  (means initially the cap was discharged)



$$(*) \quad V_c(t) = E(1 - e^{-t/RC})$$

Voltage across a charging capacitor

 - A capacitor discharging circuit,  $V_c(0)=E$ 
  - Means initially the cap was charged.



$$V_c(t) + R \cdot \bar{i}_c(t) = 0$$

$$\boxed{V_c(t) + R \cdot C \cdot \frac{d}{dt} V_c(t) = 0} \quad \textcircled{I}$$

Solve for II means find  $V_c(t)$

$$\textcircled{\star} \boxed{V_c(t) = E \cdot e^{-t/CR}}$$

Plug this into II to confirm the answer




$$\boxed{V_c(t) + R \cdot C \cdot \frac{d}{dt} V_c(t) = 0} \quad \textcircled{\text{II}}$$

$$\textcircled{\star} \boxed{V_c(t) = E \cdot e^{-t/CR}}$$



$$\begin{aligned} & E \cdot e^{-t/CR} + R \cdot C \cdot \frac{d}{dt} (E \cdot e^{-t/CR}) \\ &= E \cdot e^{-t/CR} + R \cdot C \cdot \left(-\frac{1}{RC}\right) \cdot E \cdot e^{-t/CR} = 0 \quad // \text{ proof } (\checkmark) \end{aligned}$$

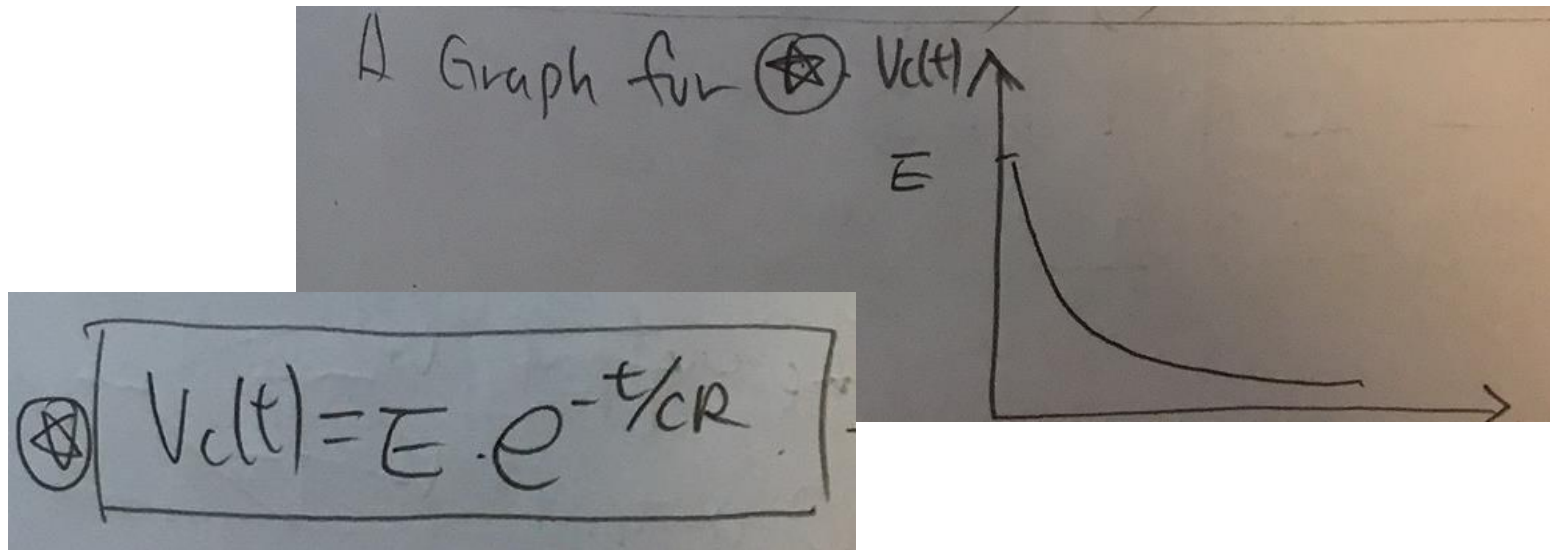- A graph for this case (initially the cap was fully charged with  $E$  [V])



Voltage across a discharging capacitor

  
- If a circuit has a pattern (charging  $\rightarrow$  discharging  $\rightarrow$  charging  $\rightarrow$  discharging....)
- $V_c(t)$  will look like this (assuming that it was discharged initially)





 
# 555 Timer Astable Time Durations

- $t_{LO} = 0.693R_B C$
- $t_{HI} = 0.693(R_A + R_B)C$



## 2. Comparators

 


Keep comparing  $V_-$  and  $V_+$

$$\begin{aligned} \text{If } V_+ &\geq V_- \Rightarrow 1 \\ \text{If } V_+ &< V_- \Rightarrow 0 \end{aligned}$$


### 3. SR Latch

S	R	Q
0	0	Unchange
1	0	1
0	1	0
1	1	no use


# 555 timer circuits

 

 
Let's investigate the path  $0 \rightarrow 1$   
 The cap was initially discharged  
 $V_c(0)=0$







 


 If  $V_+ \geq V_- \Rightarrow 1$   
 If  $V_+ < V_- \Rightarrow 0$



S	R	Q
0	0	Unchange
1	0	1
0	1	0
1	1	nouse

t	Comp	+	-	Vc(t)
0				0
				$\frac{1}{3}V_{DD}$
				$\frac{1}{2}V_{DD}$
1				$\frac{2}{3}V_{DD}$

   

$T \rightarrow$  period.


You can control  $T = \frac{1}{f}$   
by means of  $R_A$ ,  $R_B$ , and  $C$ .  
External.

$\hookrightarrow R = \tau$  // Time constant [sec].

Unit  $\frac{\cancel{\text{Volt}}}{\text{Amp}} \times \frac{\text{Charge}}{\cancel{\text{Volt}}}$   
 $V = IR$   
 $R = V/I$   
 $Q = CV$

$$= \frac{\text{Sec}}{\text{Charge}} \times \text{Charge} = \text{Sec} //$$
 
$$I = \frac{\Delta Q}{\Delta t} \left( \frac{1}{I} \right)$$



$$T = t_L + t_H$$

$$\frac{1}{T} = f = \frac{1.44}{(R_1 + 2R_2)C}$$

$$t_H = 0.7(R_1 + R_2)C, \quad t_L = 0.7R_2C$$


$$\text{Duty cycle} = \frac{t_H}{T} = \left( \frac{R_1 + R_2}{R_1 + 2R_2} \right) \times 100\%$$

Since C charges through  $R_A$  and  $R_B$  and discharges through only  $R_B$ :

- The duty cycles approaching a minimum of 50% can be achieved if  $R_B \gg R_A$
- If that happens the charging and discharging times are approximately equal
 
## 2. Monostable Multivibrators (one-shot)


- Also called as “one-shot”
  - Has one stable state ( $Q=\text{LOW}$ ,  $Q'=\text{HIGH}$ )
  - Outputs change state for a specific length of time ( $t_w$ ) when  $A'$  is triggered (negative edge)



# IC Non-retiriggerable Monostable Multivibrators

- **74121**
  - Connect RC components for proper pulse width
  - Two active-LOW trigger inputs
  - One active-HIGH trigger input
- $t_w = R_{ext} C_{ext} \ln 2 = R_{ext} C_{ext} 0.693$

- 74121 block diagram and function table

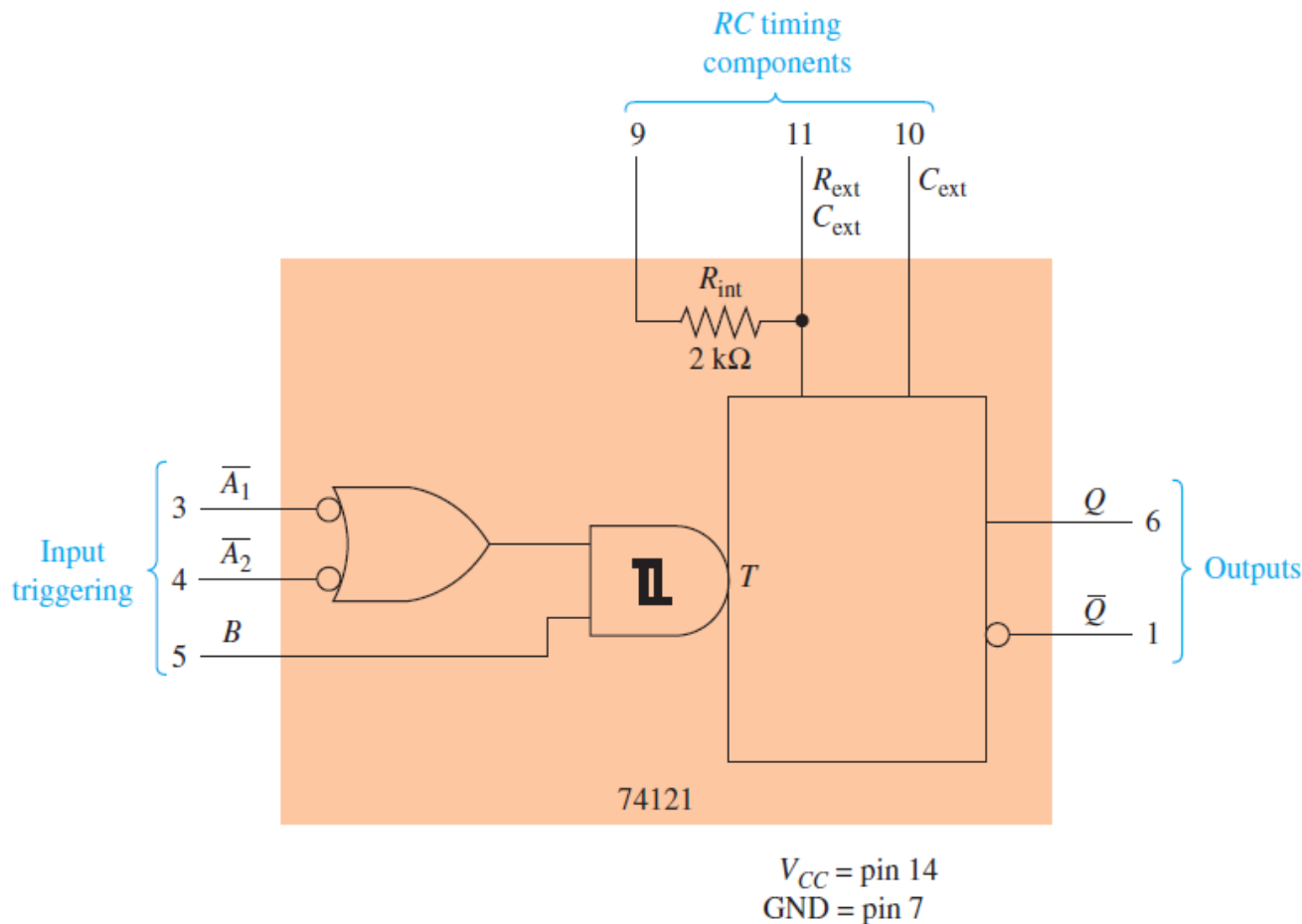

Inputs			Outputs	
$\bar{A}_1$	$\bar{A}_2$	$B$	$Q$	$\bar{Q}$
L	X	H	L	H
X	L	H	L	H
X	X	L	L	H
H	H	X	L	H
H	↓	H	⌋⌋⌋	⌋⌋⌋
↓	H	H	⌋⌋⌋	⌋⌋⌋
↓	↓	H	⌋⌋⌋	⌋⌋⌋
L	X	↑	⌋⌋⌋	⌋⌋⌋
X	L	↑	⌋⌋⌋	⌋⌋⌋


H = HIGH voltage level  
 L = LOW voltage level  
 X = Don't care  
 ↑ = LOW-to-HIGH transition  
 ↓ = HIGH-to-LOW transition


 
# IC Retriggerable Monostable Multivibrators

- **74123**

- New timing cycle each time new trigger applied




- **74123**

- Dual multivibrator
- Active low reset ( $R_D$ ) which forces Q low
- No internal timing resistor
- Pulse width is determined using, If  $C_{ext}$  is greater than or equal to 1000 pF

$$t_w = 0.28 R_{ext} C_{ext} \left( 1 + \frac{700}{R_{ext}} \right)$$

- $C_{ext} < 1000 \text{ pF}$ , the graph in Figure 14-18 can be used to select components.

- 74123 logic symbol and function table

 

Input			Output	
$R_D$	$\bar{A}$	$B$	$Q$	$\bar{Q}$
L	X	X	L	H
X	H	X	L	H
X	X	L	L	H
H	L	$\uparrow$		
H	$\downarrow$	H		
$\uparrow$	L	H		

H = HIGH voltage level

L = LOW voltage level

X = Don't care

$\uparrow$  = LOW-to-HIGH transition

$\downarrow$  = HIGH-to-LOW transition

= One HIGH-level pulse

= One LOW-level pulse

(b)

Design a circuit using a 74121 to convert a 50-kHz, 80% duty cycle square wave to a 50-kHz, 35% duty cycle square wave. The structure and connection of a 74121 chip is given on the figure below.

- (a) Determine  $R_{ext}$  value, if  $C_{ext} = 1nF$

- (b) Determine period of the 50kHz signal ( $t_{period}$ )

- (c) Determine pulse width ( $t_w$ )

$$t_w = t_{period} * \text{duty cycle}$$

# Summary

- Multivibrator circuits are used to produce free-running clock oscillator waveforms or to produce a timed digital level change triggered by an external source.
- Capacitor voltage charging and discharging rates are the most common way to produce predictable time duration for oscillator and timing operations.

- An astable multivibrator is a free-running oscillator whose output oscillates between two voltage levels at a rate determined by an attached RC circuit.
- A monostable multivibrator is used to produce an output pulse that starts when the circuit receives an input trigger and lasts for a length of time dictated by the attached RC circuit.

- The 74121 is an IC monostable multivibrator (non-retriggerable) with two active-LOW and one active-HIGH input trigger sources and an active-HIGH and an active-LOW pulse output terminal.
- Retriggerable monostable multivibrators (74123) allow multiple input triggers to be acknowledged even if the output pulse from the previous trigger had not expired.

- The 555 IC is a general-purpose timer that can be used to make astable and monostable multivibrators and perform any number of other timing functions.



## ECE210 Final Exam

Capacitor charging/discharging curve

$$\Delta v = E(1 - e^{-t/RC})$$

74121 output pulse width  $t_w$

$$t_w = R_{ext} C_{ext} \ln(2)$$

$$t_w = 0.693 R_{ext} C_{ext}$$

555 timer  $t_{HI}$  and  $t_{LO}$

$$t_{LO} = 0.693 R_B C$$

$$t_{HI} = 0.693(R_A + R_B)C$$

## Monostable Multivibrators by 74123

- If  $C_{ext} > 1000$  pF, the output pulse width  $t_w$ :

$$t_w = 0.28 R_{ext} C_{ext} \left(1 + \frac{700}{R_{ext}}\right)$$

- If  $C_{ext} \leq 1000$  pF, the output pulse width  $t_w$  can be found the right chart.

