

# Agenda

- Impedance
- Examples

Here is a summary of how a signal is represented in the time and the frequency domains.

$$v(t) = A \cos(\omega t + \phi) \rightarrow$$

$$v(t) = \operatorname{Re}\left\{Ae^{j(\omega t + \phi)}\right\} \rightarrow$$

Time domain

$$\underline{V} = Ae^{j\phi} \rightarrow$$

$$\underline{V} = A \angle \phi \quad (\text{phasor})$$


Frequency domain

# Recap

OK, let's get started  
 $Z=R+jX$ , for R, C, and L
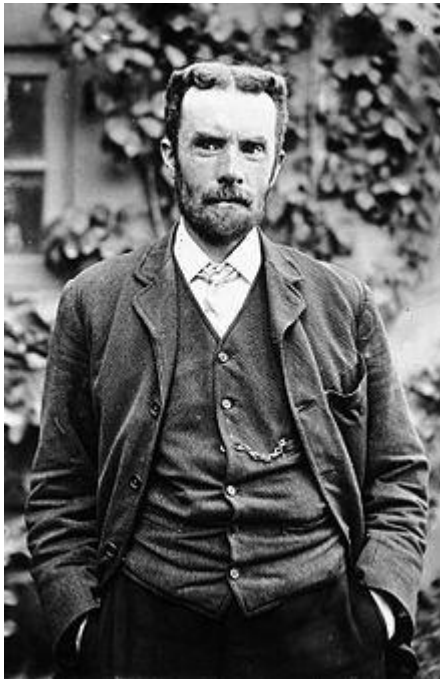
# The electrical impedance ( $Z$ )

- **The measure of the opposition** that a circuit presents to a current when a voltage is applied
- History
  - The term impedance was coined by Oliver Heaviside in July 1886.
  - Arthur Kennelly was the first to represent impedance with complex numbers in 1893.
- Defined as the frequency domain ratio of the voltage to the current.
  - **the voltage–current ratio** for a single complex exponential at a **particular frequency  $\omega$** .



Oliver Heaviside






Arthur Kennelly

# To get the impedance form

- Take a ratio of  $V$  and  $I$  phasors for each component  $R$ ,  $L$ , and  $C$ 
  - $Z=V/I$ : voltage across the component when a unit current is applied




# Resistors

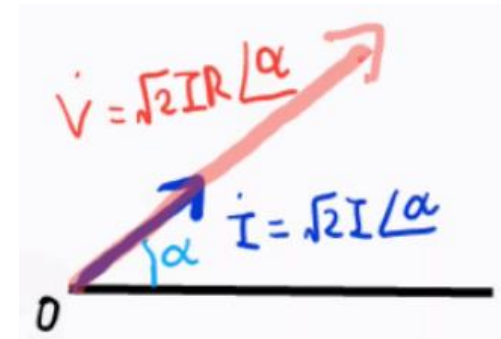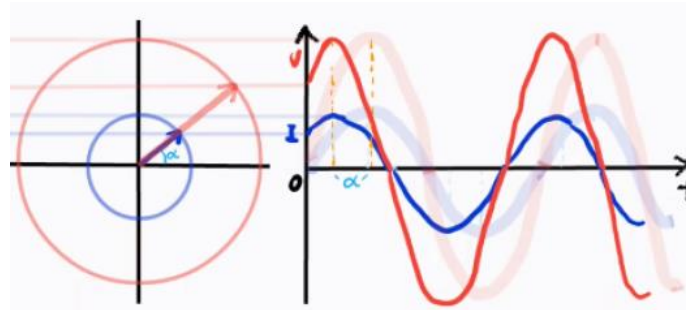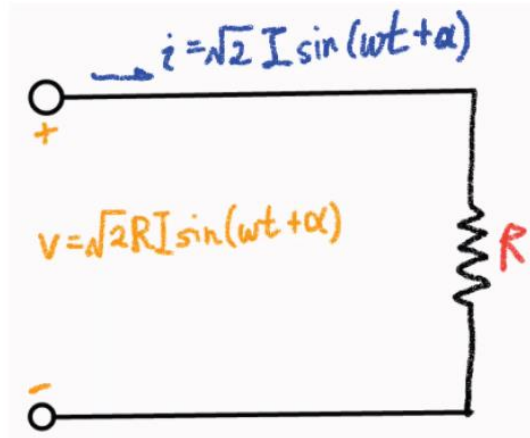

$$Z = \frac{V}{I} = \frac{\sqrt{2} I R \angle \alpha}{\sqrt{2} I \angle \alpha} = R [\Omega]$$






# Inductors

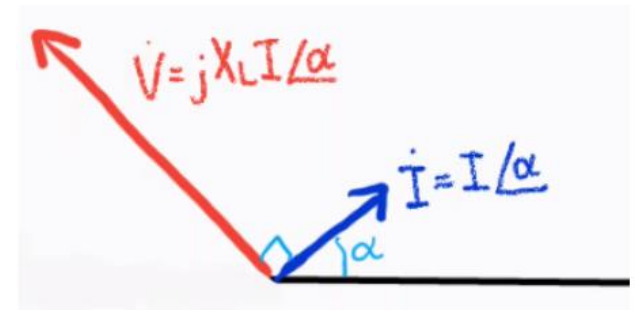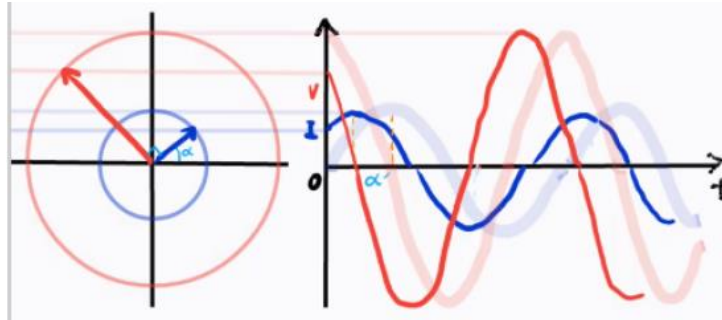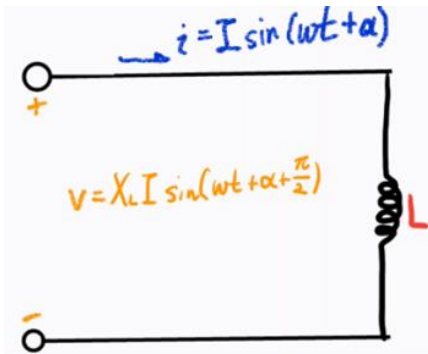

$$Z = \frac{V}{I} = \frac{jX_L I \angle \alpha}{I \angle \alpha} = jX_L = j\omega L [\Omega]$$

Where  $\omega = 2\pi f$

# Capacitors

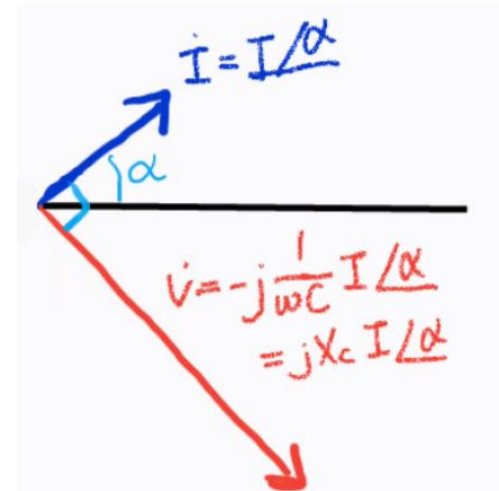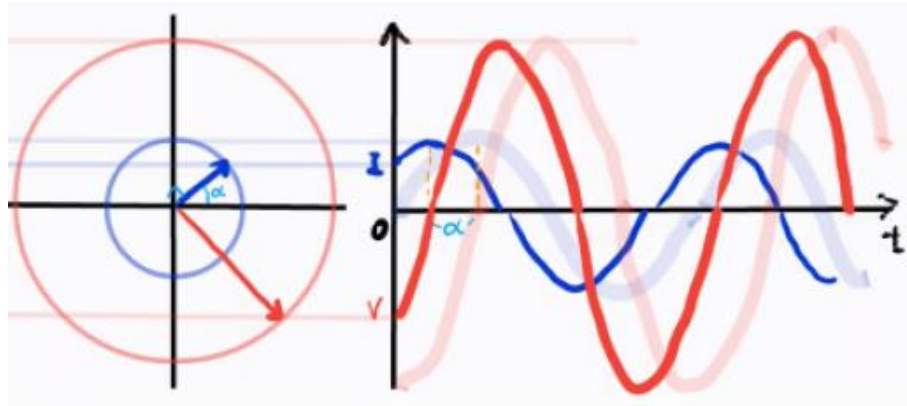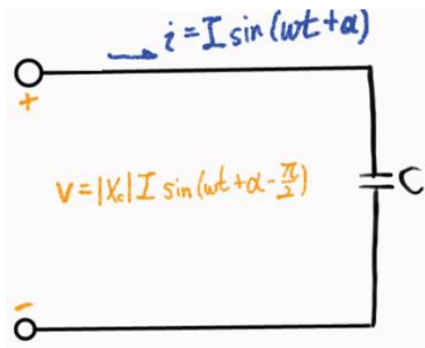

$$Z = \frac{V}{I} = \frac{j X_c I \angle \alpha}{I \angle \alpha} = j X_c = j \frac{-1}{\omega C} = \frac{1}{j \omega C} [\Omega]$$


Where  $\omega = 2\pi f$

# Impedance $Z=R+jX$ [ $\Omega$ ], where

- Series  $Z_{eq}=Z_1+Z_2+Z_3....$ 
  - $\text{Re}\{Z_{eq}\}$ : from resistors,  $\text{Im}\{Z_{eq}\}$ : inductors and caps
- Parallel  $1/Z_{eq}=1/Z_1+1/Z_2+1/Z_3....$ 
  - $\text{Re}\{Z_{eq}\}$  and  $\text{Im}\{Z_{eq}\}$ : combination of R, C, L

Let's do some practice

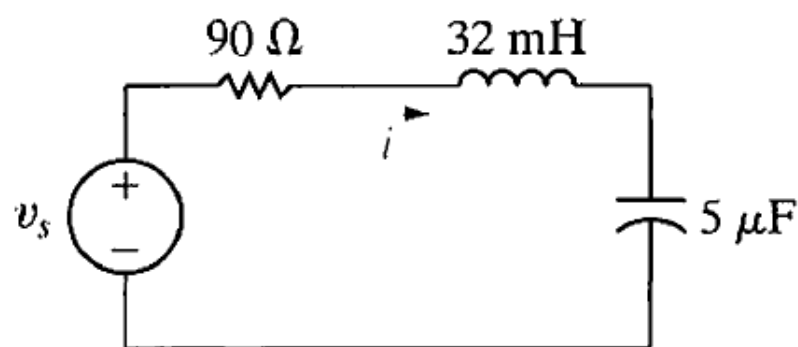A  $90\ \Omega$  resistor, a  $32\ \text{mH}$  inductor, and a  $5\ \mu\text{F}$  capacitor are connected in series across the terminals of a sinusoidal voltage source, as shown in Fig. 9.15. The steady-state expression for the source voltage  $v_s$  is  $750 \cos(5000t + 30^\circ)\ \text{V}$ .




- Construct the frequency-domain equivalent circuit.
- Calculate the steady-state current  $i$  by the phasor method.

$$Z_L = j\omega L = j(5000)(32 \times 10^{-3}) = j160 \, \Omega,$$

$$Z_C = j \frac{-1}{\omega C} = -j \frac{10^6}{(5000)(5)} = -j40 \, \Omega.$$

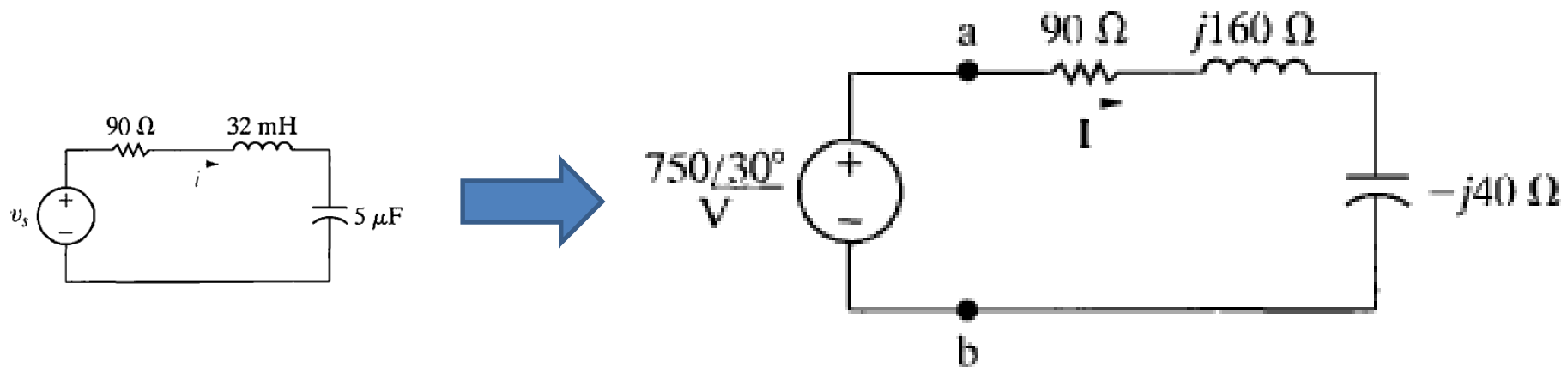
$$\mathbf{V}_s = 750 \angle 30^\circ \text{ V}.$$



$$\begin{aligned} Z_{ab} &= 90 + j160 - j40 \\ &= 90 + j120 = 150 \angle 53.13^\circ \, \Omega. \end{aligned}$$

$$\mathbf{I} = \frac{750 \angle 30^\circ}{150 \angle 53.13^\circ} = 5 \angle -23.13^\circ \text{ A}.$$
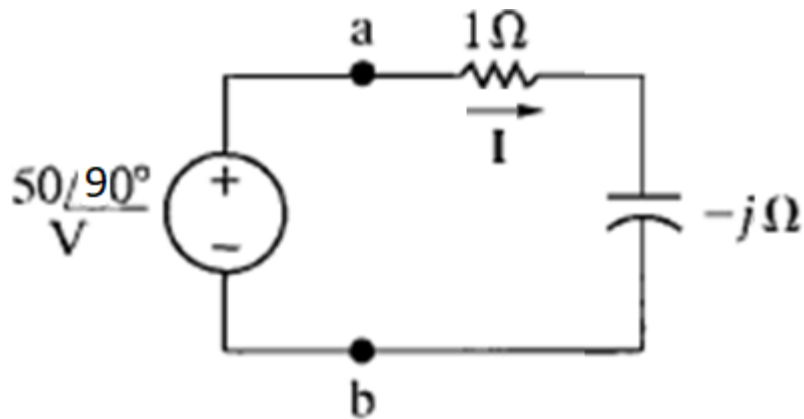
$$i = 5 \cos(5000t - 23.13^\circ) \text{ A}.$$



Compute  $i(t)$  when  
 $\omega=1$  [rad/sec]


$$\begin{aligned} \frac{V}{Z} &= I = \frac{50\angle 90^\circ}{1-j} \\ &= \frac{50\angle 90^\circ}{\sqrt{1^2 + (-1)^2} \tan^{-1} \frac{-1}{1}} \\ &= \frac{50\angle 90^\circ}{\sqrt{2} \angle -45^\circ} = 25\sqrt{2} (\angle 90^\circ - \angle -45^\circ) \\ &= 25\sqrt{2} \angle 135^\circ \\ &= -25\sqrt{2} \angle (135^\circ - 180^\circ) \\ &= -25\sqrt{2} \angle -45^\circ \end{aligned}$$

$$\begin{aligned} \angle 135^\circ &= e^{j135} = \cos 135^\circ + j \sin 135^\circ \\ &= -\frac{1}{\sqrt{2}} + j \frac{1}{\sqrt{2}} \end{aligned}$$

$$\begin{aligned} \angle -45^\circ &= e^{j-45} = \cos -45^\circ + j -\sin 45^\circ \\ &= \frac{1}{\sqrt{2}} - j \frac{1}{\sqrt{2}} \end{aligned}$$

# Complex circuit impedance Ex.

- Determine the total Z

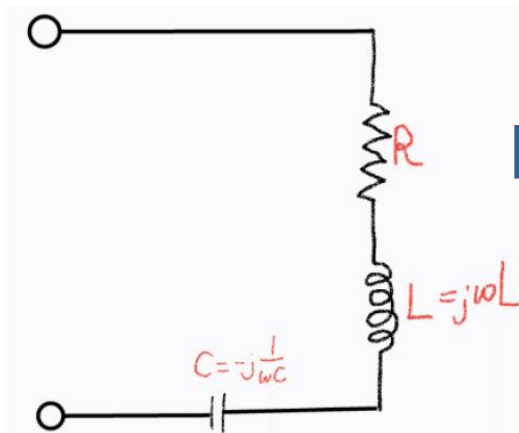


$$Z = R + j \left( \omega L - \frac{1}{\omega C} \right) [\Omega]$$

In phasor form


$$\bar{Z} = |Z|e^{j\theta} \text{ where}$$

$$\theta = \tan^{-1} \frac{\omega L - \frac{1}{\omega C}}{R}$$


$$|Z| = \sqrt{R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2}$$

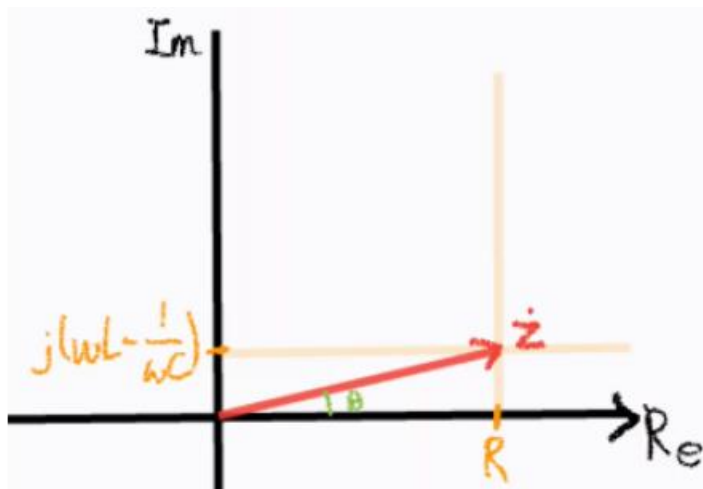

# Determine $v(t)$ (using phasor)

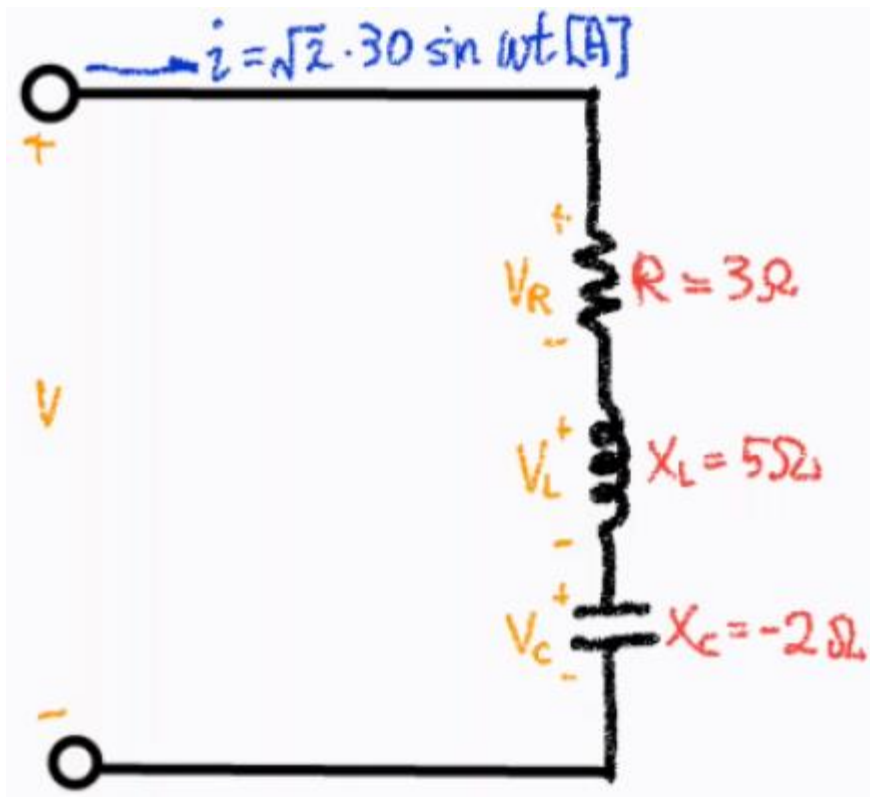


$$Z = 3 + j5 - j2 \\ = 3 + j3 [\Omega]$$

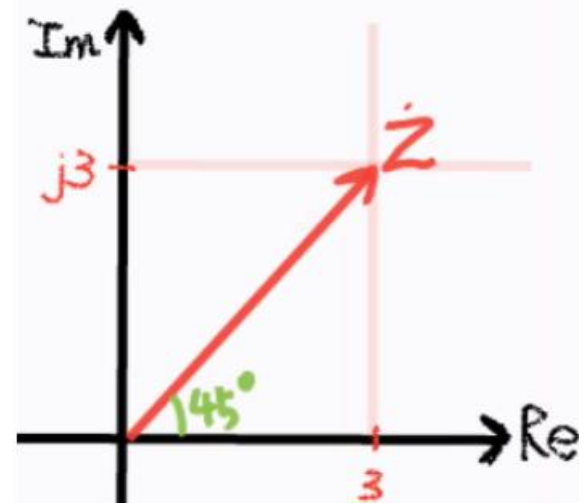

$$|Z| = \sqrt{3^2 + 3^2} = 3\sqrt{2}$$
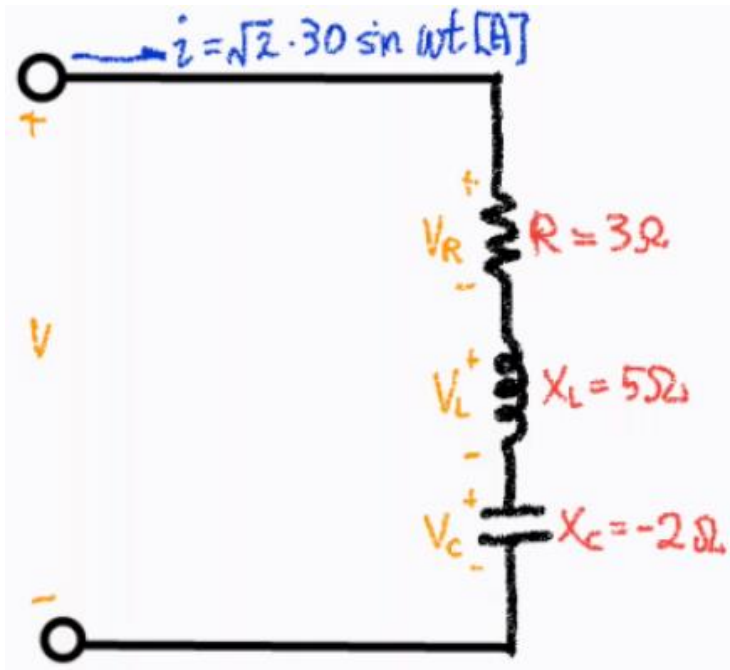
$$\theta = \tan^{-1} \frac{3}{3} = 45^\circ = \frac{\pi}{4} [\text{rad/s}]$$





$$i(t) = \sqrt{2} \cdot 30 \sin \omega t [A]$$

$$I = 30\sqrt{2}e^{-j\frac{\pi}{2}}[A]$$

$$Z = 3\sqrt{2}e^{j\frac{\pi}{4}}[\Omega]$$

Use  $V=IZ$

- $v(t)$ 's magnitude:  $I$ 's mag \*  $Z$ 's mag
- $v(t)$ 's  $\omega$ : same as  $I$
- $v(t)$ 's phase:  $I$ 's phase +  $Z$ 's phase

$$V = 180e^{j(-\frac{\pi}{4})}[V]$$

Therefore

$$\begin{aligned} v(t) &= 180 \cos(\omega t - \pi/4) \\ &= 180 \sin(\omega t + \frac{\pi}{4}) [V] \end{aligned}$$


$$\begin{aligned} \sin \omega t &= \cos(\omega t - 90^\circ) \\ \cos \omega t &= \sin(\omega t + 90^\circ) = -\sin(\omega t - 90^\circ) \end{aligned}$$

# General steps for Circuit Analysis Using Phasors and Impedances

1. Replace the time descriptions of the voltage and current sources with the corresponding phasors.
  - All of the sources must have the same frequency.
  - In general circuit analysis, the standard of the phasor is a cosine function

- 2.** Replace inductances by their complex impedances  $Z_L = j\omega L$ . Replace capacitances by their complex impedances  $Z_C = 1/(j\omega C)$ . Resistances have impedances equal to their resistances.
  
- 3.** Analyze the circuit using any of the circuit analysis techniques, performing the calculations with complex arithmetic.

# Example 1

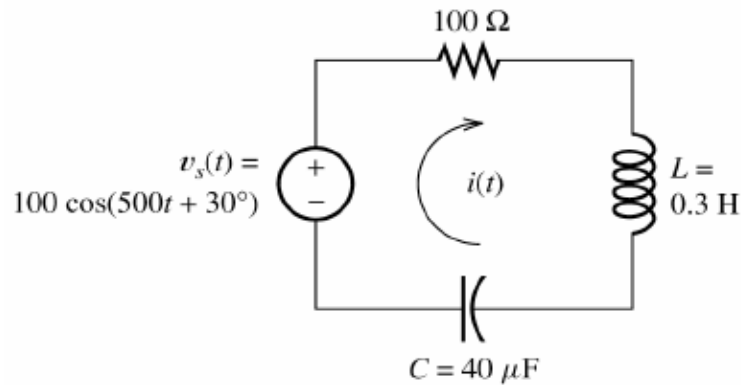

A Phasor form?

Find  $i(t)$ :

$$V_S = 100 \cos(500t + 30^\circ) \rightarrow \mathbf{V}_S = 100 \angle 30^\circ$$

$$Z_L = j\omega L = j(500)(0.3) = j150 \Omega$$


$$Z_C = -j \frac{1}{\omega C} = -j \frac{1}{(500)(40)(10^{-6})} = -j50 \Omega$$

$$\begin{aligned} Z_{eq} &= R + Z_L + Z_C = 100 + j150 - j50 = 100 + j100 \\ &= 141.4 \angle 45^\circ \end{aligned}$$

$$\mathbf{I} = \frac{\mathbf{V}_S}{Z} = \frac{100 \angle 30^\circ}{141.4 \angle 45^\circ} = 0.707 \angle -15^\circ \rightarrow i(t) = 0.707 \cos(500t - 15^\circ)$$
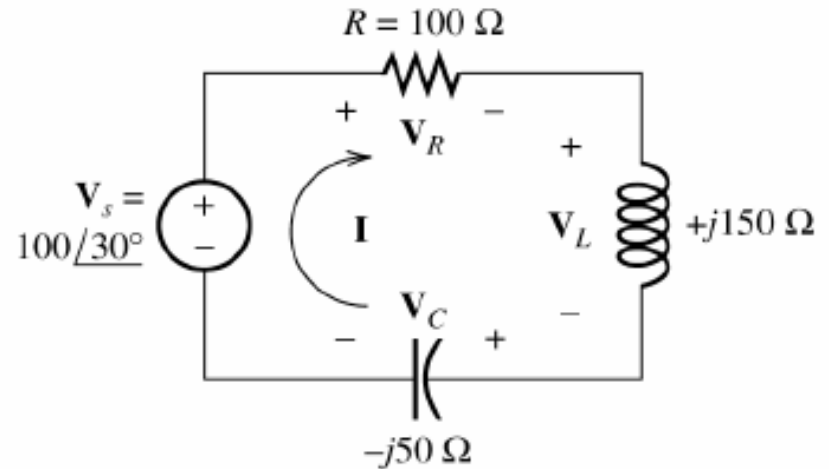
# Example 2

Find the phasor voltage across each element:



$$\mathbf{V}_S = 100\angle 30^\circ$$



$$\mathbf{I}_S = 0.707\angle -15^\circ$$

$$\mathbf{V}_R = R\mathbf{I} = (100)(0.707\angle -15^\circ)$$

$$\mathbf{V}_L = (j\omega L)\mathbf{I} = (\omega L\angle 90^\circ)\mathbf{I} = (\omega L\angle 90^\circ)(0.707\angle -15^\circ) = 106.1\angle 75^\circ$$

$$\mathbf{V}_C = \left(-j\frac{1}{\omega C}\right)\mathbf{I} = \left(\frac{1}{\omega C}\angle -90^\circ\right)\mathbf{I} = (50\angle -90^\circ)(0.707\angle -15^\circ) = 35.4\angle -105^\circ$$

# Example 3

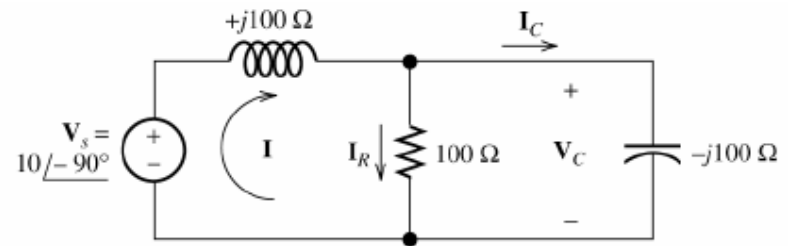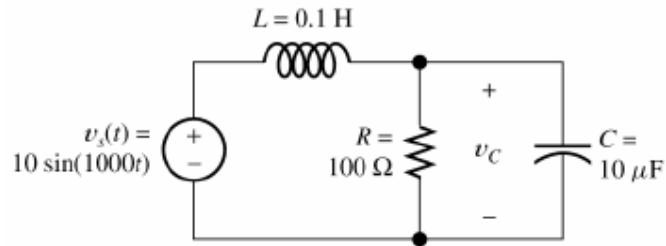

Find the voltage  $v_C(t)$  in steady state:


$$v_s(t) = 10 \sin(1000t) = 10 \cos(1000t - 90) \rightarrow \mathbf{V}_s = 10 \angle -90$$


$$Z_L = j\omega L = j(1000)(0.1) = j100\Omega$$

$$Z_C = -j \frac{1}{\omega C} = -j \frac{1}{(1000)(10 \times 10^{-6})} = -j100\Omega$$

$$Z_{RC} = \frac{1}{\frac{1}{R} + \frac{1}{Z_C}} = \frac{1}{\frac{1}{100} + \frac{1}{-j100}} = \frac{1}{0.01 + j0.01}$$
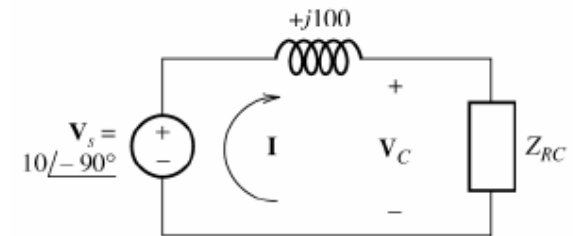
$$= \frac{1 \angle 0}{0.01414 \angle 45} = 70.71 \angle -45 = 50 - j50$$



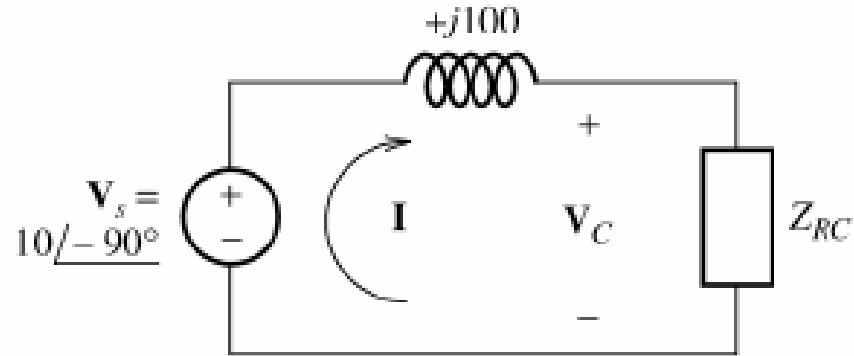

$$\begin{aligned}
 V_C &= \left( \frac{Z_{RC}}{Z_{RC} + Z_L} \right) \mathbf{V}_s = \left( \frac{70.71\angle -45^\circ}{(50 - j50) + j100} \right) (10\angle -90^\circ) \\
 &= \left( \frac{70.71\angle -45^\circ}{50 + j50} \right) (10\angle -90^\circ) \\
 &= \left( \frac{70.71\angle -45^\circ}{70.71\angle 45^\circ} \right) (10\angle -90^\circ) = (1\angle -90^\circ)(10\angle -90^\circ) = 10\angle -180^\circ
 \end{aligned}$$

$$v_C(t) = 10\cos(1000t - 180^\circ) = -10\cos(1000t)$$



# Example 4

Find the phasor current through each element:

$$\mathbf{I} = \frac{\mathbf{V}_s}{Z_L + Z_{RC}} = \frac{10\angle -90^\circ}{j100 + (50 - j50)} = \frac{10\angle -90^\circ}{50 + j50} = \frac{10\angle -90^\circ}{70.71\angle 45^\circ} = 0.1414\angle -135^\circ$$

$$\mathbf{I}_R = \frac{\mathbf{V}_C}{R} = \frac{10\angle -180^\circ}{100} = 0.1\angle -180^\circ$$

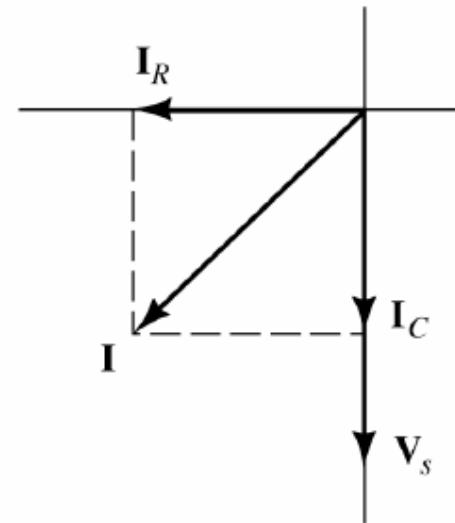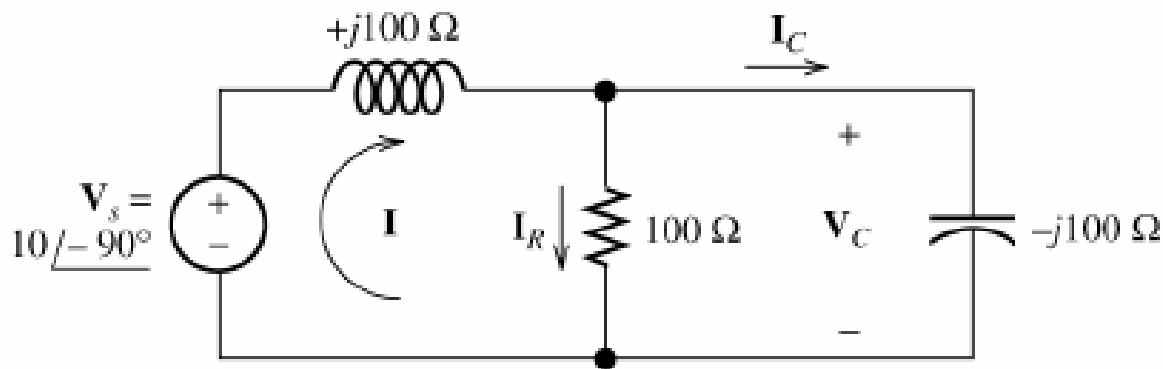
$$\mathbf{I}_C = \frac{\mathbf{V}_C}{Z_C} = \frac{10\angle -180^\circ}{-j100} = \frac{10\angle -180^\circ}{100\angle -90^\circ} = 0.1\angle -90^\circ$$




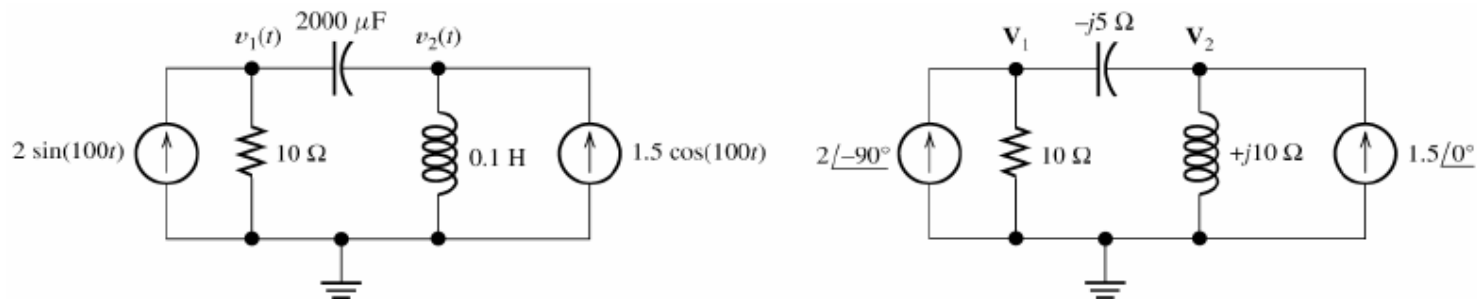
# Example 5

Use the node voltage technique to find  $v_1(t)$ :



*KCL at node 1:*

$$\frac{\mathbf{V}_1}{10} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{-j5} = 2\angle -90^\circ \rightarrow (0.1 + j0.2)\mathbf{V}_1 - j0.2\mathbf{V}_2 = -j2$$

*KCL at node 2:*

$$\frac{\mathbf{V}_2}{j10} = \frac{\mathbf{V}_1 - \mathbf{V}_2}{-j5} + 1.5\angle 0^\circ \rightarrow -j0.2\mathbf{V}_1 + j0.1\mathbf{V}_2 = 1.5$$

$$\begin{aligned}(0.1 + j0.2)\mathbf{V}_1 - j0.2\mathbf{V}_2 &= -j2 \\ -j0.2\mathbf{V}_1 + j0.1\mathbf{V}_2 &= 1.5\end{aligned}$$


$$\begin{aligned}(0.1 + j0.2)\mathbf{V}_1 - j0.2\mathbf{V}_2 &= -j2 \\ -j0.4\mathbf{V}_1 + j0.2\mathbf{V}_2 &= 3\end{aligned}$$

*Adding :*

$$(0.1 - 0.2j)\mathbf{V}_1 = 3 - 2j \rightarrow \mathbf{V}_1 = \frac{3 - 2j}{0.1 - 0.2j} = 14 + 8j = 16.12 \angle 29.74^\circ$$

$$v_1(t) = 16.1 \cos(100t + 29.7^\circ)$$

# Exercise 6

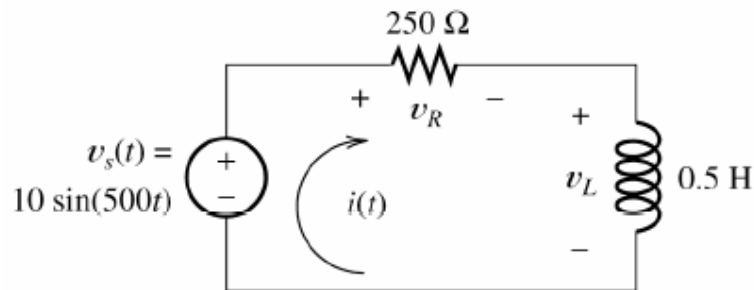

Find  $i(t)$ :

$$v_s(t) = 10 \sin(500t) = 10 \cos(500t - 90^\circ) \rightarrow \mathbf{V}_S = 10 \angle -90^\circ$$

$$Z_R = 250 \Omega$$


$$Z_L = j\omega L = j(500)(0.5) = 250j$$

KVL:

$$\mathbf{I}Z_R + \mathbf{I}Z_L = \mathbf{V}_S \rightarrow \mathbf{I} = \frac{\mathbf{V}_S}{Z_R + Z_L} = \frac{\mathbf{V}_S}{250 + j250} = \frac{10 \angle -90^\circ}{353.6 \angle 45^\circ} = 28.4 \times 10^{-3} \angle -135^\circ$$

$$i(t) = 28.4 \times 10^{-3} \cos(500t - 135^\circ)$$

# Exercise 7

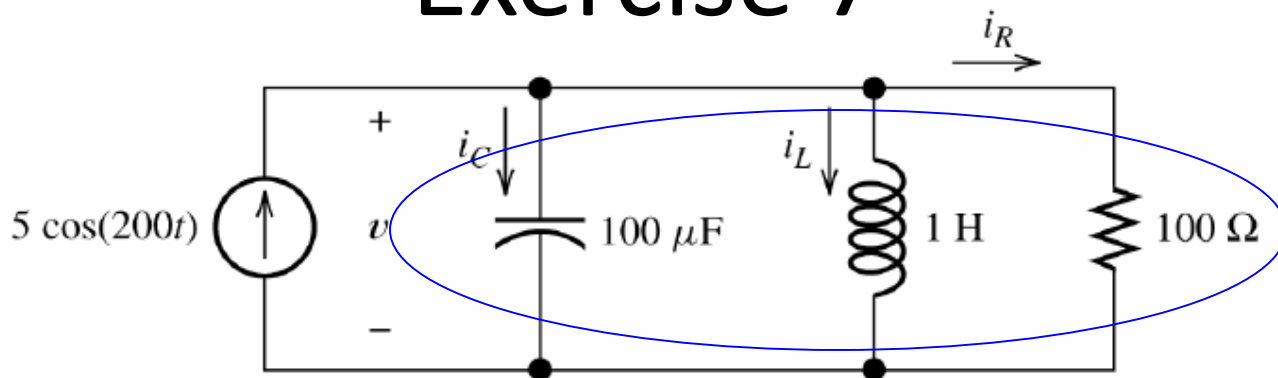

Find the phasor voltage and phasor current through each element:

$$\frac{1}{Z_{eff}} = \frac{1}{Z_C} + \frac{1}{Z_L} + \frac{1}{Z_R}$$


$$Z_C = -j \frac{1}{\omega C} = -j \frac{1}{(200)(100 \times 10^{-6})} = -50j$$

$$Z_L = j\omega L = j(200)(1) = j200$$

$$\frac{1}{Z_{eff}} = \frac{1}{-50j} + \frac{1}{j200} + \frac{1}{100} = \frac{j}{50} - \frac{j}{200} + \frac{1}{100} = \frac{2 + j3}{200}$$

$$Z_{eff} = \frac{200}{2 + j3} = 30.77 - j46.15 = 55.47 \angle -56.31^\circ$$

# Exercise 8

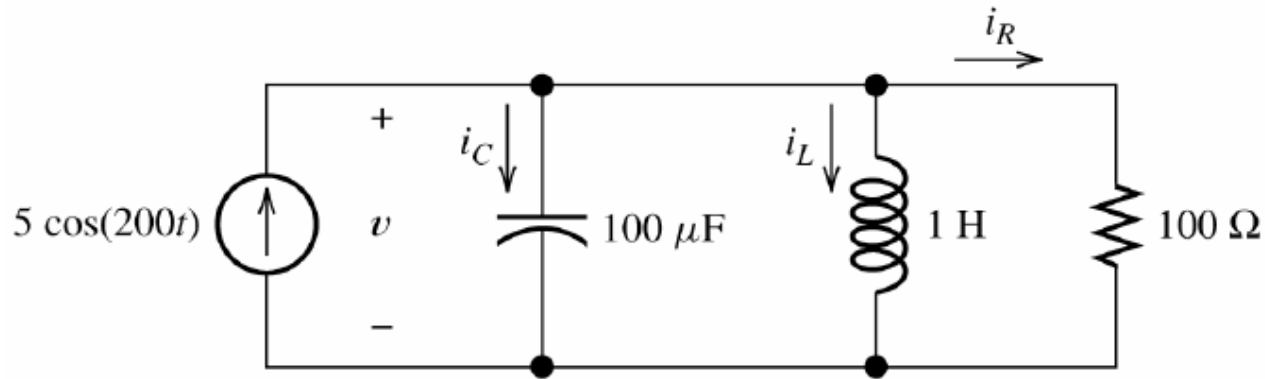

Find the phasor voltage and current through each element:


$$\mathbf{V}_C = \mathbf{V}_L = \mathbf{V}_R = \mathbf{I}Z_{eff} = (5\angle 0^\circ)(55.47\angle -56.31^\circ) = 277.3\angle -56.31^\circ$$

$$\mathbf{I}_C = \frac{\mathbf{V}_C}{Z_C} = \frac{277.3\angle -56.31^\circ}{50\angle -90^\circ} = 5.55\angle 33.69^\circ$$

$$\mathbf{I}_L = \frac{\mathbf{V}_L}{Z_L} = \frac{277.3\angle -56.31^\circ}{200\angle 90^\circ} = 1.39\angle -146.3^\circ$$

$$\mathbf{I}_R = \frac{\mathbf{V}_R}{Z_R} = \frac{277.3\angle -56.31^\circ}{100\angle 0^\circ} = 2.77\angle -56.31^\circ$$

# Exercise 9

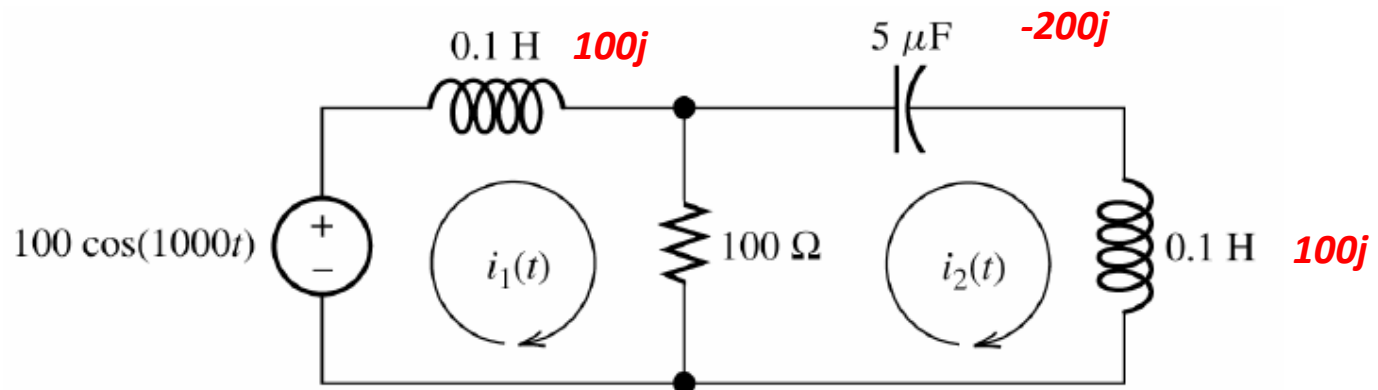

Solve for one of the mesh currents,  $i_1(t)$ :

$$I_1 Z_{L_1} + (I_1 - I_2) Z_R = 100$$

$$I_2 Z_C + I_2 Z_{L_2} = (I_1 - I_2) Z_R$$

$$(100 + 100j)I_1 - 100I_2 = 100$$

$$-100I_1 + (100 - j100)I_2 = 0$$

$$(100 + 100j)I_1 - 100I_2 = 100$$

$$-100I_1 + (100 - j100)I_2 = 0$$

$$(141\angle 45^\circ)I_1 - (100\angle 0^\circ)I_2 = 100\angle 0^\circ$$

$$(-100\angle 0^\circ)I_1 + (141\angle -45^\circ)I_2 = 0$$

$$\begin{aligned} I_1 &= \frac{(100\angle 0^\circ)(141\angle -45^\circ) - (0)(-100\angle 0^\circ)}{(141\angle 45^\circ)(141\angle -45^\circ) - (-100\angle 0^\circ)(-100\angle 0^\circ)} \\ &= \frac{14100\angle -45^\circ}{(141)^2\angle 0^\circ - (100)^2\angle 0^\circ} = \frac{9.97 \times 10^3 - j9.97 \times 10^3}{9881} = 1.009 - j1.009 = \sqrt{2}\angle -45^\circ \end{aligned}$$

$$i_1(t) = 1.41 \cos(1000t - 45^\circ)$$