
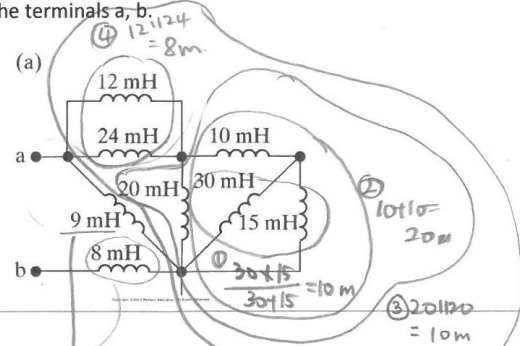


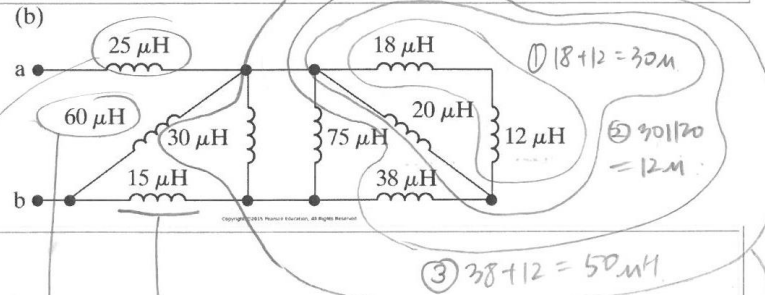7. Assume that the initial energy stored in the inductors (a) and (b) is zero. Find the equivalent inductance with respect to the terminals a, b.



(0.5)

Answer:




(0.5)

Answer:

⑦ $25 + 20 = 45 \text{ μH}$ ans 0.3

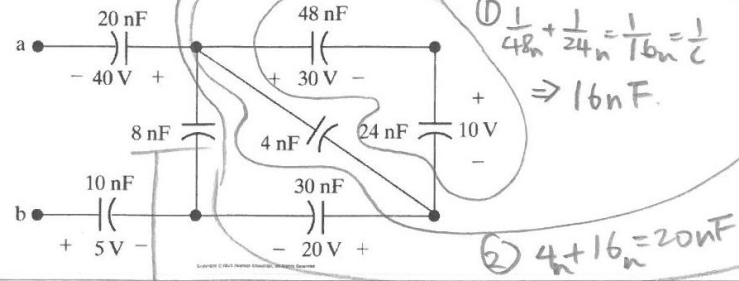
8. Find the equivalent capacitance with respect to the terminals a, b.



$$⑤ \frac{1}{C_{ab}} = \frac{1}{20n} + \frac{1}{20n} + \frac{1}{10n} = \frac{1}{5n}$$

$$\therefore C_{ab} = 5nF \leftarrow \text{answa.} \leftarrow 0.5$$

(1)

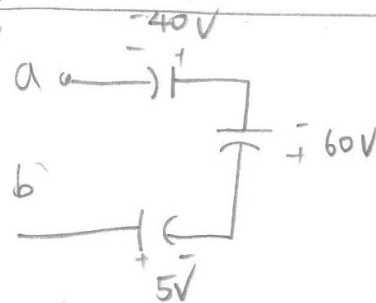

No need to show

Equivalent capacitance at terminal a & b is 5nF with an initial voltage drop of 15V.

$$= -40 + 60 + 5 = 15$$


Answer:

Questions

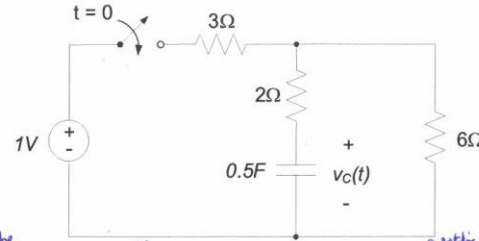1. For the circuit below, determine

"In general": RC circuit.

$$\textcircled{f} V_{Th} = \underbrace{R_{Th}}_{\substack{\text{Tau} \\ \text{a time constant}}} \cdot C \cdot \frac{d}{dt} V_c + 1 \cdot V_c$$




a) $V_c(t), t > 0$, the cap is initially uncharged. (or the circuit was opened for a long time before $t=0$). (steady state)

① Initial condition at $t=0$


$$V_c(0^-) = V_c(0^+) = 0[V] = V_c(0) \quad \because \text{the switch was opened for a long time before } t=0$$

② Final condition at $t=\infty$ (steady state)

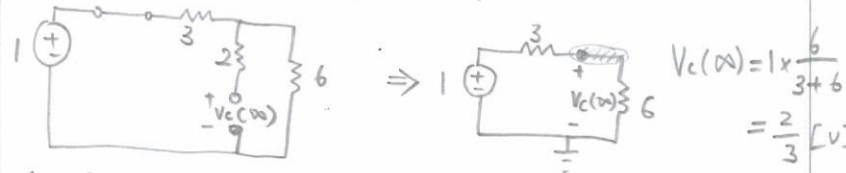\Rightarrow Cap's two plates charging status \Rightarrow Equilibrium!
 \Rightarrow no current $I_c = 0 \Rightarrow$ open circuit



③ $t > 0$

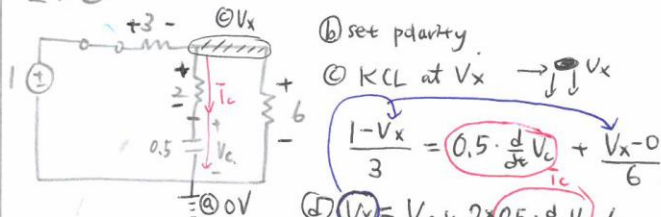

① set polarity.

② KCL at $V_x \rightarrow$

$$\frac{1-V_x}{3} = 0.5 \cdot \frac{d}{dt} V_c + \frac{V_x-0}{6}$$

$$\textcircled{d} V_x = V_c + 2 \times 0.5 \cdot \frac{d}{dt} V_c / 6$$

③ Substitute ③ to ②

$$2 - 2V_c - 2 \frac{d}{dt} V_c = 3 \frac{d}{dt} V_c + V_c + \frac{d}{dt} V_c$$

$$2 = 6 \cdot \frac{d}{dt} V_c + 3V_c \Rightarrow \frac{2}{3} = \frac{d}{dt} V_c + V_c$$

④ $\tau = RC = 2$ (✓)

⑤ Solution form: $V_c(t) = k_1 + k_2 \cdot e^{-t/\tau}$

Answer: ⑥ from ① & ②

$$V_c(0) = 0 = k_1 + k_2 \Rightarrow k_1 = \frac{2}{3}, k_2 = -\frac{2}{3}$$

$$V_c(\infty) = \frac{2}{3} = k_1$$


⑦ $V_c(t) = \frac{2}{3} (1 - e^{-t/2}) [V] \text{ for } t > 0.$

b) $v_c(t), t > 0$ if the capacitance is $1F$

⊗ double
Check τ , steady-state response.

for part (a)

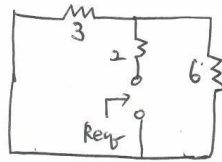Where $\tau = R_{eq} \cdot C_{eq} = R_{th} \cdot C$. looking at V_c terminals.
(capacitor's
 C : our interest V_c)



$$R_{eq} = 2 + (3 \parallel 6) = 4 \Omega$$

$$\tau = 4 \times 0.5 = 2 \text{ (V)}$$

Steady-state response.

$$\frac{d}{dt} v_c(\infty) + \frac{1}{\tau} v_c(\infty) = \frac{1}{3} \Rightarrow v_c(\infty) = \frac{2}{3} \text{ (V)}$$

match with
previous
final answer.

for this question \Rightarrow just changing capacitance to $1F$.

\Rightarrow only affects the time constant & the equivalent resistance remains the same.

$$\therefore \tau = R_{eq} \cdot C = 4 \times 1 = 4 \text{ [sec]}$$

$$\Rightarrow v_c(t) = \frac{2}{3} (1 - e^{-t/4}) \text{ [V] for } t > 0.$$

Answer:


c) $v_c(t), t > 0$ if the capacitance is $0.25F$

$$\tau = R_{eq} \cdot C = 4 \times 0.25 = 1 \text{ [sec]}$$


$$\therefore v_c(t) = \frac{2}{3} (1 - e^{-t}) \text{ [V], } t > 0.$$

Answer:

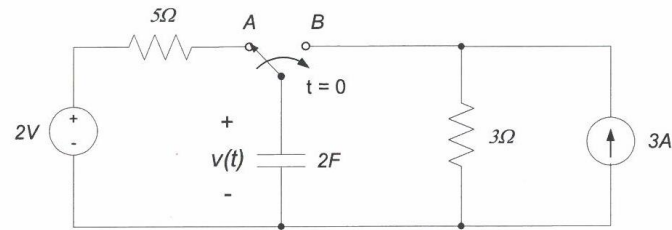3. For the circuit shown, the switch moves from position A to position B at time $t = 0$. Find $v(t)$, $t > 0$.




- ① for $t < 0$, initial condition.

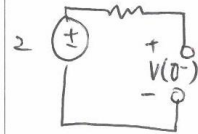


$$V(0^-) = V(0^+) = V(0) = 2 \text{ [V]}$$

- ② for $t \rightarrow \infty$.

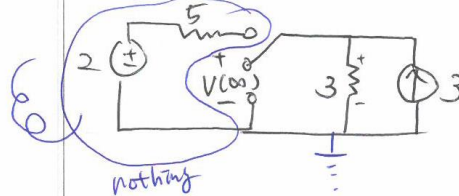

$$V(\infty) = 3 \times 3 = 9 \text{ V.}$$

- ③ $t > 0$.

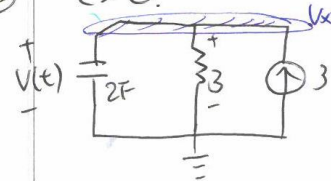

KCL at V_x

$$3 = 2 \cdot \frac{d}{dt} V(t) + \frac{V(t)}{3}$$

$$\Rightarrow 9 = 6 \cdot \frac{d}{dt} V(t) + V(t)$$

$RC = \tau$


- ④ sol form = $V(t) = K_1 + K_2 \cdot e^{-t/\tau} = K_1 + K_2 \cdot e^{-t/6} \text{ [V]}$

- ⑤ from ① & ② $2 = K_1 + K_2 \Rightarrow K_1 = 9, K_2 = -7$

- ⑥ $V(t) = 9 - 7 \cdot e^{-t/6} \text{ [V]}, t > 0$

Answer:

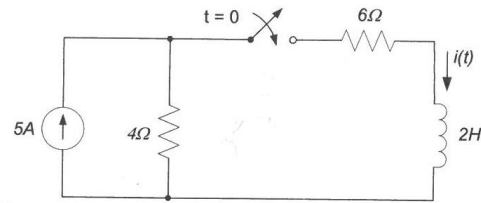4. For the circuit shown, the switch closes at time $t = 0$.



- a) Write the differential equation governing $i(t)$, $t > 0$.

① $t > 0 \Rightarrow$ The switch closes.

② $V_L(t) + 6i(t) = V_x$ ③ $V_L(t) = L \frac{di(t)}{dt}$ ④ rewrite

⑤ KCL at V_x

$$5 = \frac{V_x}{4} + i(t)$$

Where $V_x = V_L(t) + 6i(t)$

where $V_L(t) = L \frac{di(t)}{dt}$

$$5 = \frac{1}{4} \times (2 \cdot \frac{di(t)}{dt} + 6i(t)) + i(t)$$

$$5 = \frac{1}{2} (\frac{di(t)}{dt} + 3i(t)) + i(t)$$

$$10 = \frac{di(t)}{dt} + 3i(t) + 2i(t)$$

$$10 = \frac{di(t)}{dt} + 5i(t) \quad \checkmark$$

Answer:

- b) Determine initial ($t = 0$) and final ($t \rightarrow \infty$) conditions on the current $i(t)$. You may assume that no energy is stored in the inductor before $t = 0$.

① If the switch was opened for a long time $\Rightarrow i(0) = 0 \text{ A}$ for $t = 0$

② final when $t \rightarrow \infty$ $i(\infty) \Rightarrow$ an inductor \Rightarrow short

5 A 4Ω 6Ω $i(\infty)$ \Leftrightarrow 5 A 4Ω 6Ω $i(\infty)$

$$\Rightarrow i(\infty) = 5 \times \frac{4}{4+6} = 2 \text{ A for } t \rightarrow \infty$$

Answer:

- c) Find $i(t)$, $t > 0$.

① sol form: $i(t) = K_1 + K_2 \cdot e^{-t/\tau}$

② from a. $10 = \frac{di(t)}{dt} + 5i(t) \Rightarrow 2 = \frac{1}{5} \frac{di(t)}{dt} + i(t)$

$\tau = L/R$

③ plug in $i(\infty)$, $i(0)$ to ①


$i(\infty) \Rightarrow K_1 + K_2 \cdot e^{-\infty/\tau} = 2 \Rightarrow K_1 = 2$

$i(0) \Rightarrow K_1 + K_2 \cdot e^{-0/\tau} = 0 \Rightarrow K_2 = -2$

④ $\therefore i(t) = 2(1 - e^{-5t}) \text{ [A] for } t > 0$

Answer:

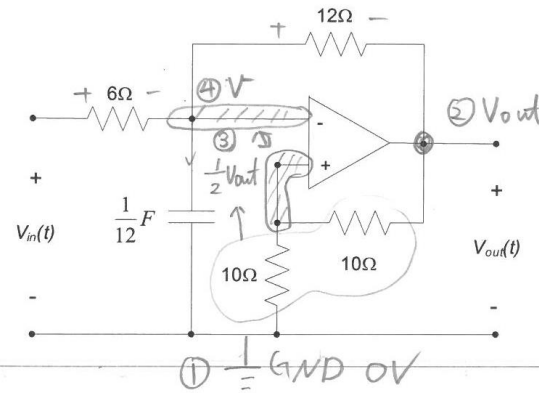5. For the circuit below, determine the differential equation relating $V_{out}(t)$ and $V_{in}(t)$.



⑤ KCL at V^-

$$\left(\frac{V_{in} - \frac{V_{out}}{2}}{6} = \frac{1}{12} \cdot \frac{d}{dt} \left(\frac{1}{2} V_{out} \right) + \frac{\left(\frac{1}{2} V_{out} - V_{out} \right)}{12} \right) \times 12$$

$$⑥ \quad 2 \left(V_{in} - \frac{V_{out}}{2} \right) = \frac{1}{2} \frac{d}{dt} V_{out} + \frac{1}{2} V_{out}$$


$$2V_{in} = V_{out} - \frac{1}{2} V_{out} + \frac{1}{2} \frac{d}{dt} V_{out}$$

$$2V_{in} = \frac{1}{2} V_{out} + \frac{1}{2} \frac{d}{dt} V_{out}$$

$$\underline{4V_{in}(t) = \frac{d}{dt} V_{out}(t) + V_{out}(t)} //$$

Answer:

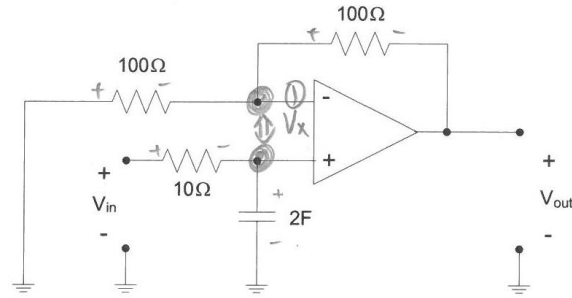6. Determine the differential equations relating V_{out} and V_{in} for the circuit below.



② KCL at V^+

$$\frac{V_{in} - V_x}{10} = 2 \cdot \frac{dV_x}{dt}$$

③ KCL at V^-

$$\frac{0 - V_x}{100} = \frac{V_x - V_{out}}{100}$$

$$\frac{0 - V_x}{100} = \frac{V_x - V_{out}}{100}$$

$$2V_x = V_{out} \Rightarrow V_x = \frac{1}{2} V_{out}$$

④ ③ \rightarrow ②

$$V_{in} - \frac{1}{2} V_{out} = 20 \frac{d}{dt} \left(\frac{1}{2} V_{out} \right)$$


$$V_{in} = \frac{1}{2} V_{out} + 10 \frac{d}{dt} V_{out}$$

or

$$\frac{V_{in}}{10} = \frac{V_{out}}{20} + \frac{d}{dt} V_{out}$$

Answer:

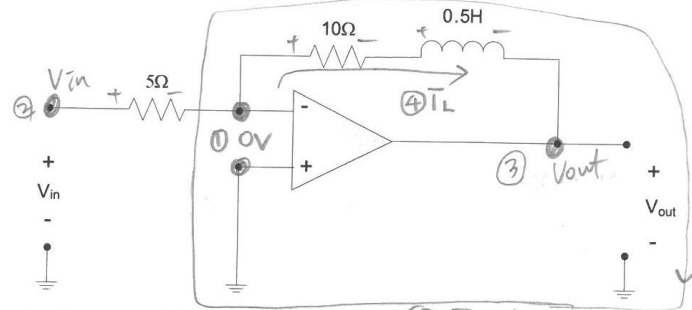8. Determine the differential equations relating V_{out} and V_{in} for the circuit below.




⑥ Feedback loop

⑤ KCL at V^-

$$\frac{V_{in} - 0}{5} = \bar{i}_L \quad \boxed{\bar{i}_L = \frac{V_{in}}{5}}$$

⑦ Redraw the feed-back loop.

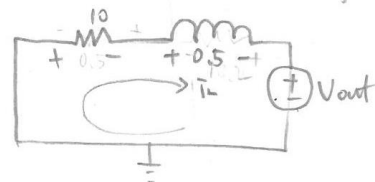

⑧ KVL for i_L loop.

Gain drop

$$0 = 10 \cdot \bar{i}_L + 0.5 \frac{d}{dt} \bar{i}_L + V_{out}$$

⑨ plug \bar{i}_L ⑤ to ⑧

$$-V_{out} = 10 \cdot \frac{V_{in}}{5} + 0.5 \frac{d}{dt} \frac{V_{in}}{5}$$

$$\boxed{-V_{out} = 2V_{in} + 0.1 \frac{d}{dt} V_{in}}$$

Answer:

