

Agenda

- Lecture: Timing in sequential logics
 - Setup/hold time
 - Clock skew

Sequential timing equations (all we need)

1. Hold Time Constraint:

$$t_{\text{hold}} < t_{\text{ccq}} + t_{\text{cd}}$$

Let's go over all
subscripts first.

2. Hold Time Constraint with Skew:

$$t_{\text{hold}} + t_{\text{skew}} < t_{\text{ccq}} + t_{\text{cd}}$$

3. Setup Time Constraint:

$$T_c \geq t_{\text{pcq}} + t_{\text{pd}} + t_{\text{setup}}$$


4. Setup Time Constraint with Skew:

$$T_c \geq t_{\text{pcq}} + t_{\text{pd}} + t_{\text{setup}} + t_{\text{skew}}$$

Recap: timing in combinational logics


Propagation & Contamination Delay

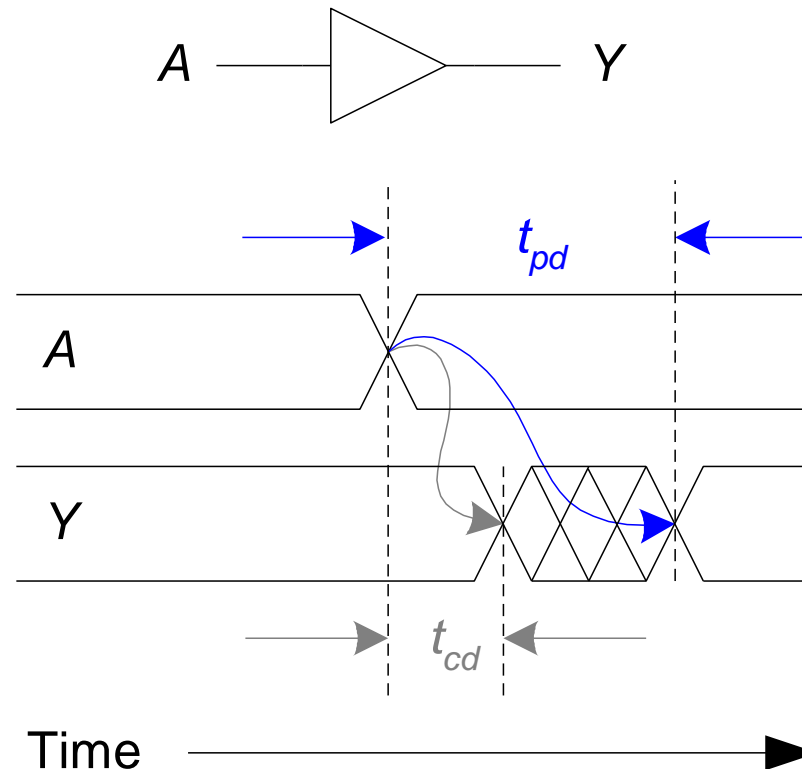- Propagation delay: $t_{pd} =$
- Contamination delay: $t_{cd} =$



Actual signal
arriving time
at outputs

Intro to timing in sequential logics

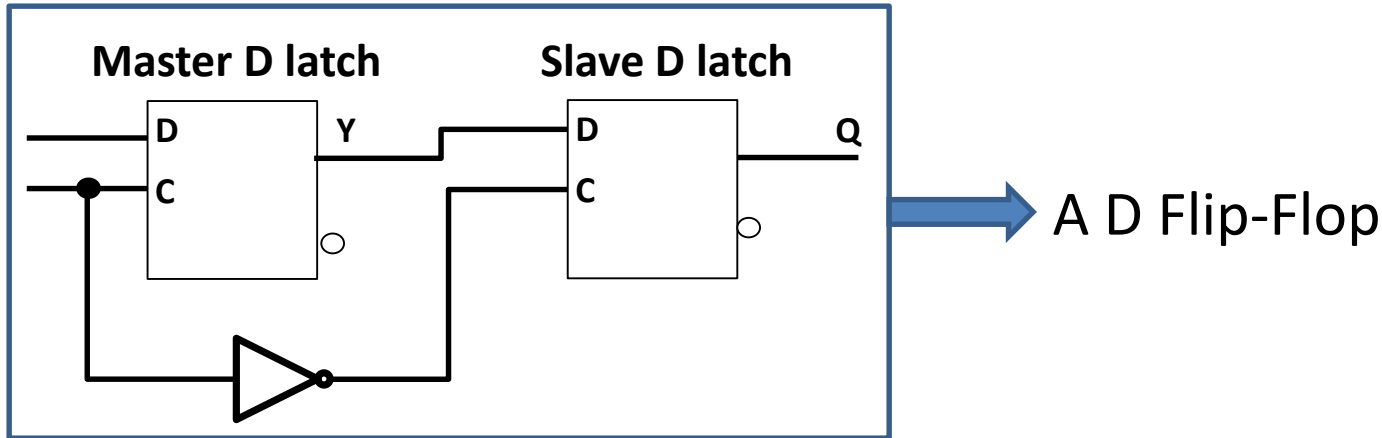

Flip-flop samples D at clock edge

- D must be stable when sampled
- D must be stable around clock edge

If not, metastability can occur

Let's explain this idea in an academic manner


- Describe the situation using terminologies as like we did in combinational logics study; propa—d, combin—d

A big picture of timing analysis in SLs:

- A step by step consideration of
inputs,
outputs,
and clock


Input Timing

 - **Setup time:** t_{setup} = time *before* clock edge data. It must be stable (i.e. not changing, guaranteed to be stable)
- **Hold time:** t_{hold} = time *after* clock edge data. It must be stable (guaranteed to be stable)
- Aperture time (Data required interval): t_a = time *around* clock edge data. It must be stable ($t_a = t_{\text{setup}} + t_{\text{hold}}$)



Output Timing

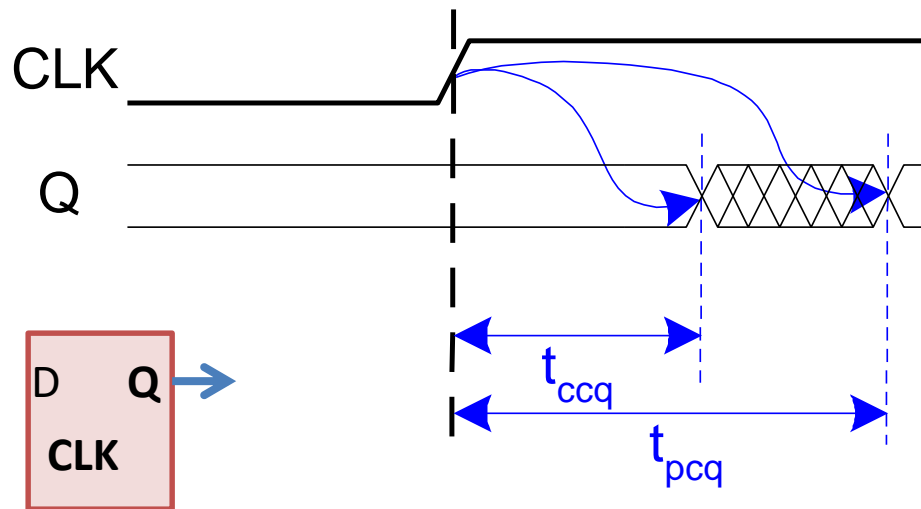
- **Propagation delay, clk to Q:** t_{pcq} = time after clock edge that the output Q is guaranteed to be stable (i.e., to stop changing, maximum t) $\leftrightarrow t_{pd}$ in Comb. logics
- **Contamination delay, clk to Q:** t_{ccq} = time after clock edge that Q might be stable (or not) (i.e., start changing, minimum t) $\leftrightarrow t_{cd}$ in Comb. logics



- Synchronous sequential circuit **inputs** must be stable during aperture (setup and hold) time around clock edge
- Specifically, **inputs** must be stable
 1. at least t_{setup} before the clock edge: setup time constraint
 2. at least until t_{hold} after the clock edge: hold time constraints
 3. 1 and 2 are considered with the clock skew concept

RECAP: cascading two components to analyze
from “OUTPUT” to “INPUT”

A chain of two buffers

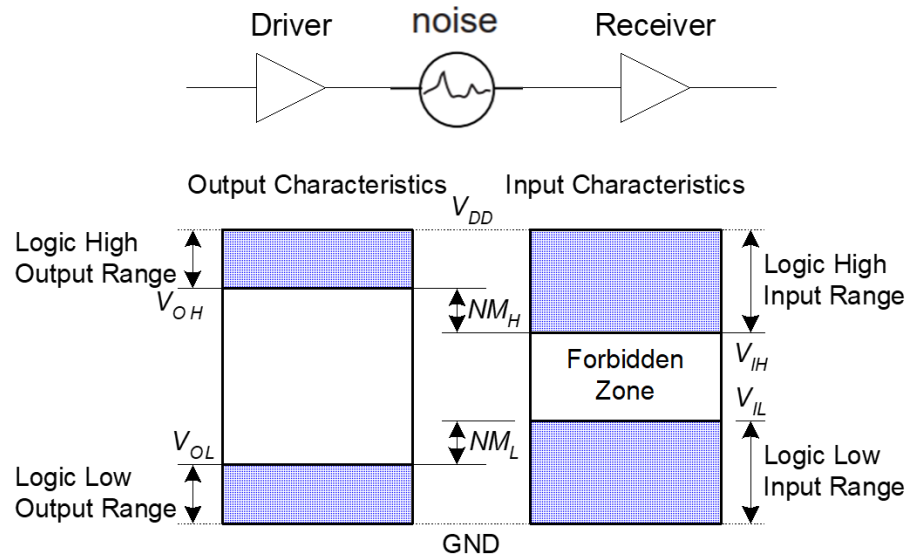


High Noise Margin: $NM_H = V_{OH} - V_{IH}$

Low Noise Margin: $NM_L = V_{IL} - V_{OL}$

Setup Time Constraint

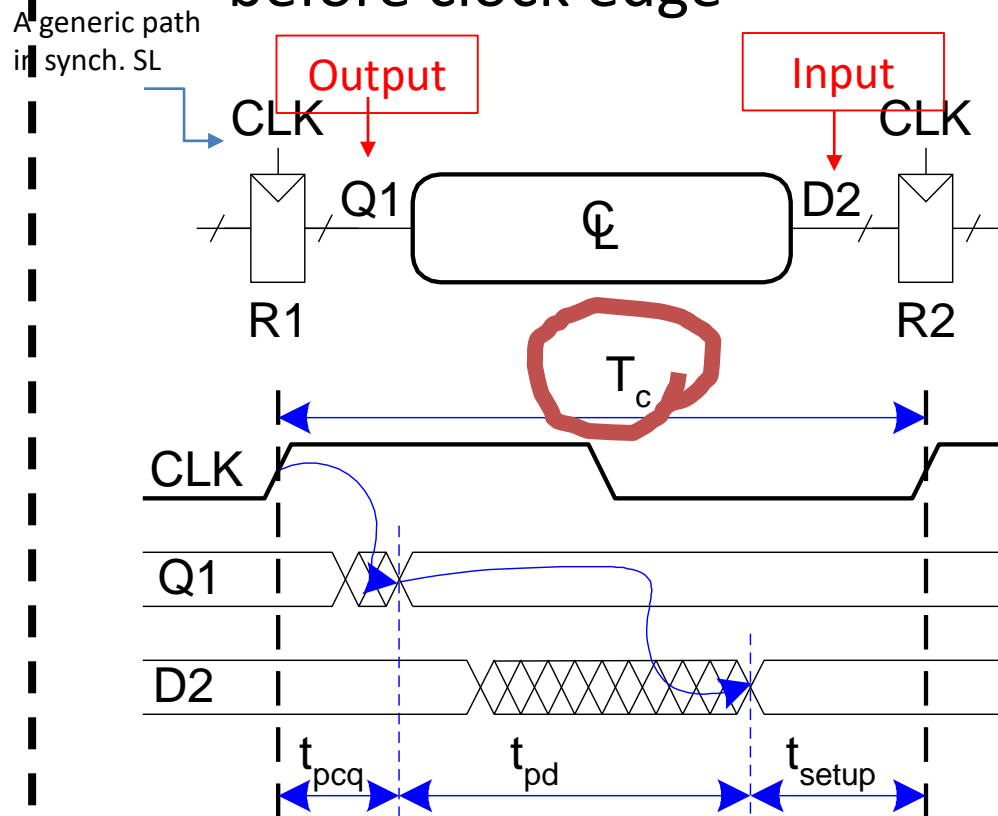- Depends on the **maximum** delay from register R1 through combinational logic to R2
- The **input** to register R2 must be stable at least t_{setup} before clock edge




CLK period must be longer than this

$$T_c \geq t_{pcq} + t_{pd} + t_{\text{setup}}$$

$(t_{pcq} + t_{\text{setup}})$: sequencing overhead

Hold Time Constraint

 - Depends on the **minimum** delay from register R1 through the combinational logic to R2
- After the rising edge of the clock, D2 must not change until t_{hold} and might change as soon as $t_{\text{ccq}} + t_{\text{cd}}$




$$t_{\text{hold}} \stackrel{?}{=} t_{\text{ccq}} + t_{\text{cd}}$$

If you hold previous input (D2) too long, you can't take next output from Q1

 Examples: Timing Analysis,
setup/hold time constraint

Q. Find the minimum clock period (in sec) to work with this circuit. And check if this circuit satisfy hold time constraint.



Timing Characteristics per gate

$$\begin{aligned} t_{ccq} &= 30 \text{ ps} \\ t_{pcq} &= 50 \text{ ps} \\ t_{\text{setup}} &= 60 \text{ ps} \\ t_{\text{hold}} &= 70 \text{ ps} \end{aligned}$$

per gate

$$\begin{aligned} t_{pd} &= 35 \text{ ps} \\ t_{cd} &= 25 \text{ ps} \end{aligned}$$

Consider
entire
CL's

$$\begin{cases} t_{pd} = \\ t_{cd} = \end{cases}$$

Critical path

Shortest pat

Hold time constraint:


$$t_{ccq} + t_{cd} > t_{\text{hold}} ?$$

Setup time constraint:

$$T_c \geq ?$$

Maximum clock frequency to
work with this circuit!

Let's add buffers to the short paths:

 

Timing Characteristics per gate

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

per gate

$$\left[\begin{array}{ll} t_{pd} & = 35 \text{ ps} \\ t_{cd} & = 25 \text{ ps} \end{array} \right.$$

$$t_{pd} = \text{Critical path}$$

$$t_{cd} = \text{Shortest path}$$


Hold time constraint:

$$t_{ccq} + t_{cd} > t_{\text{hold}} ?$$

Setup time constraint:


$$T_c \geq ?$$

Changed or not?

 


Setup/hold time constraints (+) Clock Skew

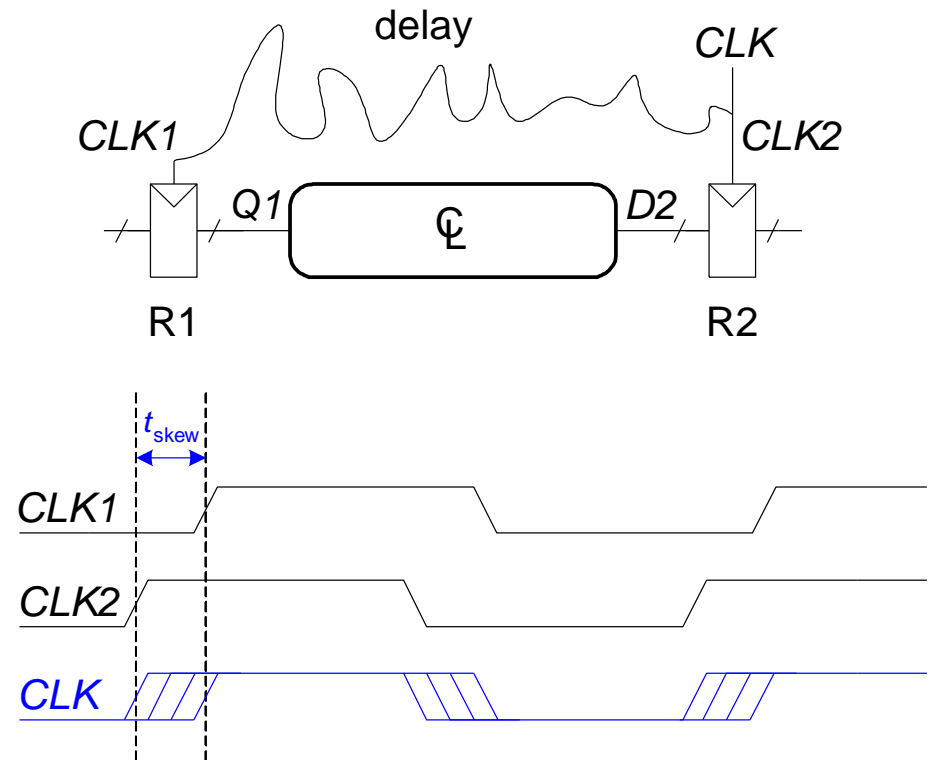- The clock doesn't arrive at all registers at same time
- **Skew**: difference between two clock edges
- Perform **worst case analysis** to guarantee dynamic discipline is not violated for any register – many registers in a system!



Setup Time Constraint with Skew

 - In the worst case, CLK2 is earlier than CLK1




$$T_c \geq ?$$

T_c should be larger than
input/output's undesired effects

Hold Time Constraint with Skew

 - In the worst case, CLK2 is later than CLK1



$$t_{\text{hold}} < t_{ccq} + t_{cd}$$

Which hand-side is for t_{skew} ?
 → clock is a kind of inputs

An example

- A sequential circuit design is shown with its delay parameters:

D-FF clk-to-q propagation delay $t_{pcq} = 18$ ps


D-FF clk-to-q contamination delay $t_{ccq} = 12$ ps

D-FF data setup time $t_s = 14$ ps

D-FF data hold time $t_h = 7$ ps

Table 1: Propagation delay for certain gates

Gate	T_{pd} (ps)	T_{cd} (ps)
2-input NAND	17	11
2-input NOR	27	16
2-input XOR	36	26
NOT	11	6

 

- Calculate the maximum clock frequency for reliable operation assuming there is no clock skew
- How much clock skew can the circuit tolerate before it experiences a hold time violation?

We discussed several equations, which one should we apply for each question?

Summary of sequential timing eqs.

1. Hold Time Constraint:

$$t_{\text{hold}} < t_{\text{ccq}} + t_{\text{cd}}$$

2. Hold Time Constraint with Skew:

$$t_{\text{hold}} + t_{\text{skew}} < t_{\text{ccq}} + t_{\text{cd}}$$

3. Setup Time Constraint:

$$T_c \geq t_{\text{pcq}} + t_{\text{pd}} + t_{\text{setup}}$$

4. Setup Time Constraint with Skew:

$$T_c \geq t_{\text{pcq}} + t_{\text{pd}} + t_{\text{setup}} + t_{\text{skew}}$$

- Calculate the maximum clock frequency for reliable operation assuming there is no clock skew
- How much clock skew can the circuit tolerate before it experiences a hold time violation?

D-FF clk-to-q propagation delay $t_{pcq} = 18$ ps


D-FF clk-to-q contamination delay $t_{ccq} = 12$ ps

D-FF data setup time $t_s = 14$ ps

D-FF data hold time $t_h = 7$ ps

Table 1: Propagation delay for certain gates

Gate	T_{pd} (ps)	T_{cd} (ps)
2-input NAND	17	11
2-input NOR	27	16
2-input XOR	36	26
NOT	11	6

 

- Calculate the maximum clock frequency for reliable operation assuming there is no clock skew
- How much clock skew can the circuit tolerate before it experiences a hold time violation?

ANS