

Questions

1. A sinusoidal current is given by the expression
 $i = 100 \cos(600t + 45^\circ) \text{ mA}$

a) Find f in hertz

0.1

Answer:

$$\omega = 2\pi f = 600 \text{ rad/s} \quad f = \frac{600}{2\pi} = 95.54 \text{ Hz}$$

b) T in milliseconds

0.1

Answer:

$$T = \frac{1}{f} = 10.47 \text{ ms}$$

c) I_m (magnitude)

0.1

Answer:

$$100 \text{ mA}$$

d) $i(0)$

0.1

Answer:

$$i(0) = 100 \cos(45^\circ) = 100 \times \frac{\sqrt{2}}{2} = 70.72 \text{ mA}$$

e) ϕ in degrees and radians

0.1

Answer:

$$45^\circ \Rightarrow \frac{\pi}{4} = 0.7857 \text{ rad}$$

f) The smallest positive value of t at which $i=0$

0.1

Answer:

$$i=0 \text{ when } 600t + 45^\circ = 90^\circ (\because \cos 90^\circ = 0)$$

$$600t + 45^\circ = 90^\circ \Rightarrow 600t = 45^\circ \Rightarrow 600t = 0.7853 \text{ [rad/s]}$$

$$t = 1.308 \text{ m sec}$$

g) The smallest positive value of t at which $di/dt=0$

0.2

Answer:


$$\frac{di}{dt} = -100 \cdot 600 \cdot \sin(600t + 45^\circ) \Rightarrow \bar{i}_{\text{max}} \text{ when } \frac{di}{dt} = 0$$

$$\Rightarrow 600t + 45^\circ = 180^\circ$$

$$\therefore 600t + 45^\circ = 180^\circ$$

$$t = 3.926 \text{ m sec}$$

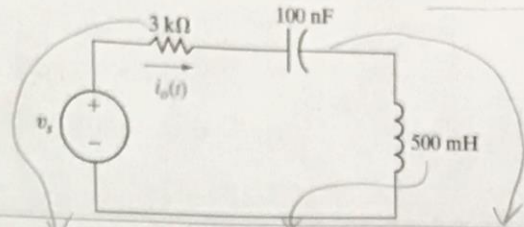2. Find the steady-state expression for $i_o(t)$ in the circuit if $v_s = 80 \cos 2000t$ V $\Rightarrow \textcircled{1} \bar{V}_s = 80 \angle 0^\circ$




0.8 $\textcircled{2} Z = 3000 + j(2000)(0.5) - j \frac{1}{(2000)(100 \times 10^{-9})} = 3000 - j4000 \Omega$

$\textcircled{3} I_o = \frac{\bar{V}_s}{Z} = \frac{80 \angle 0^\circ}{3000 - j4000} = 16 \angle 53.13^\circ \text{ mA}$

$\textcircled{4} \bar{i}_o(t) = 16 \cos(2000t + 53.13^\circ) \text{ mA}$

Answer:

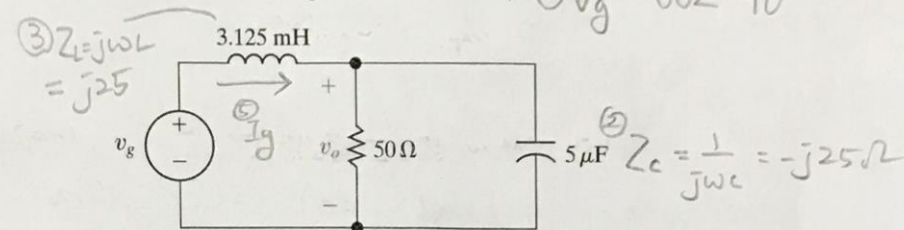3. Find the steady-state expression for $v_o(t)$ in the circuit if $v_g = 60 \sin 8000t$ V $\Rightarrow \textcircled{1} \bar{V}_g = 60 \angle -90^\circ$



0.8 $\textcircled{2} Z_L = j\omega L = j25$

$\textcircled{3} Z_C = \frac{1}{j\omega C} = -j25 \Omega$

$\textcircled{4} Z_{\text{total}} = j25 + (50 \parallel -j25) = 10 + j5 \Omega$


$\textcircled{5} I_g = \frac{\bar{V}_g}{Z_{\text{total}}} = \frac{60 \angle -90^\circ}{10 + j5} = -2.4 - j4.8 \text{ A}$

$\textcircled{6} \bar{V}_o = (50 \parallel -j25) I_g = -120 \text{ V}$

$\textcircled{7} v_o(t) = -120 \cos 8000t \text{ V}$


Answer:

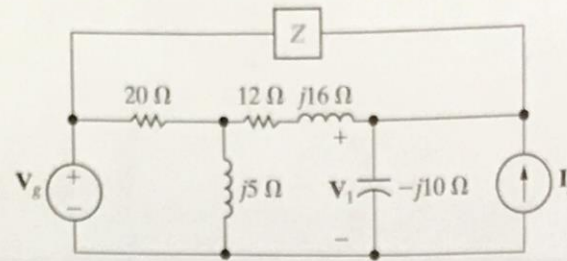4. Find the value of Z in the circuit if $V_g = 100 - j50$ V, $I_g = 30 + j20$ A, and $V_1 = 140 + j30$ V.



0.8

① Redraw the circuit in Phasor Domain

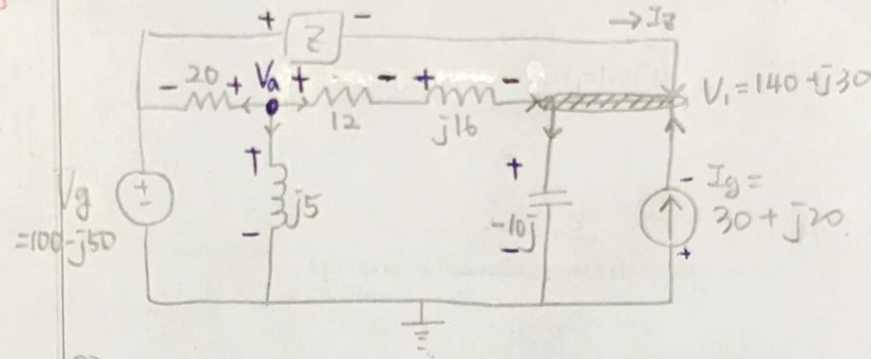

② KCL at V_a

$$\frac{V_a - (100 - j50)}{20} + \frac{V_a}{j5} + \frac{V_a - (140 + j30)}{12 + j16} = 0 \Rightarrow V_a = 40 + j30$$

③ KCL at V_1

$$I_g + (30 + j20) + \frac{(40 + j30) - (140 + j30)}{12 + j16} = \frac{140 + j30 - 0}{-j10}$$

$$\Rightarrow I_Z = -30 - j10$$


$$\textcircled{4} Z = \frac{(100 - j50) - (140 + j30)}{-30 - j10} = \underline{2 + j2 \, \Omega}$$

Answer:

(1)

Let $A = |A| \angle (\omega t + \theta_1) \Rightarrow \bar{A} = |A| \angle -\theta_1$
 $B = |B| \angle (\omega t + \theta_2) \Rightarrow \bar{B} = |B| \angle -\theta_2$
 If A & B are in phase $\theta_1 = \theta_2$
 $\therefore \frac{\bar{A}}{\bar{B}} = \frac{|A| \angle -\theta_1}{|B| \angle -\theta_1} = \frac{|A|}{|B|} \leftarrow \text{purely real.}$

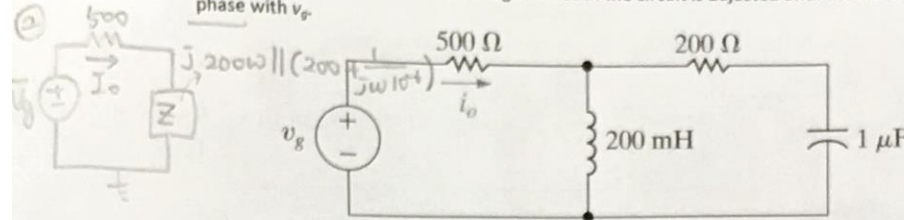5. The frequency of the sinusoidal voltage source in the circuit is adjusted until the current i_o is in phase with v_g .



- a) Find the frequency in hertz.

0.4 (3) If \bar{v}_g and \bar{I}_o are in phase, the ratio (impedance) must be purely real (\because (1))

(4) $\frac{\bar{v}_g}{\bar{I}_o} = Z_{eq} = 500 + Z = 500 + (j\omega 200 \parallel (200 + \frac{1}{j\omega 10^{-6}}))$
 real already, no need to consider.

(5) to make Z_{eq} "real"
 $Z_{eq} = \frac{(j\omega 200 \parallel (200 - j/\omega \times 10^{-6})) \times \omega}{(j\omega 200 - j/\omega \times 10^{-6} + 200) \times \omega} = \frac{j\omega 200(200\omega - j10^6)}{j(\omega^2 200 - 10^6) + 200\omega} = \frac{a+bi}{c+di}$
 $= \frac{(a+bi)(c-di)}{(c+di)(c-di)} = \frac{1}{c^2+d^2} (ac+bd + j(bc-ad))$ If this is zero then Z_{eq} = purely real.
 $\Rightarrow \omega 0.2(1 - \omega^2 0.2 \times 10^{-6}) + \omega^3 200^2 \times 0.2 \times (10^{-6})^2 = 0$
 $\omega^2 = \frac{1}{0.2 \times 10^{-6} - 200^2 (10^{-6})^2} = 6250.000 \Rightarrow \omega = 2500 \text{ rad/s}$

Answer: (7) $f = \frac{\omega}{2\pi} = 396.9 \text{ Hz}$

- b) Find the steady-state expression for i_o (at the frequency found in [a]) if $v_g = 90 \cos \omega t \text{ V}$.

0.4 $Z = 500 + Z_{eq} = 500 + j0.2 \times 2500 \parallel (200 - \frac{j}{2500 \times 10^{-6}})$
 $= 500 + \frac{500j(200 - j400)}{500j + 200 - j400} = \frac{20 \times 10^4 + 10 \times 10^4 j}{200 + 100j}$
 $= 1500 \Omega$
 $I_g = \frac{\bar{V}_g}{Z} = \frac{90 \angle 0^\circ}{1500} = 60 \text{ mA}$
 Answer: $i_g(t) = 60 \cos 2500t \text{ mA}$