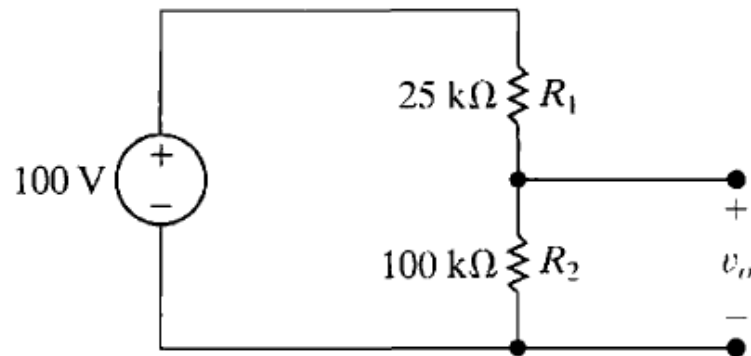


CET 141: Day 2

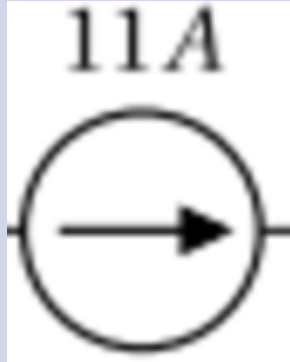

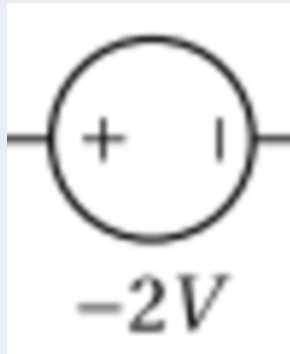
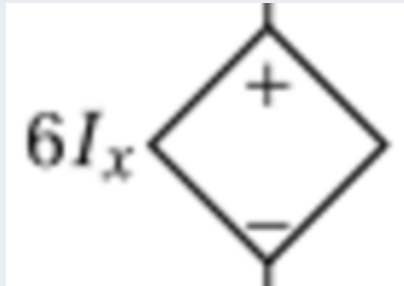
Dr. Noori KIM

- The resistors used in the voltage-divider circuits have a tolerance of $\pm 10\%$. Find the maximum and minimum value of v_o




- The maximum value of v_o occurs when R_2 is 10% high and R_1 is 10% low
- The minimum value of v_o occurs when R_2 is 10% low and R_1 is 10% high

Electrical Sources

	Independent (Circle)	Dependent (Diamond)
Current (Arrow)		
Voltage (Polarity)		

Dependent sources

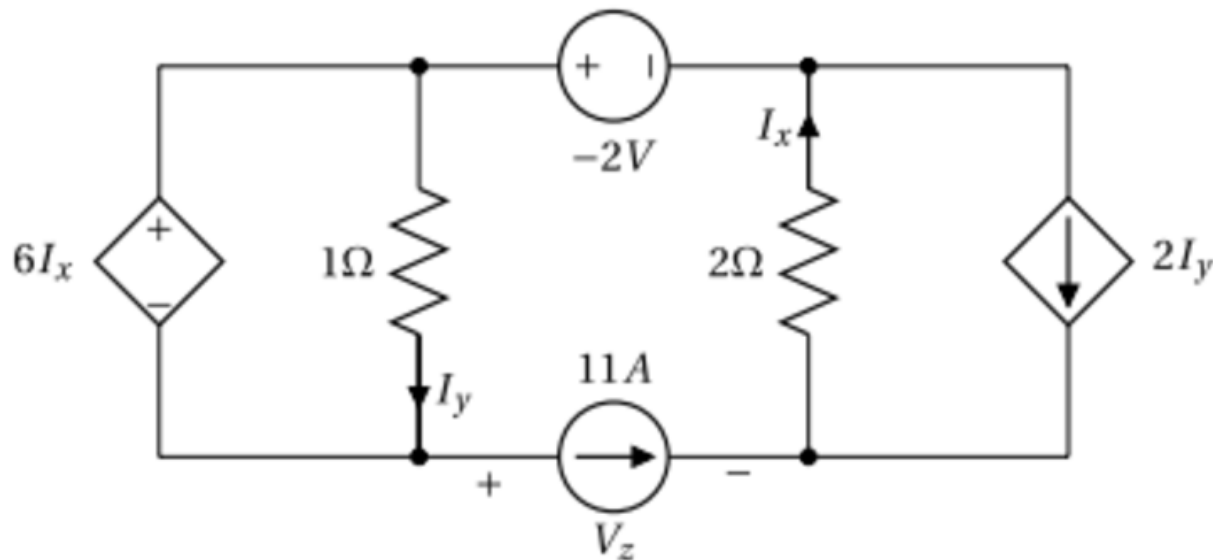
- **A dependent source**
 - a voltage **source** or a current **source**
 - whose value depends on a voltage or current somewhere else in the network.




Wheatstone bridge

- A device which is used to measure the electrical resistance by comparison method
- To measure an unknown resistance by passing current through the unknown resistor
- Brief History:
 - First founded by Samuel Hunter Christie in 1833
 - Sir Charles **Wheatstone** claimed the various applications of the device and showed its importance to the people (the device name after him)

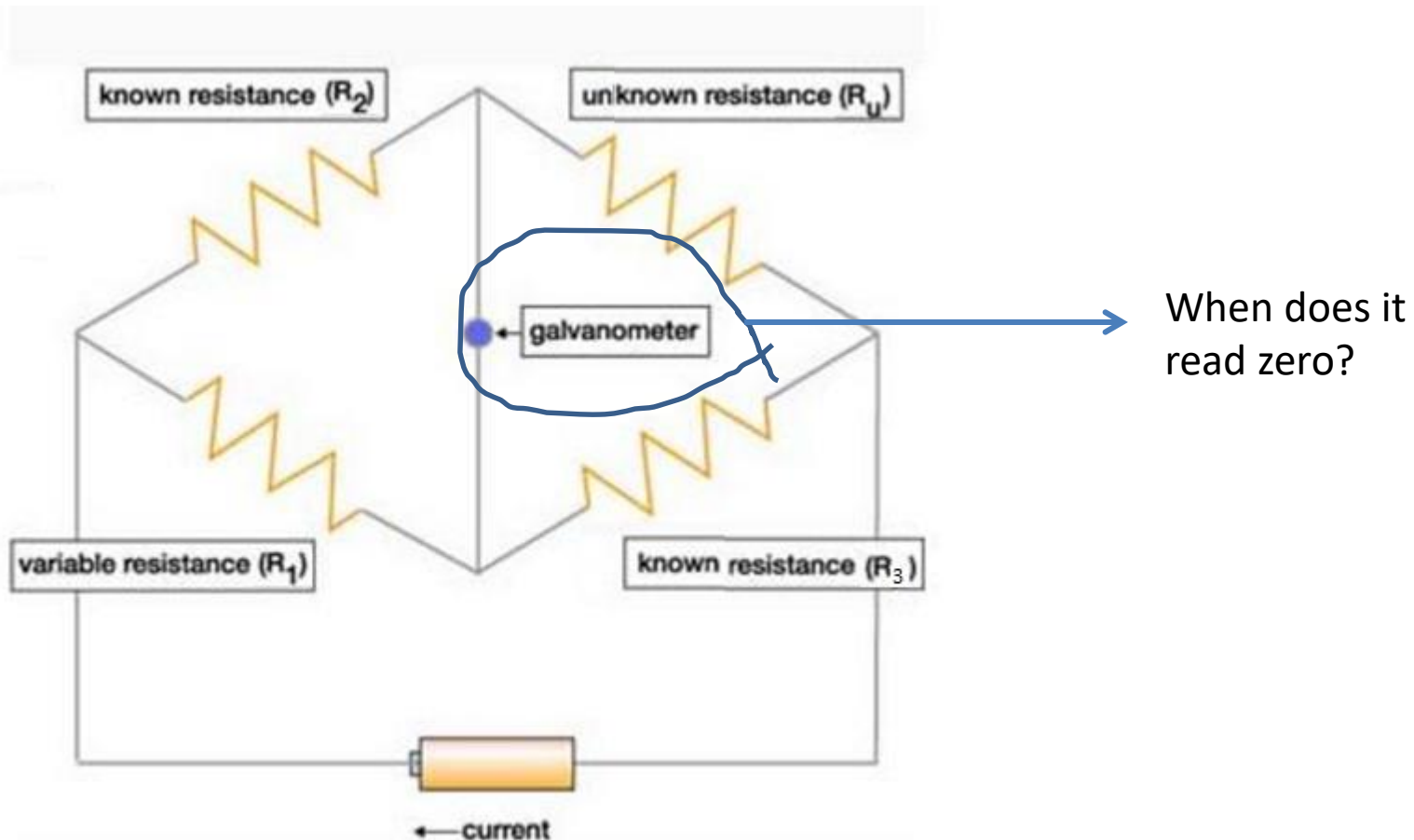
- R_1 , R_2 , R_3 and R_u
- R_u is the resistor whose resistance is to be found and R_1 is the only adjustable resistor (in this setting)



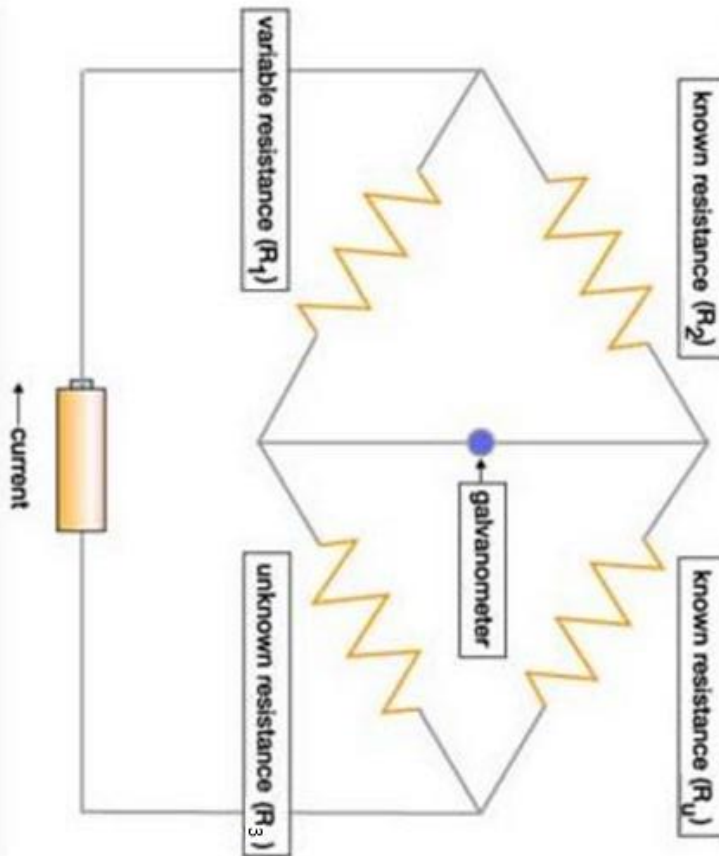

- Known path: R₂, R₁ = Unknown path: R_u, R₃
 - The reading current at the galvanometer=0
 - Varying R₁ to find R_u: **$R_u = (R_3 * R_2) / R_1$**
 - **Or varying one of variable resistors among R₁, R₂, or R₃**

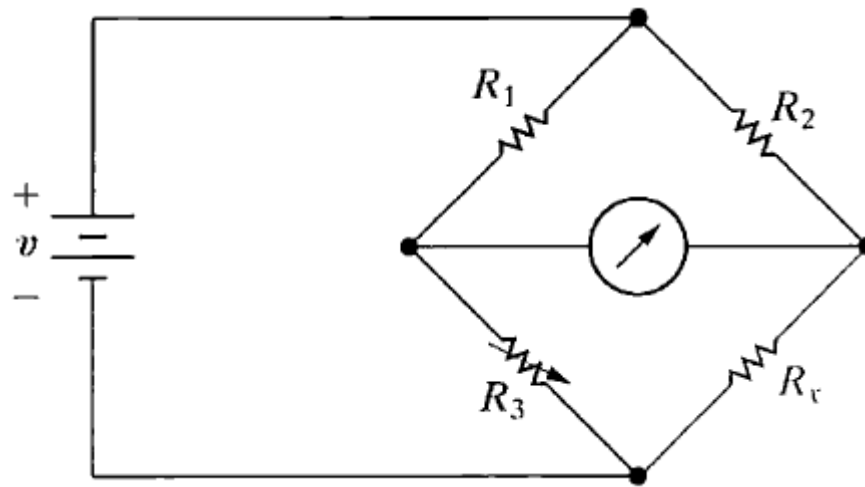- The bridge circuit shown is balanced when $R_1 = 100\Omega$, $R_2 = 1000\Omega$, and $R_3 = 150\Omega$. The bridge is energized from a 5 V dc source. What is the value of R_x ?





- Suppose each bridge resistor is capable of dissipating 250 mW. Can the bridge be left in the balanced state without exceeding the power-dissipating capacity of the resistors (without damaging the bridge)?

Hint>>

➤ Calculate dissipating power for each resistor and compare it to 250mW

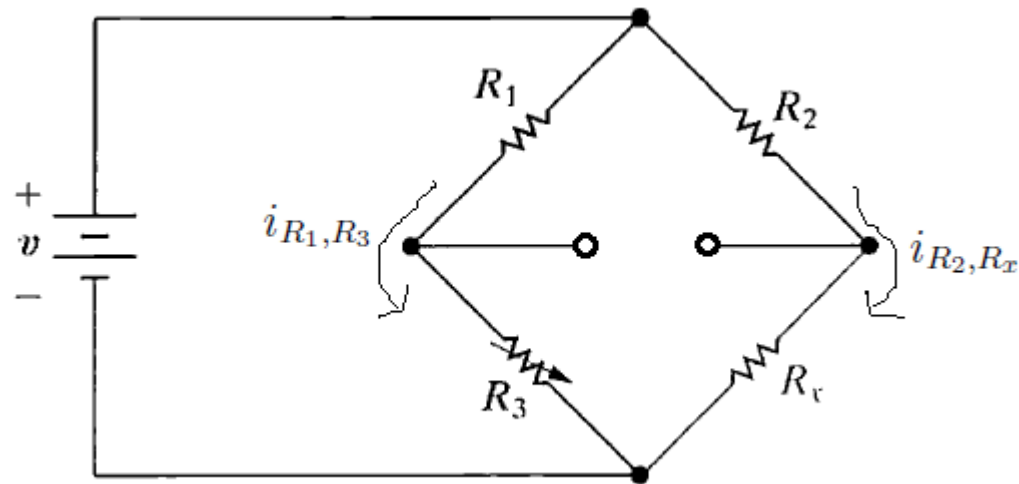➤ When the bridge is balanced, there is no current flowing through the meter, so the meter acts like an open circuit.



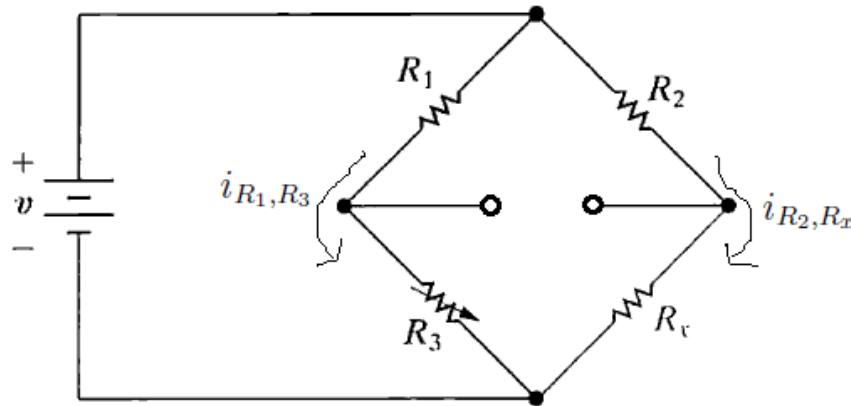

$$i_{R_1, R_3} = \frac{5 \text{ V}}{100 \Omega + 150 \Omega} = 20 \text{ mA} \quad i_{R_2, R_4} = \frac{5 \text{ V}}{1000 + 1500} = 2 \text{ mA}$$

$$p = Ri^2:$$

$$p_{100\Omega} =$$

$$p_{150\Omega} =$$

$$p_{1000\Omega} =$$


$$p_{1500\Omega} =$$

$\left. \begin{array}{l} \\ \\ \\ \end{array} \right\} \ll 250 \text{ mW}$

The bridge can be left in the balanced state without exceeding the power-dissipating capacity of the resistors

Delta-to-Wye Equivalent Circuits

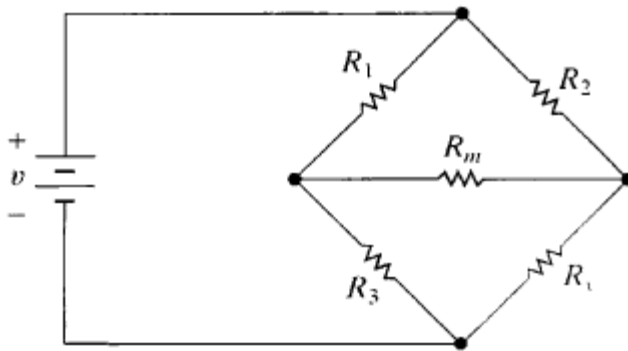
- From the Wheatstone bridge, we **replace the galvanometer** with its equivalent resistance R_m ,



delta (Δ) interconnection

or

Pi (π) interconnection

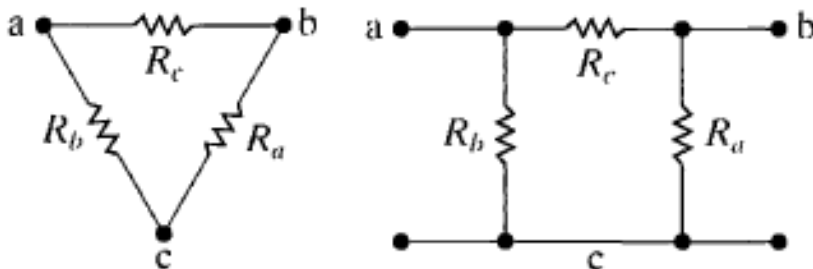

as the Δ can be shaped into a π without disturbing the electrical equivalence of each node

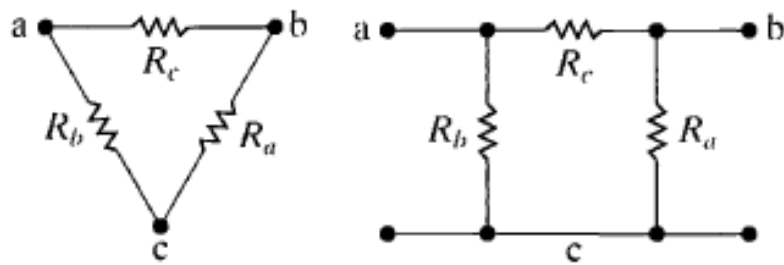


Figure 3.29 ▲ A Δ configuration viewed as a π configuration.

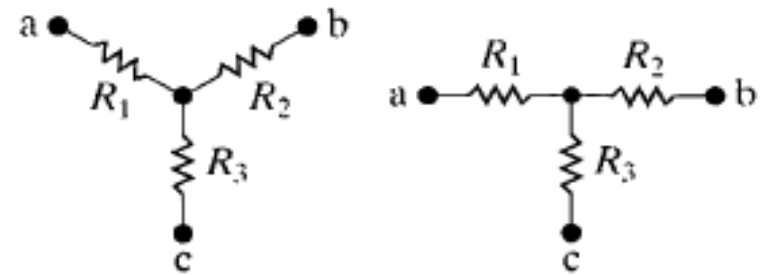


Figure 3.30 ▲ A Y structure viewed as a T structure.

Transformations without disturbing the electrical equivalence

Then, how about this?



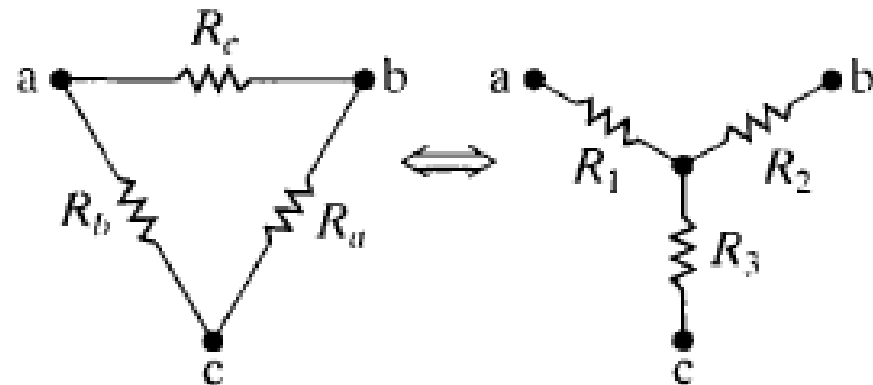


Figure 3.31 ▲ The Δ -to-Y transformation.

Basic idea of the transformation

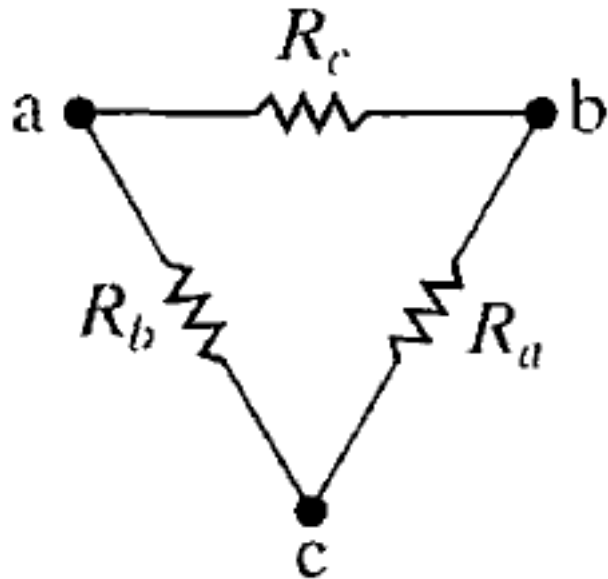

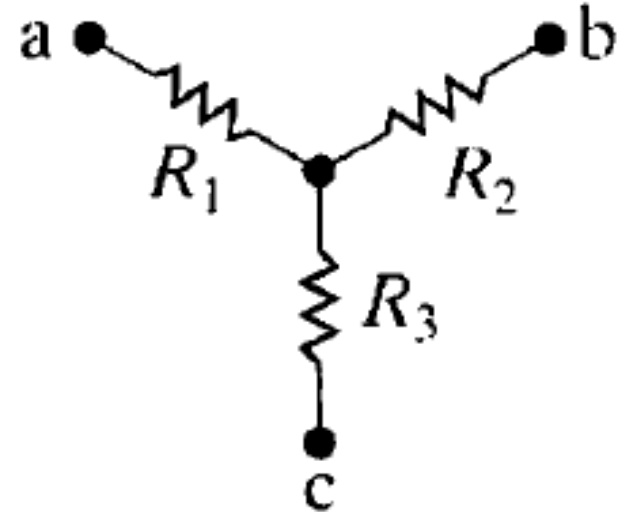Two parallel resistors viewed as two series resistors





$$R_{ab} = \frac{R_c(R_a + R_b)}{R_a + R_b + R_c} = R_1 + R_2$$

$$R_{bc} = \frac{R_a(R_b + R_c)}{R_a + R_b + R_c} = R_2 + R_3$$

$$R_{ca} = \frac{R_b(R_c + R_a)}{R_a + R_b + R_c} = R_1 + R_3$$

Preserve node a, b, c voltages

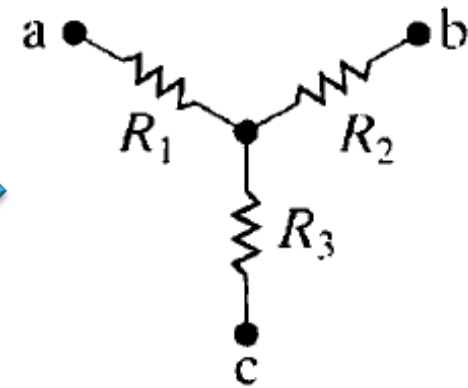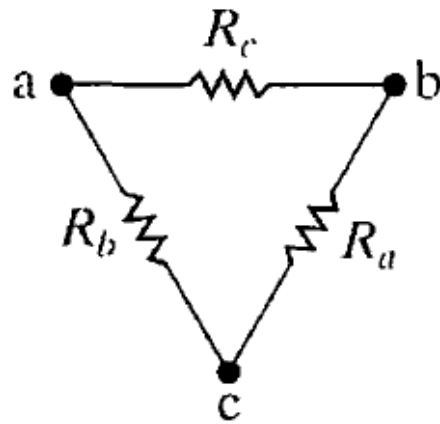Solve for R_1 , R_2 , and R_3 in terms of R_a , R_b , and R_c



$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1},$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2},$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}.$$






$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c},$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c},$$


$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}.$$

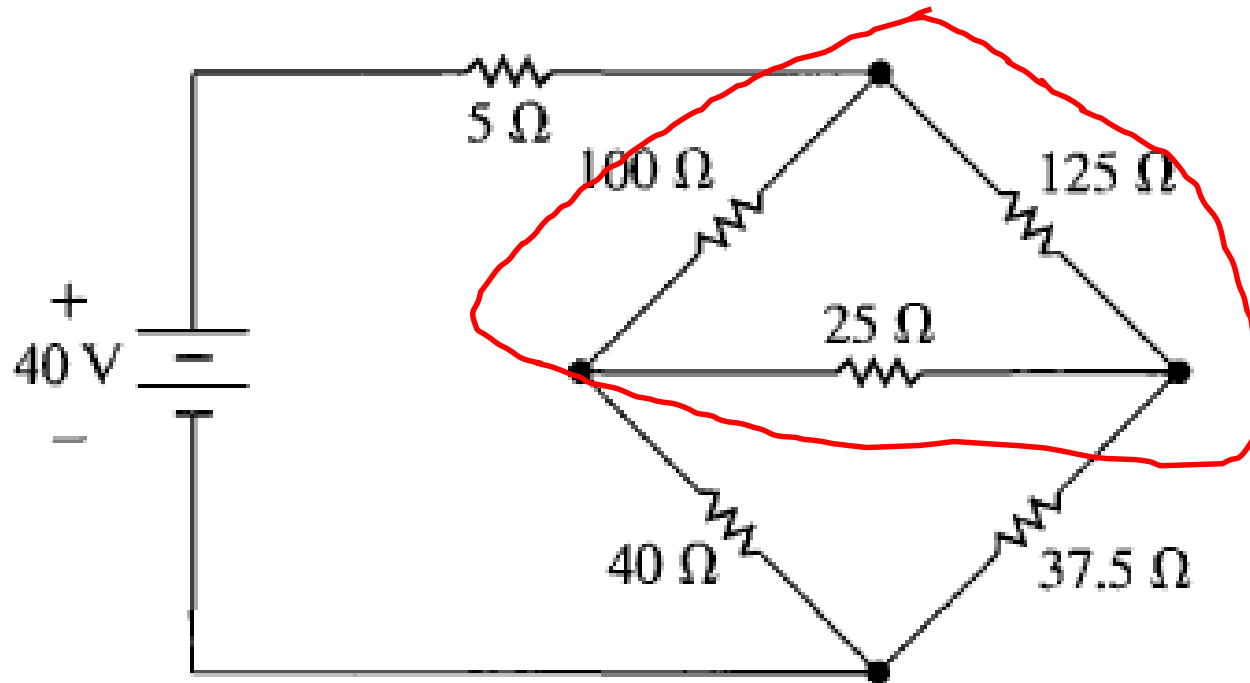- Find the current and power supplied by the 40V source



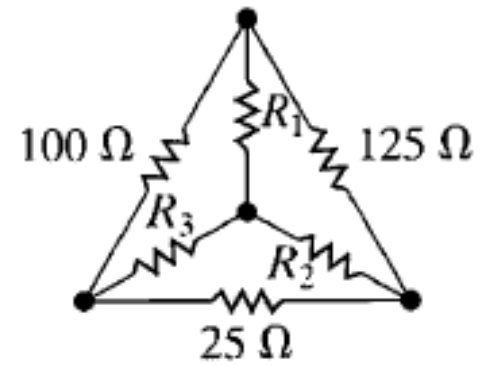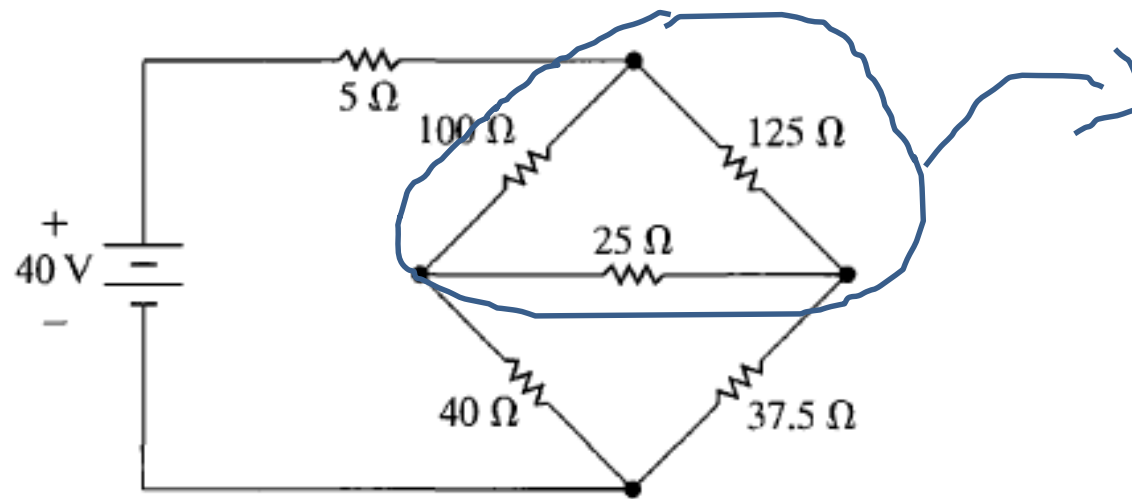


Source transformation

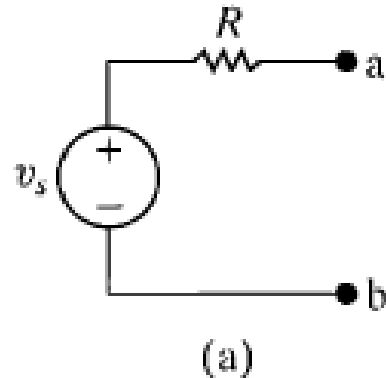

$$V_{ab} = V_s * R_L / (R + R_L)$$

Where $i_s = v_s / R$ \Updownarrow

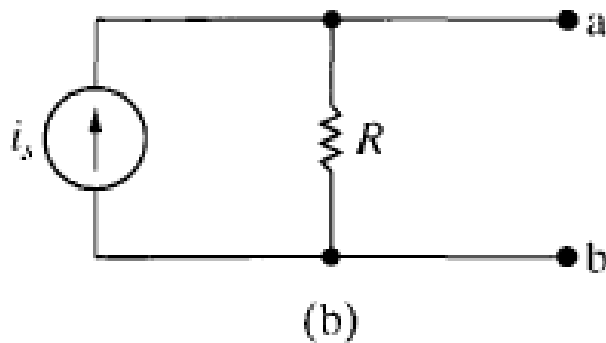

$$V_{ab} = I_s * (R_L * R) / (R + R_L)$$

Figure 4.36 ▲ Source transformations.

- Find the power associated with the 6 V source.

