

# CET 141: Day 7

Dr. Noori KIM

# Agenda

- R, L, and C under AC conditions
- Complex plane and Phasor

# All tools for today

## 1. Phasor

$$- v(t) = A \cos(\omega t + \theta) [V] \rightarrow V_{phasor} = Ae^{j\theta} [V]$$

## 2. Impedance ( $Z=R+jX$ [ $\Omega$ ])

$$- Z_R = R [\Omega]$$

$$- Z_C = \frac{1}{j\omega C} = jX_C = -j\frac{1}{\omega C} [\Omega]$$

$$- Z_L = jX_L = j\omega L [\Omega]$$

# Recap: R, L, and C under DC conditions

- DC sources (i.e,  $V=9V$  or  $I=3A$ ),
  - Resistance  $R$ 
    - Follows Ohm's law,  $V=IR$
  - Capacitance,  $C$ 
    - Opened,  $I=0$
  - Inductance,  $L$ 
    - Shorted,  $V=0$  (just a wire)

# Complete R = Transient R + Steady-State R

Tell us everything that you remember about each response.

If a source is AC

→ through RLC circuits


→ Steady-State R is also AC

→ phasor analysis can be used in *frequency domain*




$$\omega = 2\pi f$$

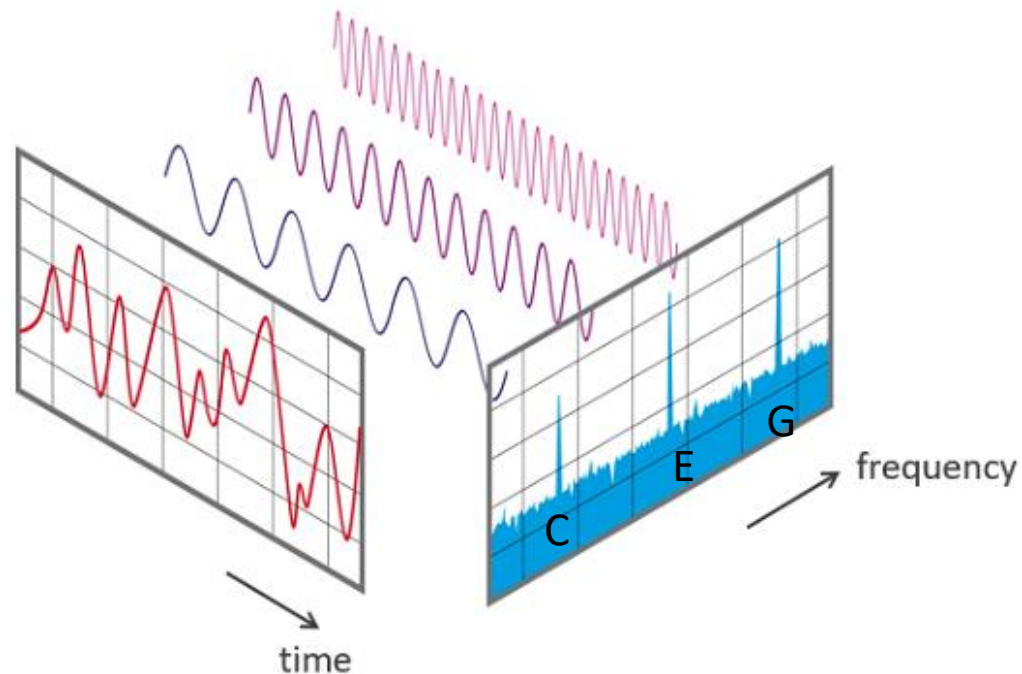- $\omega$  and  $f$  are both measures of frequency
- $\omega$  [rad/sec] and  $f$  [Hz]




# Cycles (radian) and Frequency relation

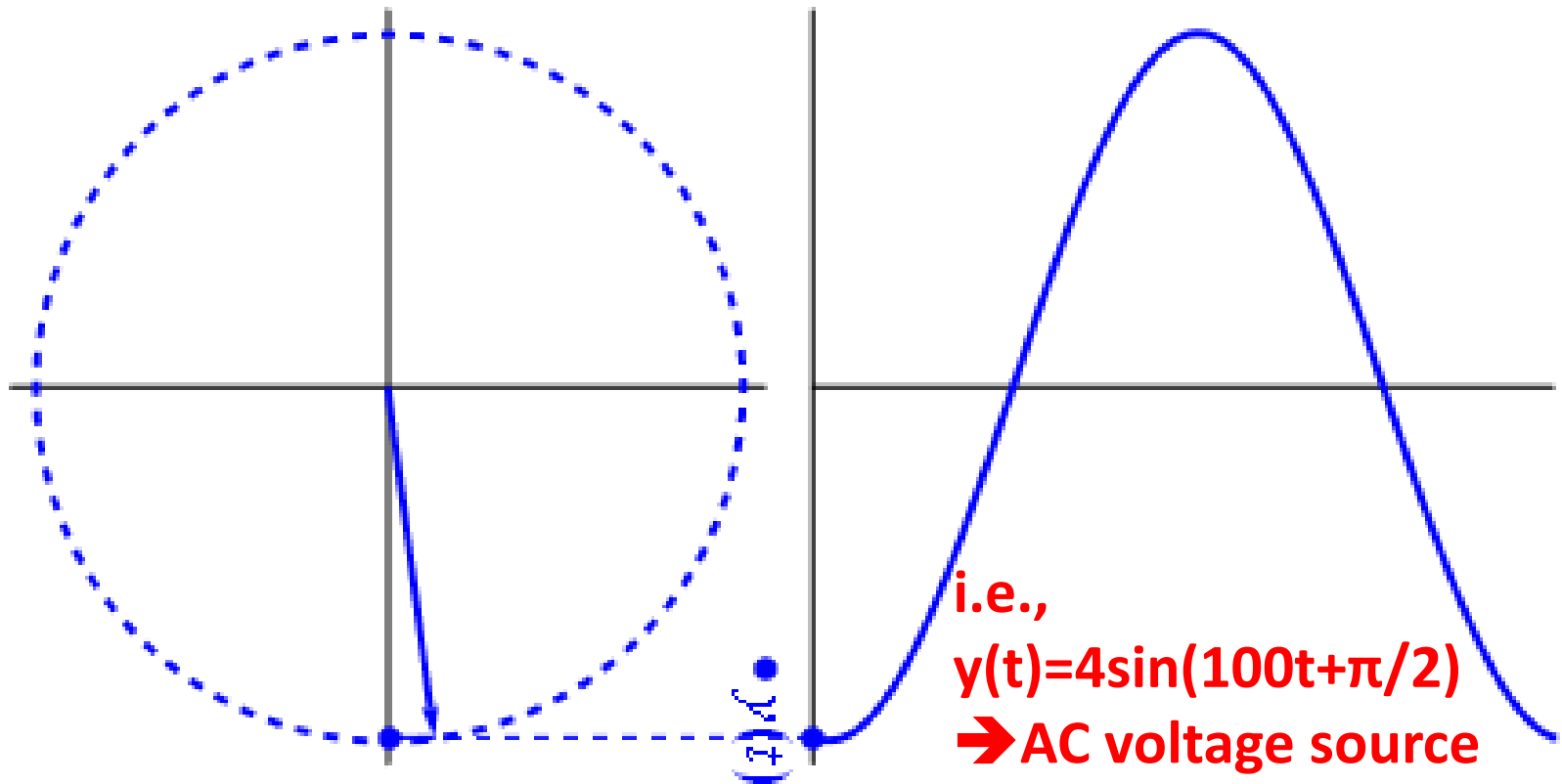

*\*Look at the time domain graph and think about why only steady-state  $R$  is considered in frequency domain analysis*
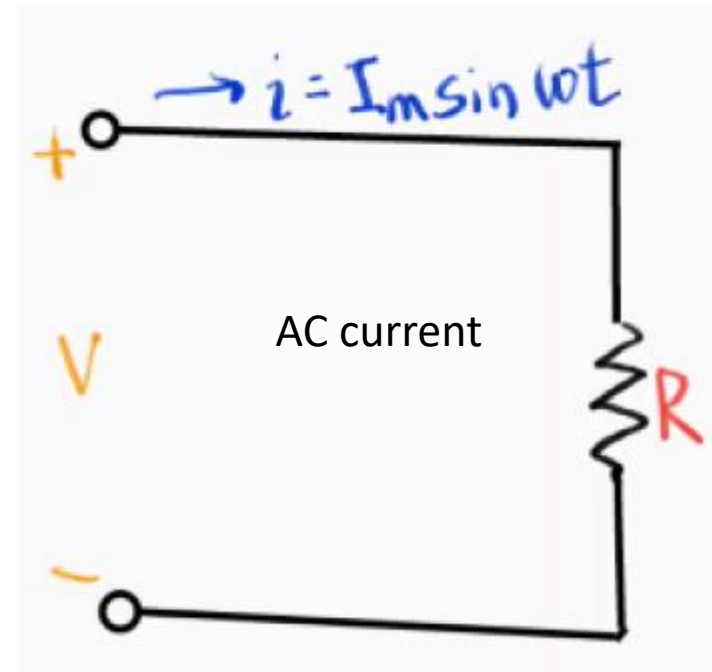
# R under AC

- How do we calculate V?
  - Based on Ohm's law  $V=iR$   
 $V = Ri = \mathbf{R}I_m \sin \omega t$  [V]
- R: a proportional constant between voltage v and current i
- If **i** is a sinusoidal form, then **v** is also a sinusoidal form sharing the same  $\omega$  (angular freq)
  - (+) No phase diff.
  - Same phase = same angle...




$$\begin{aligned} i &= \mathbf{I_m} \sin \omega t \text{ [A]} \\ V &= RI_m \sin \omega t \\ &= \mathbf{V_m} \sin \omega t \text{ [V]} \end{aligned}$$




$$i = I_m \sin \omega t [A], V = V_m \sin \omega t [V]$$

Max values!!!

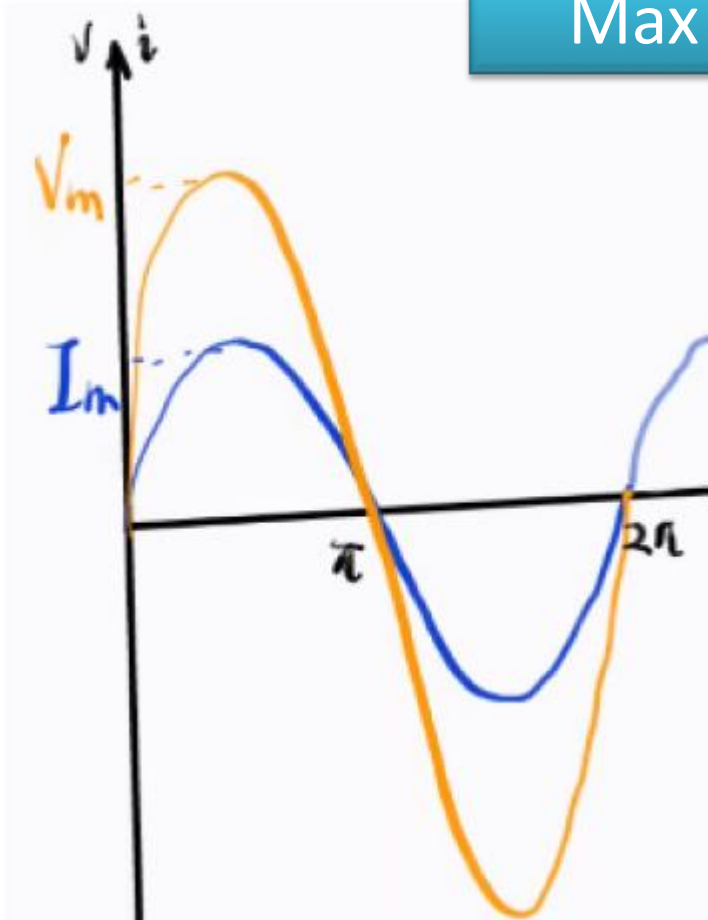

- Whether you use a current source or a voltage source;
  - the current flows through R
  - or
  - the voltage across the R
- R Will not change.

# Example: find $i$

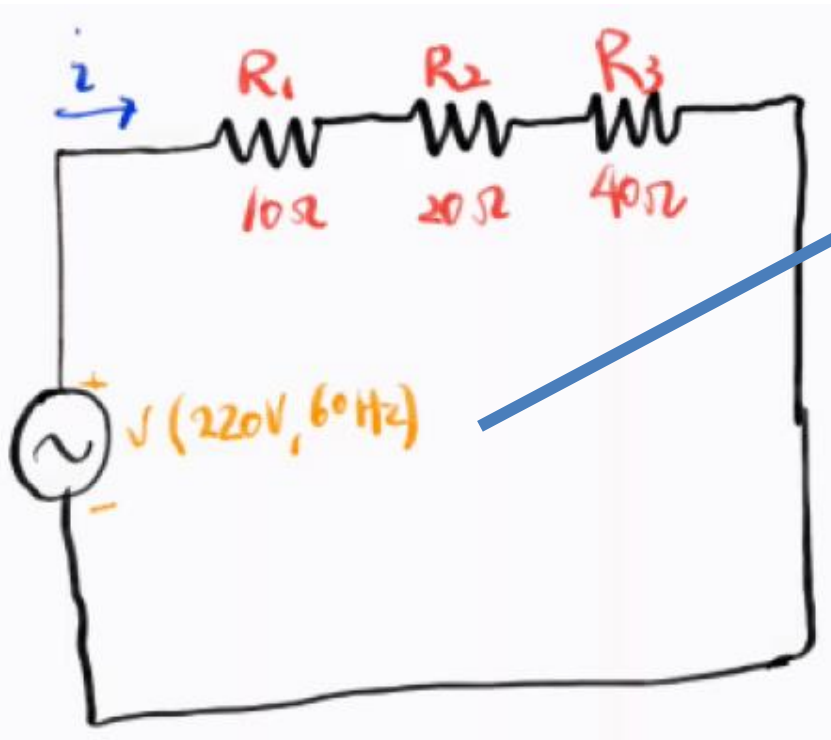

The V is given in this format (think about all appliances that we have 110V-60Hz...110V-50Hz...)

# L under AC

- How do we calculate V?


$$L = \frac{N^2 \mu A}{\ell} \rightarrow \Phi = L \cdot I \rightarrow V = \frac{\Delta \Phi}{\Delta t} \rightarrow V = L \cdot \frac{d}{dt} I$$

$$v = L \frac{d}{dt} (I_m \sin \omega t)$$

$$= \omega L I_m \cos \omega t$$

$$= \omega L I_m \sin(\omega t + 90^\circ) \text{ [V]}$$

$$i = I_m \sin \omega t \text{ [A]}$$

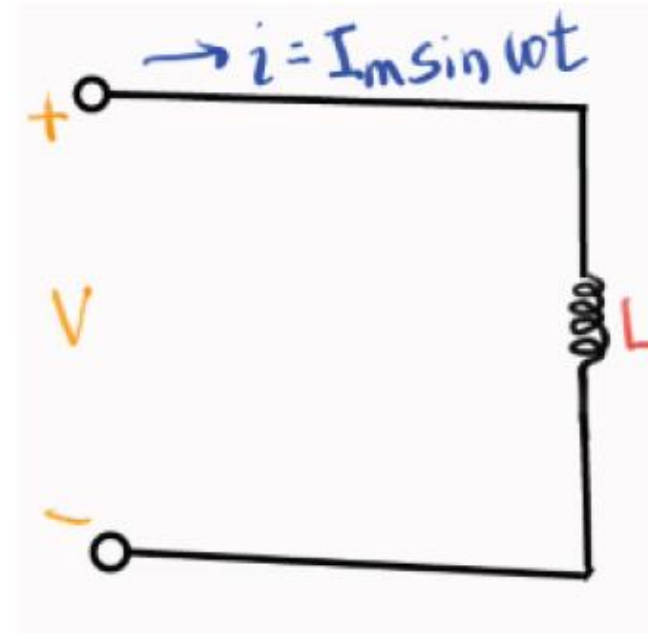

Do you see the clear difference compared to the R case?

$$\cos(\omega t + \phi) = \sin(\omega t + \phi + 90^\circ)$$

$$\sin(\omega t + \phi) = \cos(\omega t + \phi - 90^\circ)$$

$$-\sin(\omega t) = \sin(\omega t \pm 180^\circ)$$

$$-\cos(\omega t) = \cos(\omega t \pm 180^\circ)$$

$$-\cos(\omega t) = \sin(\omega t \pm 270^\circ)$$

$$\pm \sin(\omega t) = \cos(\omega t \pm 90^\circ)$$

$$\pm \cos(\omega t) = \sin(\omega t \pm 90^\circ)$$


$$-\sin(\omega t) = \sin(-\omega t)$$

$$\cos(\omega t) = \cos(-\omega t)$$

$$i = I_m \sin \omega t \text{ [A]},$$

$$V = \omega L I_m \sin(\omega t + 90^\circ) \text{ [V]}$$

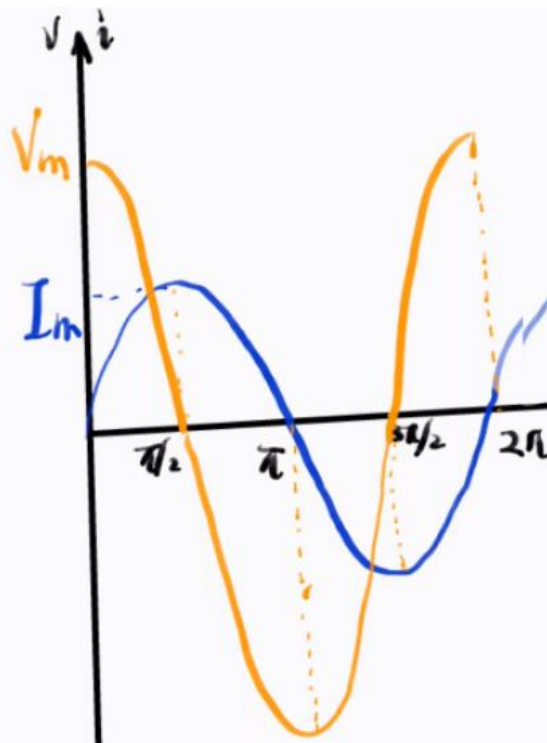OMG!!! There is a phase difference between the V and I!!!




- $\omega$  is the same for V and I, but affects magnitude of I
- The V period is shifted  $\frac{\pi}{2}$  from the I (to the left)
- The max V ( $V_m$ ) is multiplied by  $\omega L$  from the max I ( $I_m$ )

# $\omega L$ : Inductive reactance $X_L$

- Imag. Coeffic. of impedance  $Z$  with a unit of  $\Omega$ -ohm
  - $Z=R+jX$  [ $\Omega$ ]
  - $Z$ : impedance
  - $R$ : resistance (real part),  $X$ : reactance (imaginary part) where units for both  $R$  and  $X$  are  $\Omega$
- Basically it is a resistance (disturbing current flows) but depends on the frequency

- Therefore if *frequency ( $\omega=2\pi f$ ) increases*,  $\omega L$  *increases*.
  - An Inductor: Blocking high frequency signals.
  - At DC status,  $f=0 \rightarrow \omega =0$ :
    - Basically no inductive restiveness in the circuit, as  $X_L=\omega L=0$
    - An Inductor behaves Just like a wire

# Example find $L_{\min}$

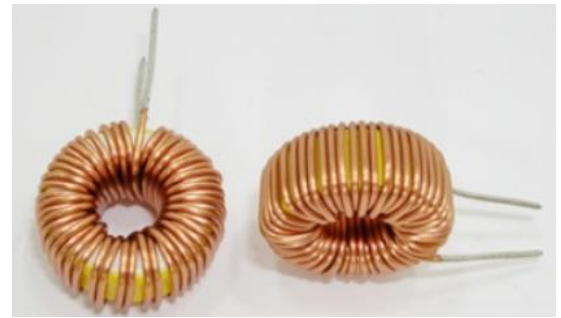

- A choke coil is an inductor used to block higher-frequency alternating current (AC) in an electrical circuit, while passing lower-frequency or direct current (DC).
- Determine the inductance of choke coil to exceed  $8000\Omega$  at 60Hz and above.



# C under AC

- How do we calculate V?

$$C = \frac{\epsilon \cdot A}{d} \rightarrow Q = CV \rightarrow I = \frac{\Delta Q}{\Delta t} \rightarrow I_c = C \cdot \frac{d}{dt} V_c \rightarrow V_c = \frac{1}{C} \int I_c dt$$


$$v = \frac{1}{C} \int I_m \sin \omega t dt$$

$$= -\frac{1}{\omega C} I_m \cos \omega t$$

$$= \frac{1}{\omega C} I_m \sin(\omega t - 90^\circ) \text{ [V]}$$




$$i = I_m \sin \omega t \text{ [A]}$$

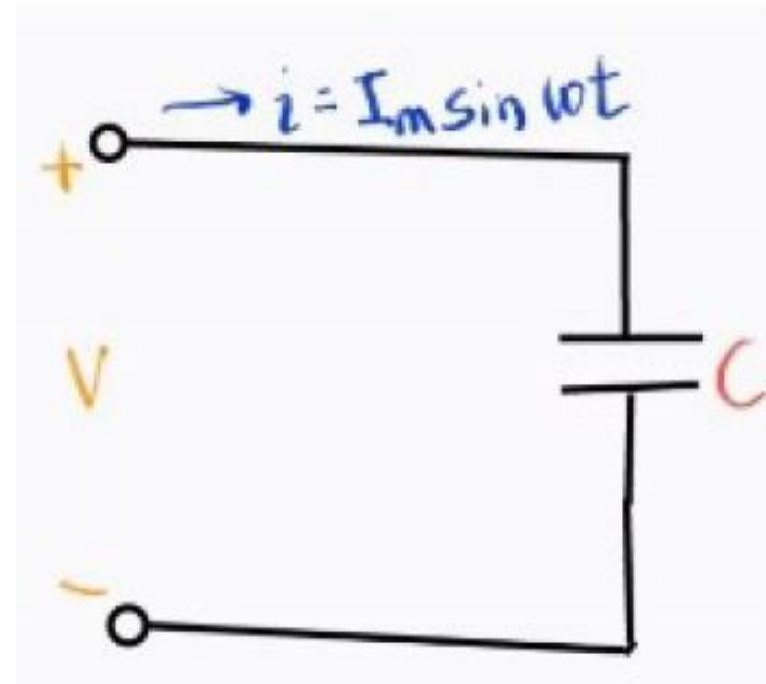

$$i = I_m \sin \omega t [A],$$

$$V = \frac{1}{\omega C} I_m \sin(\omega t - 90^\circ) [V]$$

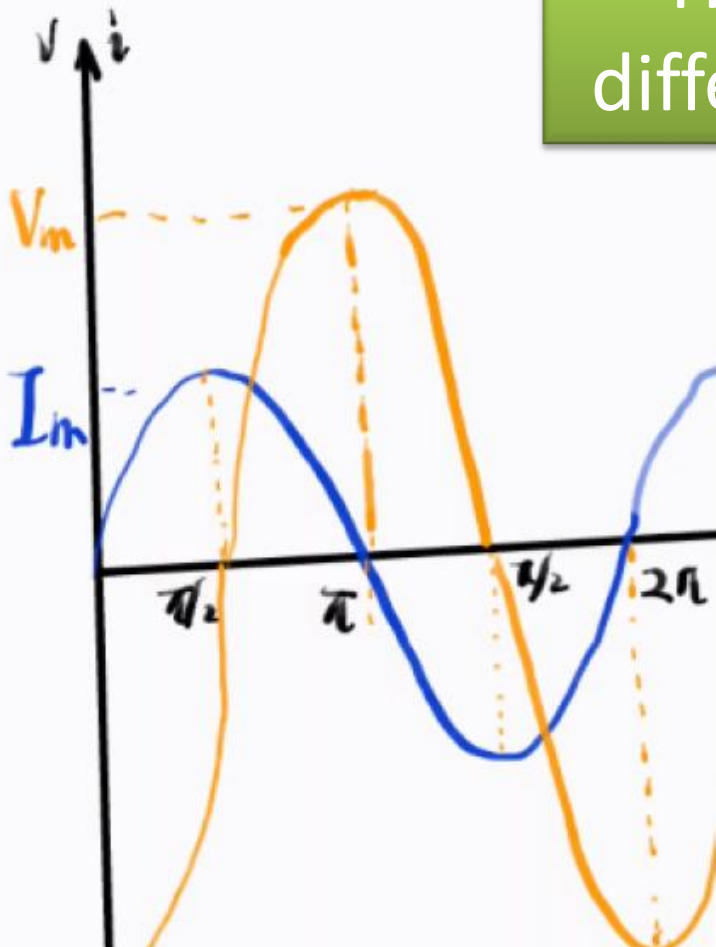Here we have another phase difference between the V and I!!!



- $\omega$  is same for both V and I, but affects magnitude of V
- The V period is shifted  $\frac{\pi}{2}$  from the I (to the right)
- The max V ( $V_m$ ) is multiplied by  $\frac{1}{\omega C}$  from the max I ( $I_m$ )

# $\frac{1}{\omega C}$ : Capacitive reactance $X_c$

- Imag. Coeffic. of impedance Z with a unit of  $\Omega$ -ohm
  - $Z=R+jX$  [ $\Omega$ ], where Z: impedance
  - R: resistance (real part), X: reactance (imaginary part) where units for both R and X are  $\Omega$
- Basically **it is a resistance (disturbing current flows)** but **depends on the frequency**

- Therefore if *frequency ( $\omega=2\pi f$ ) decreases*,

$$\frac{1}{\omega C} \text{ *increases* .}$$

– A capacitor: **Blocking low** frequency signals.

– At DC status,  $f=0 \rightarrow \omega =0$ :

- Basically infinity capacitive reactance in the circuit, as  $X_C=\infty$ , current can't flow this path.
- A capacitor behaves Just like disconnected wires (O.C.)

LL pass  
CH pass

# Summary on the impedance

- An impedance ( $Z$ ) is a concept to be defined for (in) the frequency domain
  - It is a sum of resistance ( $R$ ) and reactance ( $X$ )
  - $Z=R+jX \rightarrow$  unit: “Ohm”  $\rightarrow$  a measure of restiveness of the circuit  $\rightarrow$  if  $Z$  is high, electrons are hard to flow (low current)
- A resistor ( $R$ )
  - has an impedance form of  $R \rightarrow$  resistance
- An inductor ( $L$ )
  - has an impedance form of  $j\omega L \rightarrow$  reactance
- A Capacitor ( $C$ )
  - Has an impedance for of  $\frac{1}{j\omega C} \rightarrow$  reactance

# Please, Do remember..

- Capacitive reactance  $X_c: 1/(\omega C)$ 
  - between  $V$  and  $I$ ,  $\omega t$ : no change only  $-90$  phase diff.
- Inductive reactance  $X_L: \omega L$ 
  - between  $V$  and  $I$ ,  $\omega t$ : no change only  $+90$  phase diff.
- Impedance  $Z=R+jX$  [ $\Omega$ ], where
  - Series  $Z_{eq}=Z_1+Z_2+Z_3....$ 
    - $\text{Re}\{Z_{eq}\}$ : from resistors,  $\text{Im}\{Z_{eq}\}$ : inductors and caps
  - Parallel  $1/Z_{eq}=1/Z_1+1/Z_2+1/Z_3....$ 
    - $\text{Re}\{Z_{eq}\}$  and  $\text{Im}\{Z_{eq}\}$ : combination of  $R, C, L$

$$\sin(a + b) = \sin(a)\cos(b) + \cos(a)\sin(b)$$

$$\sin\left(\frac{\pi}{2} + x\right) = \sin\left(\frac{\pi}{2}\right) \cdot \cos(x) + \cos\left(\frac{\pi}{2}\right) \cdot \sin(x)$$

$$\sin\left(\frac{\pi}{2}\right) = 1$$

$$\cos\left(\frac{\pi}{2}\right) = 0$$

So we have :

$$\sin\left(\frac{\pi}{2} + x\right) = \cos(x)$$

$$\begin{aligned}\cos x &= \sin\left(\frac{\pi}{2} - x\right) = \sin\left(-\left(x - \frac{\pi}{2}\right)\right) \\ &= -\sin\left(x - \frac{\pi}{2}\right)\end{aligned}$$

To the frequency domain

# **COMPLEX PLANE AND PHASOR**



- Before learning phasor, we need to review the complex plane
- There are two methods to represent complex numbers
  - Rectangular (Cartesian) coordinate
  - Polar (angular) coordinate
- **$y = a + jb \rightarrow \text{Re}\{Y\} = a$  and  $\text{Im}\{Y\} = jb$** 
  - $\rightarrow |y| = \sqrt{a^2 + b^2} = r$ ,  $\text{angle}\{y\} = \tan^{-1} \frac{b}{a} = \theta$**
  - $\rightarrow y = r e^{j\theta}$**
  - $\rightarrow y = r(\cos \theta + j \sin \theta)$**

Euler's formula:  $e^{jx} = \cos x + j \sin x$


VIF: very important formula

Euler's formula:  $e^{jx} = \cos x + j \sin x$

Along with  $i_c$  and  $v_L$  26


# Rectangular (Cartesian) coordinate

- $y = a + jb$

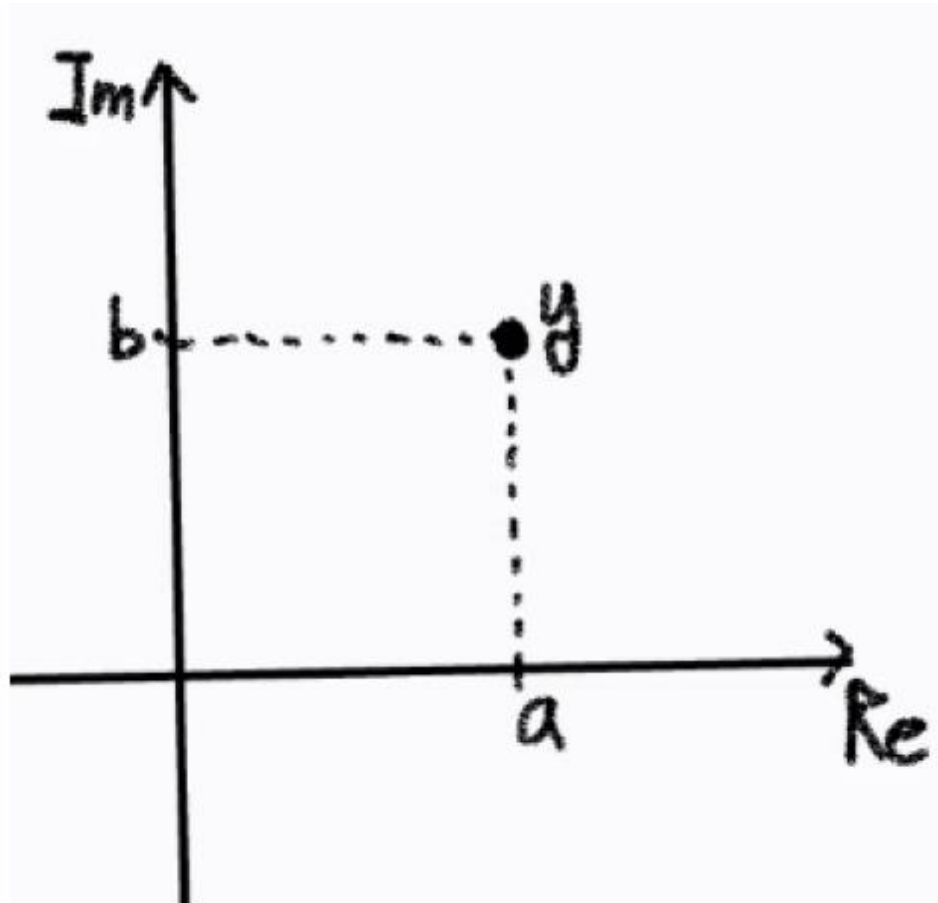

# Polar (angular) coordinate

- $y = a + jb$

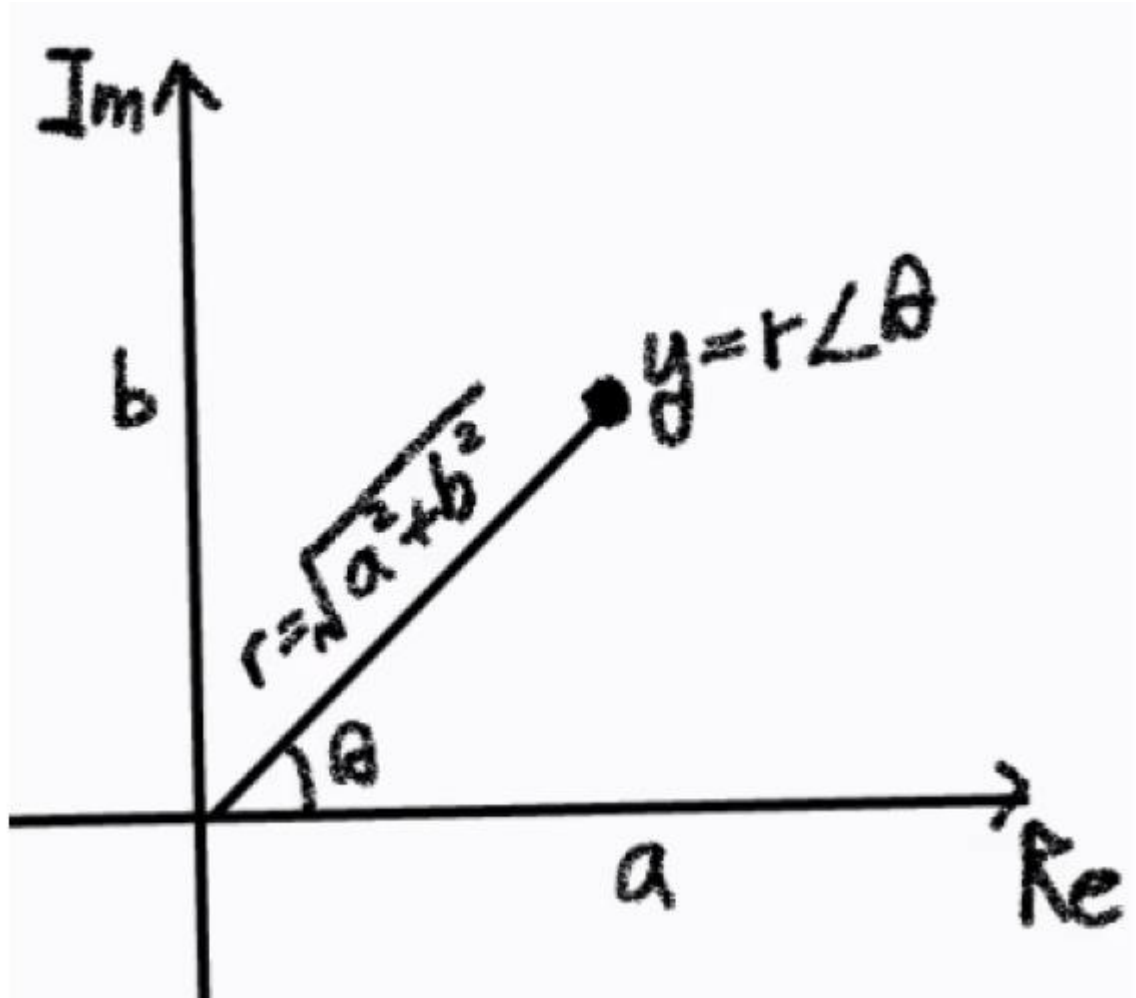

# A phasor

- A complex number, representing a sinusoidal function, whose
  - Amplitude  $M$
  - Angular frequency  $\omega$
  - Initial phase  $\theta$
- Example
  - A sinusoidal function  $x(t)$ 
$$x(t) = M \cos(\omega t + \theta), \quad -\infty < t < \infty$$
  - A phasor form of  $x(t)$ , namely  $\bar{X}$ 
$$\bar{X} = M e^{j\theta} = M \cos \theta + jM \sin \theta$$

Let's investigate the situation from  $x(t) \rightarrow \bar{X}$  or vice versa

$$\mathbf{x(t)} = \text{Re}\{\bar{X}e^{j\omega t}\} \text{ proof!!}$$

$$x(t) = M \cos(\omega t + \theta) \longleftrightarrow \bar{X} = Me^{j\theta} = M \cos \theta + jM \sin \theta$$

- $\text{Re}\{\bar{X}e^{j\omega t}\}$ 

$$= \text{Re}\{Me^{j\theta}e^{j\omega t}\}$$

$$= \text{Re}\{Me^{j(\theta+\omega t)}\}$$

$$= \text{Re}\{M \cos(\theta + \omega t) + jM \sin(\theta + \omega t)\}$$

$$= M \cos(\theta + \omega t)$$

$$= \mathbf{x(t)} = \text{Re}\{\bar{X}e^{j\omega t}\}$$
- The sinusoidal signal  **$\mathbf{x(t)}$  is the real part of phasor** taking back its original angular frequency
- When we **represent a sinusoidal signal in phasor form**, the complex exponential  **$e^{j\omega t}$  factors out!!!**

- Apply this to the sum of two sinusoidal **at the same frequency**

$$\begin{aligned} & A \cos(\omega t + \theta) + B \cos(\omega t + \varphi) \\ &= \operatorname{Re}\{Ae^{j(\omega t + \theta)}\} + \operatorname{Re}\{Be^{j(\omega t + \varphi)}\} \\ &= \operatorname{Re}\{Ae^{j(\omega t + \theta)} + Be^{j(\omega t + \varphi)}\} \\ &= \operatorname{Re}\{e^{j\omega t}(Ae^{\theta} + Be^{\varphi})\} \end{aligned}$$


- Why do we learn this?
  - Do you remember V and I for L and C cases?
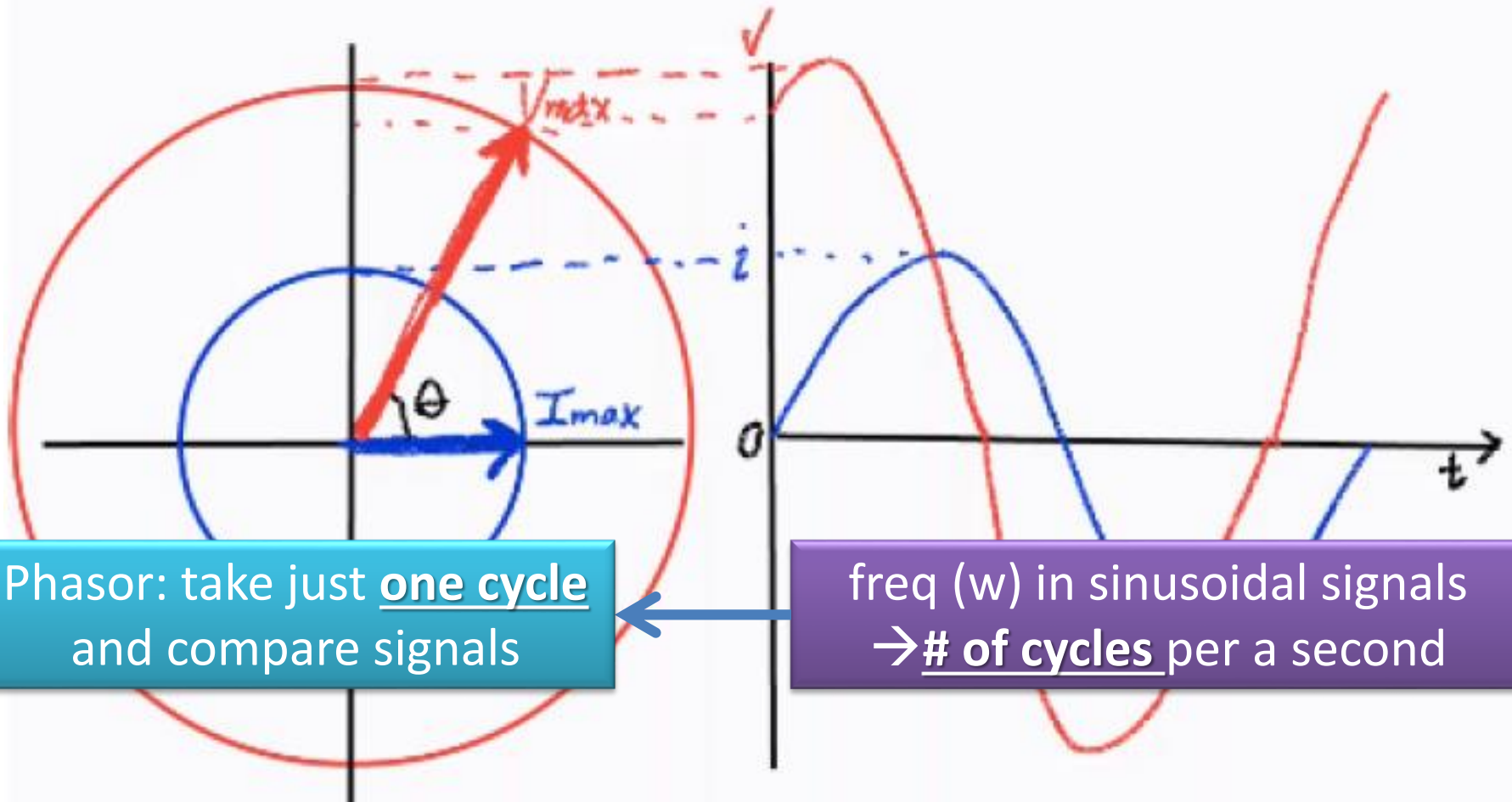
## Recall

- Capacitive reactance  $X_c: 1/(\omega C)$ 
  - between  $V$  and  $I$ ,  **$\omega t$ : no change** only  $-90$  phase diff.
- Inductive reactance  $X_L: \omega L$ 
  - between  $V$  and  $I$ ,  **$\omega t$ : no change** only  $+90$  phase diff.

The phasor looks like a very  
useful tool for circuit  
analysis!!





Phasor: take just one cycle and compare signals

freq ( $\omega$ ) in sinusoidal signals  
 $\rightarrow$  # of cycles per a second



Phasor graph, at  $t=0$

Sinusoidal graph

$t=0$

A phasor is meant to represent the magnitude and phase between  $V$  and  $I$

$t=\pi/2$

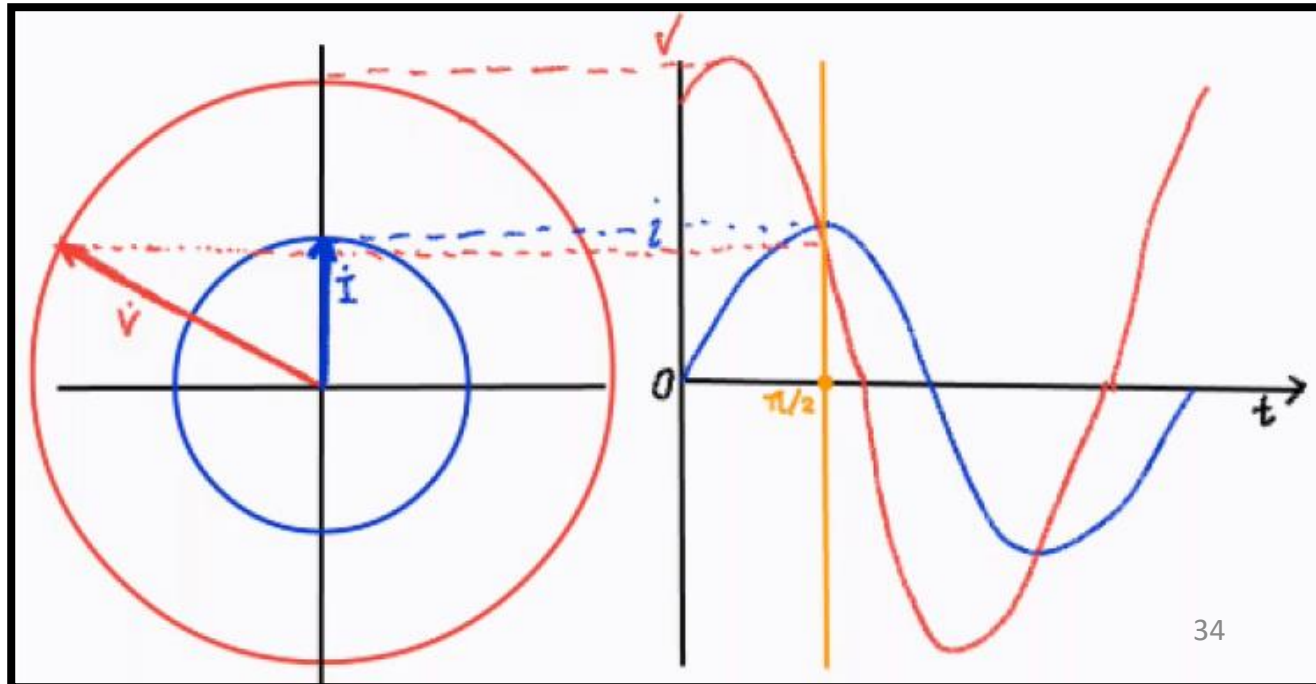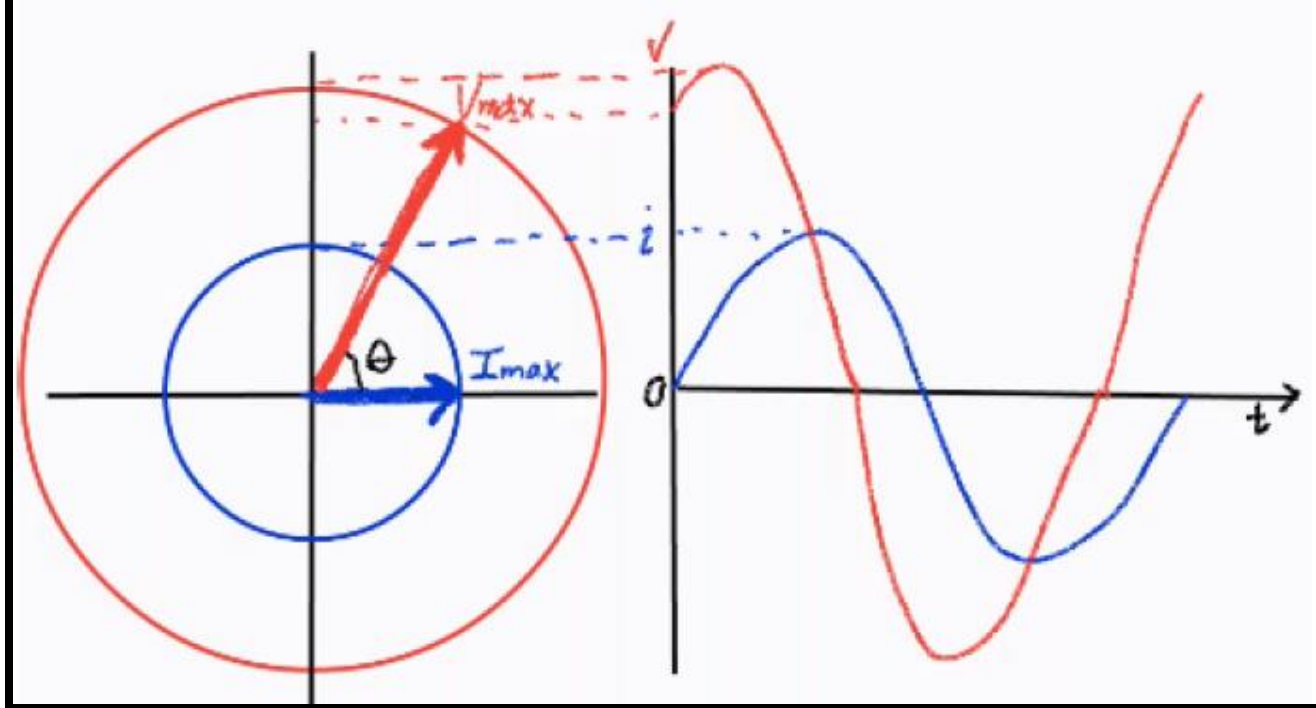

# Euler's Formula

$$e^{j\theta} = \cos(\theta) + j \sin(\theta)$$

$$e^{-j\theta} = \cos(\theta) - j \sin(\theta)$$

$$\cos(\theta) = \operatorname{Re}(e^{j\theta})$$

$$\sin(\theta) = \operatorname{Im}(e^{j\theta})$$

$$|e^{j\theta}| = \sqrt{\cos^2(\theta) + \sin^2(\theta)} = 1$$

$$e^{j\theta} = 1 \angle \theta$$

$$e^{j\theta} = \cos(\theta) + j \sin(\theta)$$

$$e^{j\pi} = \cos(\pi) + j \sin(\pi) = -1$$

$$e = 2.718281828459045235360287\dots = \lim_{n \rightarrow \infty} \left( 1 + \frac{1}{n} \right)^n$$

$$\pi = 3.141592653589793238462643\dots$$

$$j = \sqrt{-1}$$

$$e^{j\pi} = -1$$

$$\begin{aligned} \sin \omega t &= \cos \omega t - 90^\circ \\ \cos \omega t &= \sin \omega t + 90^\circ = -\sin \omega t - 90^\circ \end{aligned}$$

$$\sin \omega t = \cos(\omega t - 90^\circ)$$